

# Output Stages and Power Amplifiers

張大中

中央大學 通訊工程系

dcchang@ce.ncu.edu.tw

# Power BJTs

- ❑ Power transistors are large-area devices. Because of difference in geometry and doping concentrations, their properties tend to vary from those of the small-signal devices.
- ❑ The current gain of power BJTs is generally smaller in the range of 20 to 100, and may be a strong function of collector current and temperature.
- ❑ At high current levels, the current gain tends to drop off significantly, and parasitic resistances in the base and collector regions may become significant, affecting the transistor terminal characteristics.
- ❑ The maximum rated collector current  $I_{C, \text{rated}}$
- ❑ The avalanche breakdown voltage (when the base is open)  $V_{CEO}$
- ❑ The minimum voltage sustaining the transistor in breakdown  $V_{CE(sus)}$
- ❑ Second breakdown: permanent failure

 


Figure 8.1 Typical dc beta characteristics ( $h_{FE}$  versus  $I_C$ ) for 2N3055

 


Figure 8.2 Typical collector current versus collector-emitter voltage characteristics of a bipolar transistor, showing breakdown effects

# Safe Operating Area of BJTs

- The instantaneous and average power dissipation

$$p_Q = v_{CE}i_C + v_{BE}i_B \approx v_{CE}i_C$$

$$\bar{P}_Q = \frac{1}{T} \int_0^T v_{CE}i_C dt$$

- DC maximum rated power



$$P_T = V_{CE}I_C$$

- Safe Operating Area (SOA): The region where the transistor can be operated safely.

✓ SOA is bounded by

$$I_{C,rated}, V_{CE(sus)}, P_T,$$

Second breakdown curve

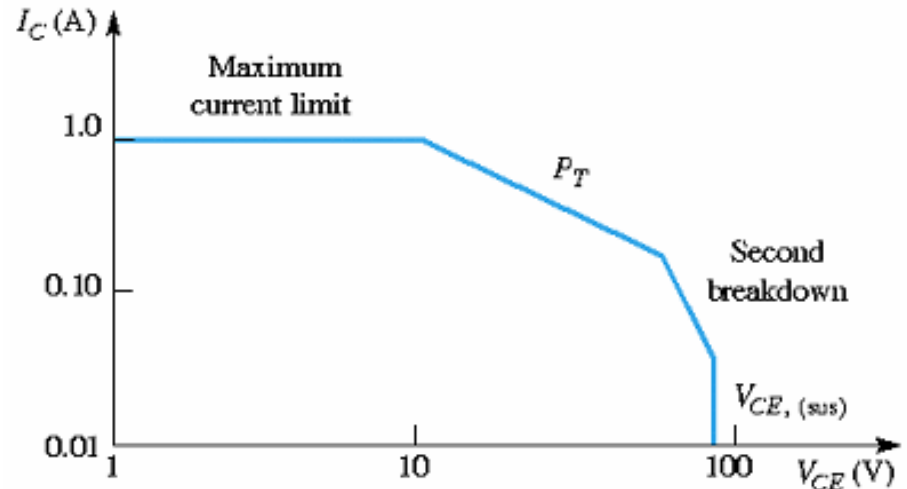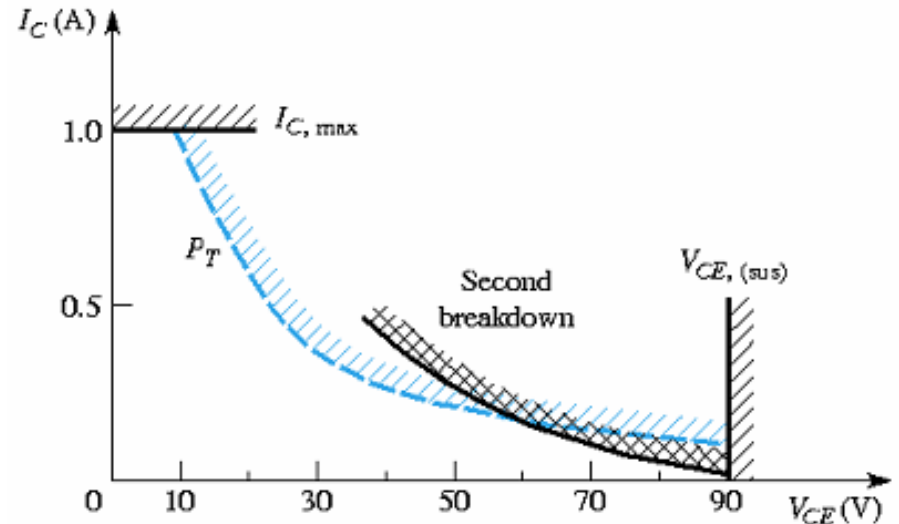

**Example 8.1 Objective:** Determine the required current, voltage, and power ratings of a power BJT.

Consider the common-emitter circuit in Figure 8.4. The parameters are  $R_L = 8 \Omega$  and  $V_{CC} = 24 \text{ V}$ .

**Solution:** For  $V_{CE} \approx 0$ , the maximum collector current is

$$I_C(\text{max}) = \frac{V_{CC}}{R_L} = \frac{24}{8} = 3 \text{ A}$$

For  $I_C = 0$ , the maximum collector-emitter voltage is

$$V_{CE}(\text{max}) = V_{CC} = 24 \text{ V}$$

The load line is given by

$$V_{CE} = V_{CC} - I_C R_L$$

and must remain within the safe operating area, as shown in Figure 8.5.

The transistor power dissipation is therefore

$$P_T = V_{CE} I_C = (V_{CC} - I_C R_L) I_C = V_{CC} I_C - I_C^2 R_L$$

The current at which the maximum power occurs is found by setting the derivative of this equation equal to zero as follows:

$$\frac{dP_T}{dI_C} = 0 = V_{CC} - 2I_C R_L$$

which yields

$$I_C = \frac{V_{CC}}{2R_L} = \frac{24}{2(8)} = 1.5 \text{ A}$$


The C-E voltage at the maximum power point is

$$V_{CE} = V_{CC} - I_C R_L = 24 - (1.5)(8) = 12 \text{ V}$$


The maximum power dissipation in the transistor occurs at the center of the load line.

The maximum transistor power dissipation is therefore

$$P_T = V_{CE} I_C = 12(1.5) = 18 \text{ W}$$

 

**Figure 8.4** Figure for Example 8.1

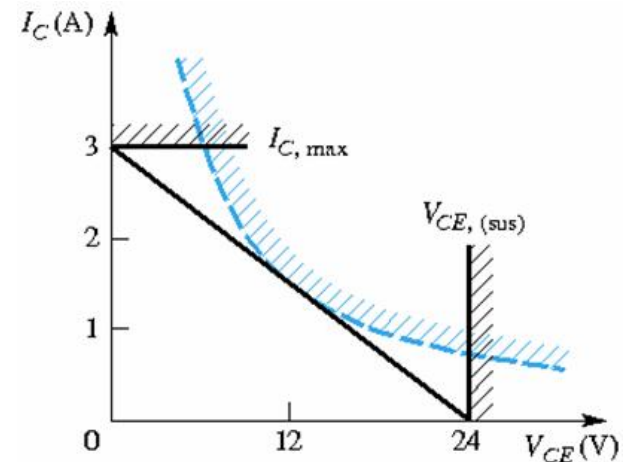


## Power MOSFETs

- ❑ The superior performance characteristics of power MOSFETs
  - ✓ Faster switching times
  - ✓ No second breakdown
  - ✓ Stable gain and response over a wide temperature range
  
- ❑ A MOSFET is a high impedance, voltage-controlled device, the drive circuitry is simpler.
  - ✓ The gate of a 10A power MOSFET may be driven by the output of a standard logic circuit.
  - ✓ In contrast, if the current gain of a 10A BJT is  $\beta = 10$ , then a base current of 1A is required for a collector current of 10A.

## Heat Sinks

- ❑ The power dissipated in a transistor increases its internal temperature above the ambient temperature.
- ❑ If the device or junction temperature becomes too high, the transistor may suffer permanent damage.
- ❑ Special precautions must be taken in packaging power transistors and in providing heat sinks so that heat can be conducted from the transistor.

 

**Figure 8.10** Two packaging schemes: (a) and (b) for power transistors and (c) typical heat sink


## Thermal Resistance

- The temperature difference across an element with a thermal resistance  $\theta$  is

$$T_2 - T_1 = P\theta$$

$P$ : thermal power through the element

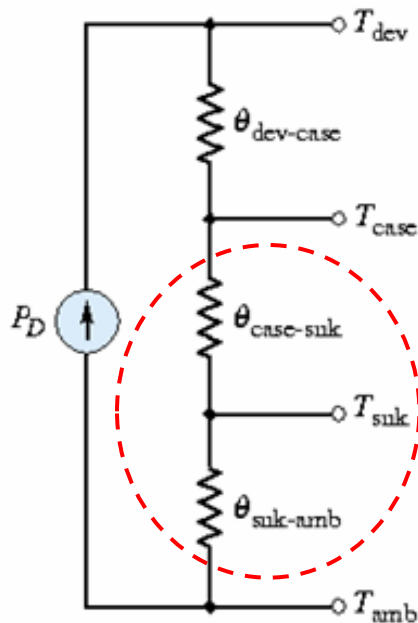- Electrical equivalent circuit for heat flow from the device to the ambient



When a heat sink is used:

$$T_{dev} - T_{amb} = P_D (\theta_{dev-case} + \theta_{case-sink} + \theta_{sink-amb})$$

When a heat sink is not used:

$$T_{dev} - T_{amb} = P_D (\theta_{dev-case} + \theta_{case-amb})$$

**Figure 8.11** Electrical equivalent circuit for heat flow from the device to the ambient

**Example 8.2 Objective:** Determine the maximum power dissipation in a transistor.

Consider a power MOSFET for which the thermal resistance parameters are:

$$\theta_{\text{dev-case}} = 1.75 \text{ }^\circ\text{C/W} \quad \theta_{\text{case-snk}} = 1 \text{ }^\circ\text{C/W}$$

$$\theta_{\text{snk-amb}} = 5 \text{ }^\circ\text{C/W} \quad \theta_{\text{case-amb}} = 50 \text{ }^\circ\text{C/W}$$

The ambient temperature is  $T_{\text{amb}} = 30 \text{ }^\circ\text{C}$ , and the maximum junction or device temperature is  $T_{j,\text{max}} = T_{\text{dev}} = 150 \text{ }^\circ\text{C}$ .

**Solution:** When no heat sink is used, the maximum device power dissipation is found from Equation (8.7) as

$$P_{D,\text{max}} = \frac{T_{j,\text{max}} - T_{\text{amb}}}{\theta_{\text{dev-case}} + \theta_{\text{case-amb}}} = \frac{150 - 30}{1.75 + 50} = 2.32 \text{ W}$$

When a heat sink is used, the maximum device power dissipation is found from Equation (8.6) as


$$\begin{aligned} P_{D,\text{max}} &= \frac{T_{j,\text{max}} - T_{\text{amb}}}{\theta_{\text{dev-case}} + \theta_{\text{case-snk}} + \theta_{\text{snk-amb}}} \\ &= \frac{150 - 30}{1.75 + 1 + 5} = 15.5 \text{ W} \end{aligned}$$

**Comment:** These results illustrate that the use of a heat sink allows more power to be dissipated in the device, while keeping the device temperature at or below its maximum limit.



## Classes of Power Amplifiers

- ❑ Power amplifiers are classified according to the percent of time the **output transistors** are conducting (turned on).
- ❑ Four principal classifications: class-A, class-B, class-AB, class-C

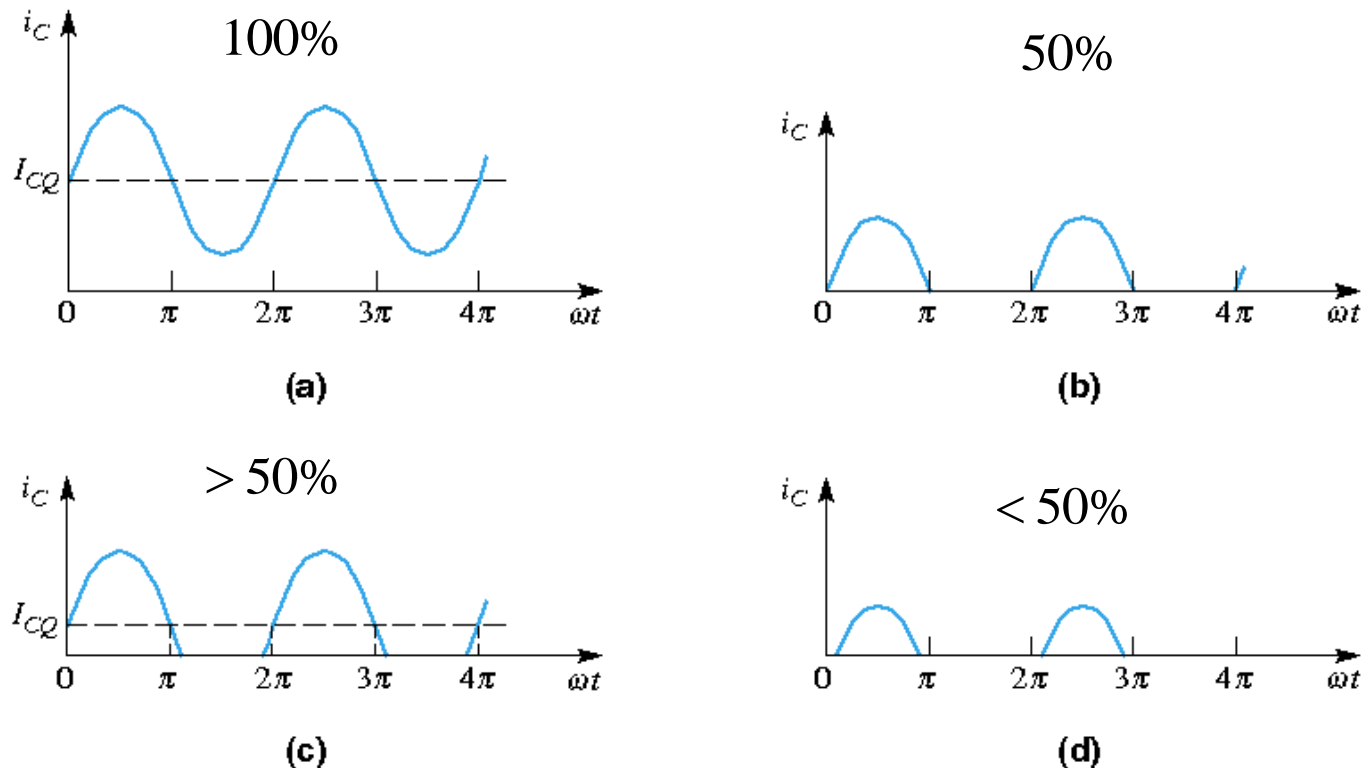

**Figure 8.15** Collector current versus time characteristics: (a) class-A amplifier, (b) class-B amplifier, (c) class-AB amplifier, and (d) class-C amplifier

# Class-A Operation

## Standard Class-A Amplifier

$$p_Q = v_{CE} i_C$$

$$i_C = I_{CQ} + I_{CQ} \sin \omega t$$


$$v_{CE} = \frac{V_{CC}}{2} - \frac{V_{CC}}{2} \sin \omega t$$

$$p_Q = v_{CE} i_C = \frac{V_{CC} I_{CQ}}{2} (1 - \sin^2 \omega t)$$

Load average **ac power**  $\bar{P}_L = \frac{1}{2} \cdot \frac{V_{CC}}{2} \cdot I_{CQ} = \frac{V_{CC} I_{CQ}}{4}$

Power supply  $\bar{P}_S = V_{CC} I_{CQ}$


Power Conversion Efficiency  $\eta = \frac{\bar{P}_L}{\bar{P}_S} = 25\%$

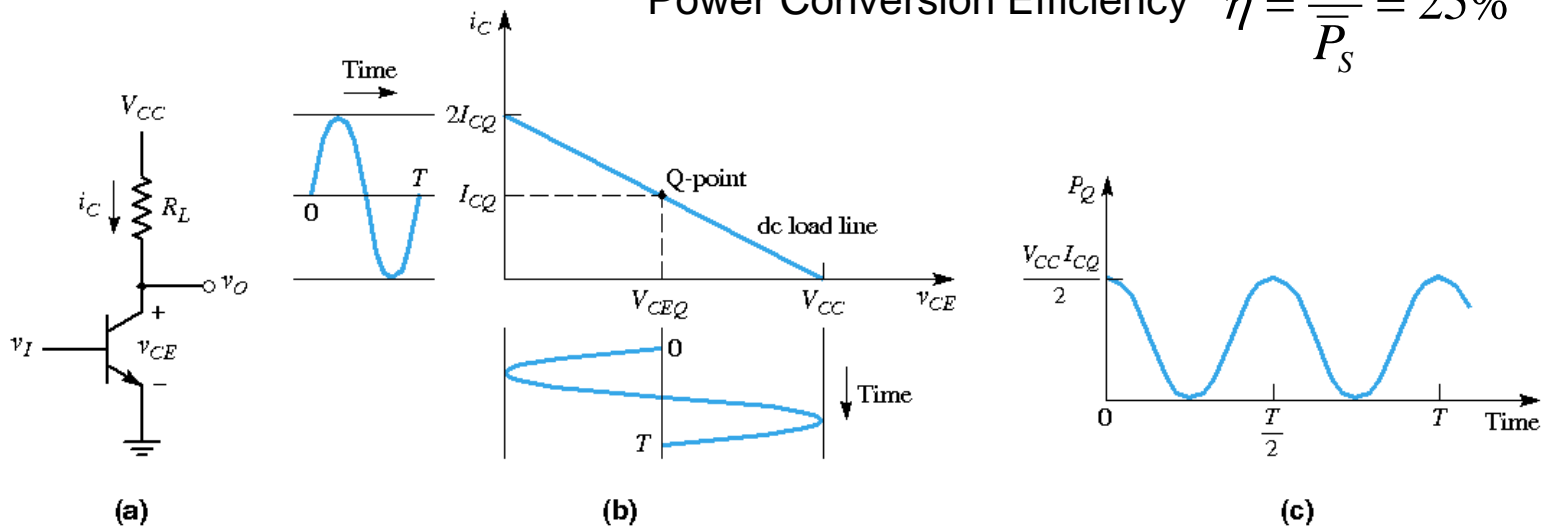

**Figure 8.16** (a) Common-emitter amplifier, (b) dc load line, and (c) instantaneous power dissipation versus time in the transistor

 **Example 8.4 Objective:** Calculate the actual efficiency of a class-A output stage.

Consider the common-source circuit in Figure 8.13. The circuit parameters are  $V_{DD} = 10\text{ V}$  and  $R_D = 5\text{ k}\Omega$ , and the transistor parameters are:  $K_n = 1\text{ mA/V}^2$ ,  $V_{TN} = 1\text{ V}$ , and  $\lambda = 0$ . Assume the output voltage swing is limited to the range between the transition point and  $v_{DS} = 9\text{ V}$ , to minimize nonlinear distortion.



**Solution:** The load line is given by

$$V_{DS} = V_{DD} - I_D R_D$$

At the transition point, we have

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

and

$$I_D = K_n (V_{GS} - V_{TN})^2$$

Combining these expressions, the transition point is determined from

$$V_{DS}(\text{sat}) = V_{DD} - K_n R_D V_{DS}^2(\text{sat})$$

or

$$(1)(5)V_{DS}^2(\text{sat}) + V_{DS}(\text{sat}) - 10 = 0$$

which yields

$$V_{DS}(\text{sat}) = 1.32\text{ V}$$

To obtain the maximum symmetrical swing under the conditions specified, we want the  $Q$ -point midway between  $V_{DS} = 1.32\text{ V}$  and  $V_{DS} = 9\text{ V}$ , or

$$V_{DSQ} = 5.16\text{ V}$$

The maximum ac component of voltage across the load resistor is then

$$v_r = 3.84 \sin \omega t$$

and the average power delivered to the load is

$$\bar{P}_L = \frac{1}{2} \cdot \frac{(3.84)^2}{5} = 1.47\text{ mW}$$

The quiescent drain current is found to be

$$I_{DQ} = \frac{10 - 5.16}{5} = 0.968\text{ mA}$$

The average power supplied by the  $V_{DD}$  source is


$$\bar{P}_S = V_{DD} I_{DQ} = (10)(0.968) = 9.68\text{ mW}$$

and the power conversion efficiency, from Equation (8.12), is

$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{1.47}{9.68} \Rightarrow 15.2\%$$

# Class-B Operation

## Complementary Push-Pull Output Stage

 

**Figure 8.18** Basic complementary push-pull output stage

$$1. -0.6V < v_I < 0.6V$$


Qn: off, Qp: off  
 $v_o = 0$

$$2. v_I > 0.6V$$


Qn: on, Qp: off  
 $v_o = v_I - 0.6$

$$3. v_I < -0.6V$$

Qn: off, Qp: on  
 $v_o = v_I + 0.6$

 

**Figure 8.19** Voltage transfer characteristics of basic complementary push-pull output stage

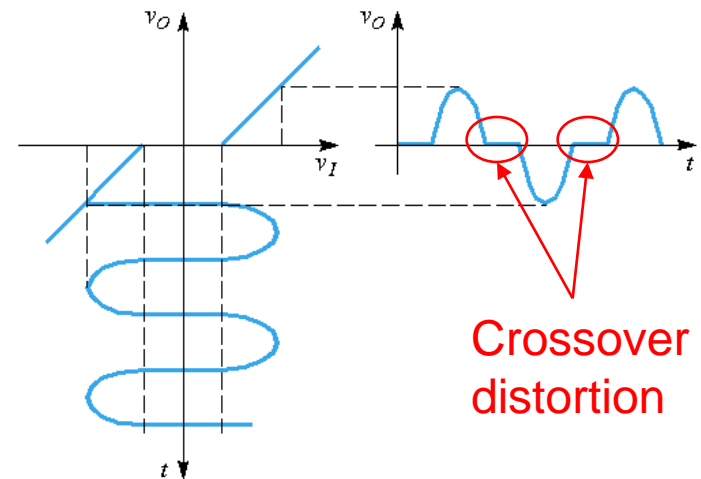

**Figure 8.20** Crossover distortion of basic complementary push-pull output stage

# Power Efficiency

For idealized class-B output stage,

$$v_O = V_p \sin \omega t$$

The instantaneous power dissipation in  $Q_n$  is

$$P_{Qn} = v_{CEn} i_{Cn}$$

$$(1) \quad 0 \leq \omega t < \pi$$

$$i_{Cn} = \frac{v_O}{R_L} = \frac{V_p}{R_L} \sin \omega t$$

$$v_{CEn} = V_{CC} - V_p \sin \omega t$$


$$P_{Qn} = (V_{CC} - V_p \sin \omega t) \left( \frac{V_p}{R_L} \sin \omega t \right)$$

$$(2) \quad \pi \leq \omega t < 2\pi$$


$$i_{Cn} = 0 \quad P_{Qn} = 0$$

The average power dissipation in  $Q_n$  is

$$\bar{P}_{Qn} = \frac{1}{2\pi} \int_0^\pi \left( \frac{V_{CC} V_p}{R_L} \sin \theta - \frac{V_p^2}{R_L} \sin^2 \theta \right) d\theta = \frac{V_{CC} V_p}{\pi R_L} - \frac{V_p^2}{4R_L}$$

 

**Figure 8.18** Basic complementary push-pull output stage

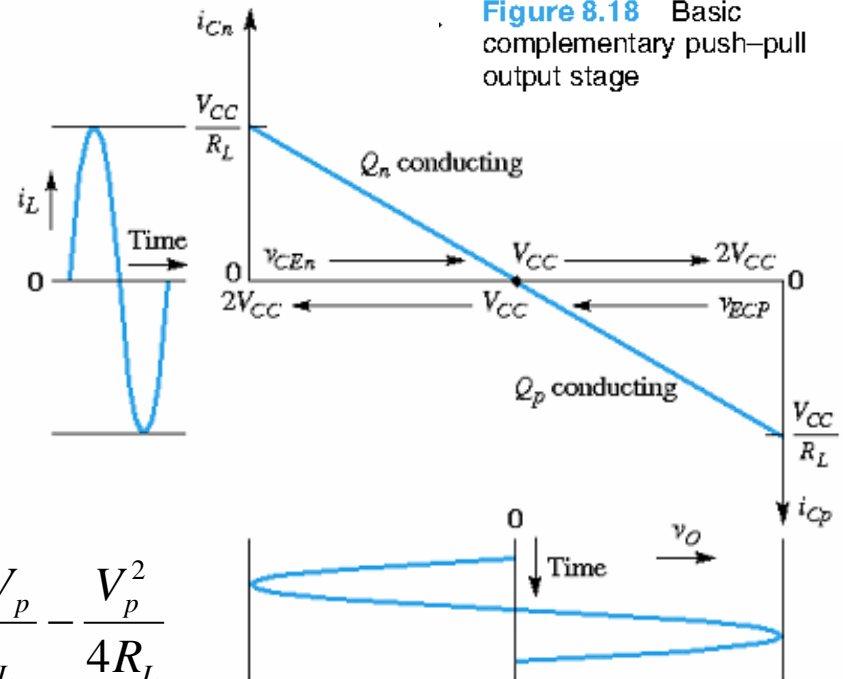

**Figure 8.21** Effective load line of the class-B output stage

# Power Efficiency

- Maximum average power dissipation setting the derivative of  $\bar{P}_{Qn}$  with respect to  $V_p$  equal to zero,

$$\bar{P}_{Qn}(\max) = \frac{V_{CC}^2}{\pi^2 R_L}$$

$$V_{P|\bar{P}_{Qn}(\max)} = \frac{2V_{CC}}{\pi}$$

- Power conversion efficiency



The average power delivered to the load  $\bar{P}_L = \frac{1}{2} \frac{V_p^2}{R_L}$

The average current supplied by each source  $\frac{1}{2\pi} \int_0^\pi \frac{V_p}{R_L} \sin \theta d\theta = \frac{V_p}{\pi R_L}$

The average current supplied by each source  $\bar{P}_{V^+} = \bar{P}_{V^-} = \frac{V_{CC} V_p}{\pi R_L}$

The total average power  $\bar{P}_S = \frac{2V_{CC} V_p}{\pi R_L}$

  The conversion efficiency  $\eta = \left( \frac{1}{2} \frac{V_p^2}{R_L} \right) / \left( \frac{2V_{CC} V_p}{\pi R_L} \right) = \frac{\pi}{4} \frac{V_p}{V_{CC}}$



## Maximum Conversion Efficiency

- Maximum Conversion Efficiency

$$\eta = \frac{\pi}{4} \frac{V_p}{V_{CC}}, \quad V_p \leq V_{CC}$$

$$\eta(\text{max}) = \frac{\pi}{4} = 78.5\%, \quad \text{when } V_p = V_{CC}$$

- Actual Conversion Efficiency: less than 78.5%

- ✓ Circuit losses

- ✓ Peak output voltage less than  $V_{CC}$  to avoid transistor saturation

- Conversion Efficiency when the maximum transistor power dissipation occurs

$$V_{P|\bar{P}_{Qn(\text{max})}} = \frac{2V_{CC}}{\pi}$$

$$\eta(\bar{P}_{Qn(\text{max})}) = \frac{\pi}{4} \frac{V_p}{V_{CC}} = \frac{\pi}{4} \frac{2V_{CC}/\pi}{V_{CC}} = 1/2 = 50\%$$

## Class-AB Operation

- Class-AB output stage: applying a small quiescent bias on each output transistor to eliminate crossover distortion.

Let  $v_I = 0, v_O = 0$ , then  $V_{BB}/2$  is applied to the B/E junction.

$$i_{Cn} = i_{Cp} = I_S e^{V_{BB}/2V_T}$$

(1) As  $v_I$  increases,

$$v_O = v_I + V_{BB}/2 - v_{BE n}$$

$$i_{Cn} = i_L + i_{Cp}$$

$$v_O \uparrow \Rightarrow i_L \uparrow \Rightarrow i_{Cn} \uparrow \Rightarrow v_{BE n} \uparrow \Rightarrow v_{EB p} \downarrow \Rightarrow i_{Cp} \downarrow$$

(2) As  $v_I$  goes negative,

$$v_O = v_I - V_{BB}/2 + v_{EB p}$$

$$v_O \downarrow \Rightarrow v_{EB p} \uparrow \Rightarrow i_{Cp} \uparrow \Rightarrow v_{BE n} \downarrow \Rightarrow i_{Cn} \downarrow$$

 


Figure 8.23 Bipolar class-AB output stage




# Class-AB Operation

$$V_{BE_n} + v_{EB_p} = V_{BB}$$


$$V_T \ln\left(\frac{i_{C_n}}{I_S}\right) + V_T \ln\left(\frac{i_{C_p}}{I_S}\right) = 2V_T \ln\left(\frac{I_{C_Q}}{I_S}\right)$$

$I_{C_Q}$  : quiescent collector current

$$i_{C_n} i_{C_p} = I_{C_Q}^2$$

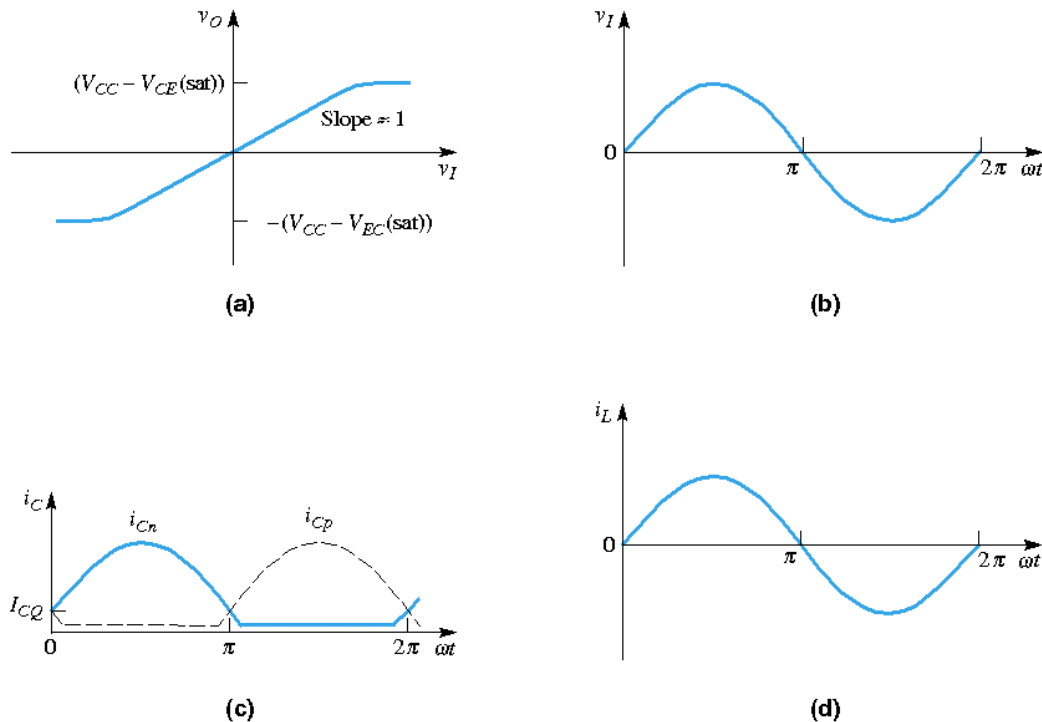

**Figure 8.24** Characteristics of a class-AB output stage: (a) voltage transfer curve, (b) sinusoidal input signal, (c) collector currents, and (d) output current

 

**Figure 8.23** Bipolar class-AB output stage

## Advantage of Class-AB Output Stages

- ❑ For a zero input signal, quiescent collector currents exist in the output transistors, the average power supplied by each source and the average power dissipated in each transistor are larger than for a class-B configuration.
  - ✓ Power conversion efficiency is less than for an idealized class-B circuit.
  
- ❑ The quiescent collector currents are usually small compared to the peak current, this increase in power dissipation is not great.
  
- ❑ The advantage of eliminating crossover distortion in the class-AB output stage greatly outweighs the slight disadvantage of reduced conversion efficiency and increased power dissipation.

**Example 8.7 Objective:** Determine the required biasing in a MOSFET class-AB output stage.

The circuit is shown in Figure 8.25. The parameters are  $V_{DD} = 10\text{ V}$  and  $R_L = 20\ \Omega$ . The transistors are matched, and the parameters are  $K = 0.20\text{ A/V}^2$  and  $|V_T| = 1\text{ V}$ . The quiescent drain current is to be 20 percent of the load current when  $v_O = 5\text{ V}$ .

**Solution:** For  $v_O = 5\text{ V}$ ,

$$i_L = 5/20 = 0.25\text{ A}$$

Then, for  $I_Q = 0.05\text{ A}$  when  $v_O = 0$ , we have

$$I_{DQ} = 0.05 = K \left( \frac{V_{BB}}{2} - |V_T| \right)^2 = (0.20) \left( \frac{V_{BB}}{2} - 1 \right)^2$$

which yields

$$V_{BB}/2 = 1.50\text{ V}$$

The input voltage for  $v_O$  positive is

$$v_I = v_O + v_{GSn} - \frac{V_{BB}}{2}$$

For  $v_O = 5\text{ V}$  and  $i_{Dn} \cong i_L = 0.25\text{ A}$ , we have


$$v_{GSn} = \sqrt{\frac{i_{Dn}}{K}} + |V_T| = \sqrt{\frac{0.25}{0.20}} + 1 = 2.12\text{ V}$$

The source-to-gate voltage of  $M_p$  is

$$v_{SGp} = V_{BB} - V_{GSn} = 3 - 2.12 = 0.88\text{ V}$$

which means that  $M_p$  is cut off and  $i_{Dn} = i_L$ . Finally, the input voltage is


$$v_I = 5 + 2.12 - 1.5 = 5.62\text{ V}$$

 

**Figure 8.25** MOSFET class-AB output stage

## Class-C Operation

- ❑ For class-C operation, the transistor has a reverse-biased BE voltage at the Q-point.
- ❑ The collector current is not negative, but is zero at the quiescent point.
- ❑ The transistor conducts for less than a half-cycle, which defines class-C operation.
- ❑ Conversion efficiency is large than 78.5% and usually used for RF circuits.

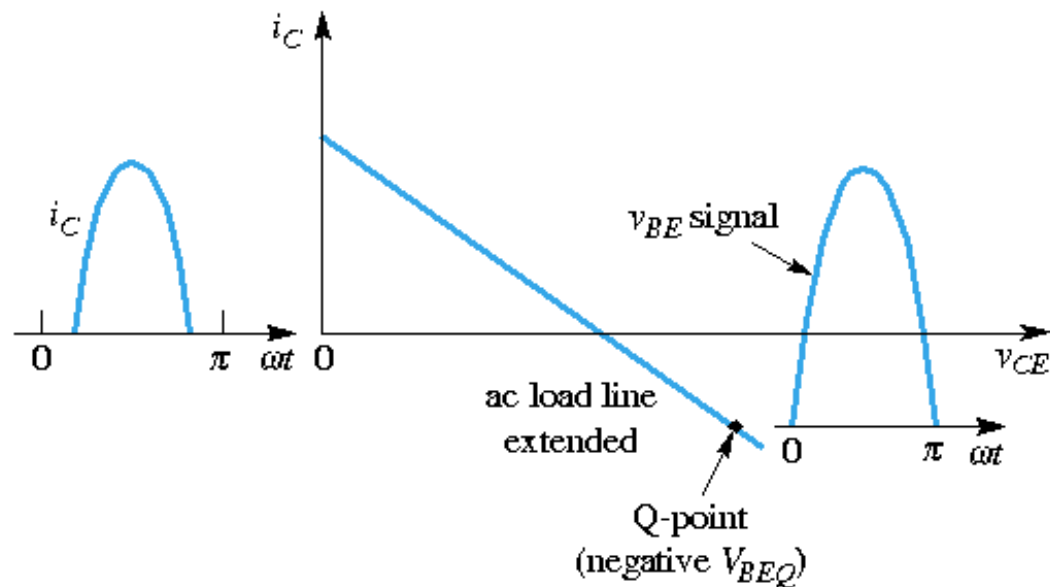

**Figure 8.26** Effective ac load line of a class-C amplifier