

#1

$$(a) \quad T_{j,\max} - T_{amb} = P_T (\theta_{dev-case} + \theta_{snk-amb} + \theta_{case-snk})$$

$$120 - 25 = P_T (1.5 + 2.8 + 0.6) \Rightarrow P_T = 19.39 \text{ W}$$

$$(b) \quad T_{case} = 25 + (19.39)(0.6 + 2.8) = 90.9^\circ\text{C}$$

$$(c) \quad T_{snk} = 25 + (19.39)(2.8) = 79.3^\circ\text{C}$$


---

#2

$$(a) \quad V_{CEQ} = 6 = V_{CC} - I_{CQ} R_L = 12 - I_{CQ}(1) \Rightarrow I_{CQ} = 6 \text{ mA}$$

$$P_Q = I_{CQ} V_{CEQ} = (6)(6) = 36 \text{ mW}$$

$$(b) \quad (i) \quad \bar{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{1}{2} \cdot \frac{(4.5)^2}{1} = 10.1 \text{ mW}$$

$$(ii) \quad \eta = \frac{10.1}{I_{CQ} V_{CC}} \times 100\% = \frac{10.1}{(6)(12)} \times 100\% = 14.1\%$$

$$(iii) \quad \bar{P}_Q = 36 - 10.1 = 25.9 \text{ mW}$$


---

#3

$$(a) \quad \text{For } v_o = 8 \text{ V, } i_L = \frac{8}{25} = 0.32 \text{ A}$$

$$I_{DQ} = (0.2)(0.32) \Rightarrow 64 \text{ mA}$$

$$I_{DQ} = K(V_{GS} - V_{TN})^2$$

$$64 = 250(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = \frac{V_{BB}}{2} = 1.706 \text{ V}$$

$$\text{Then } V_{BB} = 3.412 \text{ V}$$


---

#4

See textbook P642-643

#5

We have the general relation that

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{[R_4/R_3]}{1 + [R_4/R_3]}\right) v_{I2} - \frac{R_2}{R_1} v_{I1}$$

$$R_1 = R_3 = 10 \text{ k}\Omega, \quad R_2 = 20 \text{ k}\Omega, \quad R_4 = 21 \text{ k}\Omega$$

$$v_o = \left(1 + \frac{20}{10}\right) \left(\frac{[21/10]}{1 + [21/10]}\right) v_{I2} - \left(\frac{20}{10}\right) v_{I1}$$

$$v_o = 2.0323v_{I2} - 2.0v_{I1}$$

$$A_{cm} = \frac{v_o}{v_{cm}} = 0.0323$$

$$CMRR_{dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}}\right)$$

$$A_d = \frac{2.0323}{2} - (2.0) \left(-\frac{1}{2}\right) = 2.016$$

$$CMRR_{dB} = 20 \log_{10} \left(\frac{2.016}{0.0323}\right) = 35.9 \text{ dB}$$

---

#6

See textbook

---

#7

$$v_{OB} = \left(1 + \frac{40}{12}\right) v_I$$

$$v_{OC} = -\frac{30}{12} v_I$$

$$v_O = v_{OB} - v_{OC}$$

$$\frac{v_O}{v_I} = \frac{3.417}{0.5} = 6.83$$