

Electronics II, Spring 2016 Exam3 Solution 2016/5/13

#1 (15%)

$$V_{BE1} + I_{REF}R_{E1} = V_{BE2} + I_0R_{E2}$$

$$V_{BE1} - V_{BE2} = I_0R_{E2} - I_{REF}R_{E1}$$

For matched transistors

$$V_{BE1} = V_T \ln\left(\frac{I_{REF}}{I_S}\right)$$

$$V_{BE2} = V_T \ln\left(\frac{I_0}{I_S}\right)$$

$$\text{Then } V_T \ln\left(\frac{I_{REF}}{I_0}\right) = I_0R_{E2} - I_{REF}R_{E1}$$

#2 (20%)

$$I_{REF} = \left(\frac{50}{2}\right)(15)(V_{SG1} - 0.5)^2 = \left(\frac{50}{2}\right)(3)(V_{SG3} - 0.5)^2$$

$$V_{SG1} + V_{SG3} = 10 \Rightarrow V_{SG3} = 10 - V_{SG1}$$

$$\sqrt{\frac{15}{3}}(V_{SG1} - 0.5) = 10 - V_{SG1} - 0.5$$


$$3.236V_{SG1} = 10.618 \Rightarrow V_{SG1} = 3.28 \text{ V}$$

$$I_{REF} = \left(\frac{50}{2}\right)(15)(3.28 - 0.5)^2 \Rightarrow I_{REF} = 2.90 \text{ mA}$$

$$I_O = I_{REF} = 2.90 \text{ mA}$$

$$V_{SD2}(\text{sat}) = V_{SG2} + V_{TP} = 3.28 - 0.5 \Rightarrow \underline{V_{SD2}(\text{sat}) = 2.78 \text{ V}}$$

#3 (20%)

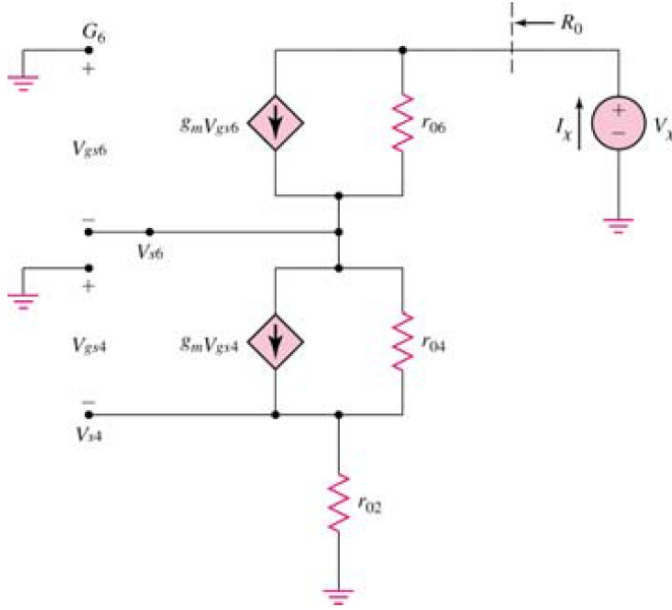

$$V_{gs4} = -I_X r_{02}$$

$$V_{S6} = (I_X - g_m V_{gs4}) r_{04} + I_X r_{02}$$

$$= (I_X + g_m I_X r_{02}) r_{04} + I_X r_{02}$$

$$V_{S6} = I_X [r_{02} + (1 + g_m r_{02}) r_{04}] = -V_{gs6}$$

$$I_X = g_m V_{gs6} + \frac{V_X - V_{S6}}{r_{06}} = \frac{V_X}{r_{06}} - V_{S6} \left(g_m + \frac{1}{r_{06}} \right)$$

$$I_X = \frac{V_X}{r_{06}} - I_X \left(g_m + \frac{1}{r_{06}} \right) [r_{02} + (1 + g_m r_{02}) r_{04}]$$

$$I_X \left\{ 1 + \left(g_m + \frac{1}{r_{06}} \right) [r_{02} + (1 + g_m r_{02}) r_{04}] \right\} = \frac{V_X}{r_{06}}$$

$$\frac{V_X}{I_X} = R_0 = r_{06} + (1 + g_m r_{06}) [r_{02} + (1 + g_m r_{02}) r_{04}]$$

$$I_0 \approx I_{REF} = 0.2 \text{ mA} = 0.2 (V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.2)(2 - 1) = 0.4 \text{ mA/V}$$

$$r_{02} = r_{04} = r_{06} = \frac{1}{\lambda I_0} = \frac{1}{(0.02)(0.2)} = 250 \text{ k}\Omega$$

$$R_0 = 250 + [1 + (0.4)(250)] \times \{ 250 + [1 + (0.4)(250)](250) \}$$

$$R_0 = 2575750 \text{ k}\Omega \Rightarrow \underline{R_0 = 2.58 \times 10^9 \Omega}$$

#4 (25%)

$$g_{m1} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_1 I_{D1}} = 2\sqrt{\left(\frac{0.1}{2}\right)(20)(0.1)} = 0.6325 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_n I_{D1}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$R_{o2} = r_{o2} + r_{o3}(1 + g_{m2}r_{o2})$$

$$g_{m2} = 2\sqrt{\left(\frac{0.06}{2}\right)(80)(0.1)} = 0.9798 \text{ mA/V}$$

$$r_{o2} = r_{o3} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$R_{o2} = 500 + 500[1 + (0.9798)(500)] = 245,949 \text{ k}\Omega$$

$$A_v = -g_{m1}(r_{o1} \parallel R_{o2}) = -(0.6325)(500 \parallel 245,949) = -316$$

#5 (20%)

$$24 = I_{REF}R + V_{SG} + V_{GS}$$

$$V_{SG} = \sqrt{\frac{I_{REF}}{\left(\frac{k'_p}{2}\right)(1)}} - V_{TP} = 5.7735\sqrt{I_{REF}} + 0.8$$

$$V_{GS} = \sqrt{\frac{I_{REF}}{\left(\frac{k'_n}{2}\right)(1)}} + V_{TN} = 4.472\sqrt{I_{REF}} + 0.8$$

$$\text{So } 24 = I_{REF}(100) + 5.7735\sqrt{I_{REF}} + 0.8 + 4.4721\sqrt{I_{REF}} + 0.8$$

$$\text{Let } \sqrt{I_{REF}} = x$$

$$\text{Then } 100x^2 + 10.2456x - 22.4 = 0 \Rightarrow x = 0.4248 \Rightarrow x^2 = I_{REF} = 0.1805 \text{ mA}$$

$$I_1 = (0.2)I_{REF} = 0.0361 \text{ mA}$$

$$I_2 = (1.25)I_{REF} = 0.2256 \text{ mA}$$

$$I_3 = (0.8)I_{REF} = 0.1444 \text{ mA}$$

$$I_4 = (4)I_{REF} = 0.722 \text{ mA}$$