

**1. (total 30 points: 5 points, 10 points, 10 points, 5 points)**

For the circuit in Figure P7.21, the transistor parameters are  $\beta = 120$ ,  $V_{BE(on)} = 0.7$  V, and  $V_A = 50$  V. (a) Design a bias-stable circuit such that  $I_{EQ} = 1.5$  mA. (b) Using the results of part (a), find the small-signal mid-band voltage gain. (c) Determine the output resistance  $R_o$ . (d) What is the lower 3 dB corner frequency?

(Note: Bias-stable circuit means that  $R_{th} = 0.1 \times (1 + \beta)R_E$ .)

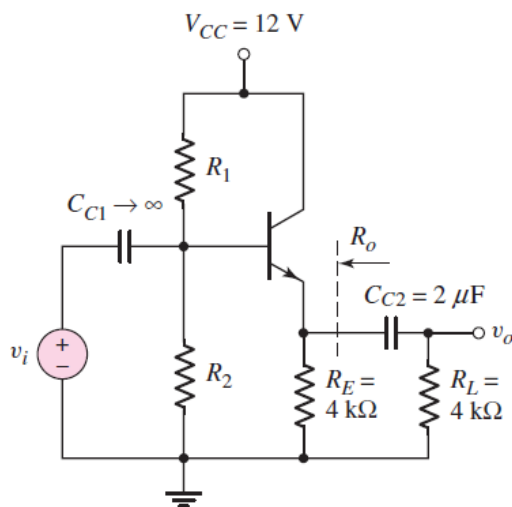


Figure P7.21

**2. (total 30 points: 15 points, 15 points)**

In the common-gate circuit in Figure P7.72, the transistor parameters are:  $V_{TN} = 1$  V,  $K_n = 3$  mA/V<sup>2</sup>,  $\lambda = 0$ ,  $C_{gs} = 15$  pF, and  $C_{gd} = 4$  pF. Determine the upper 3 dB frequency and midband voltage gain.


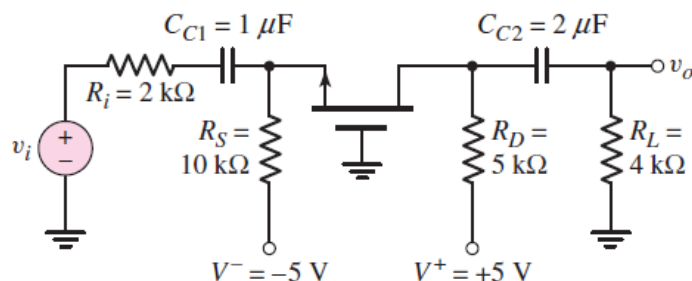


Figure P7.72

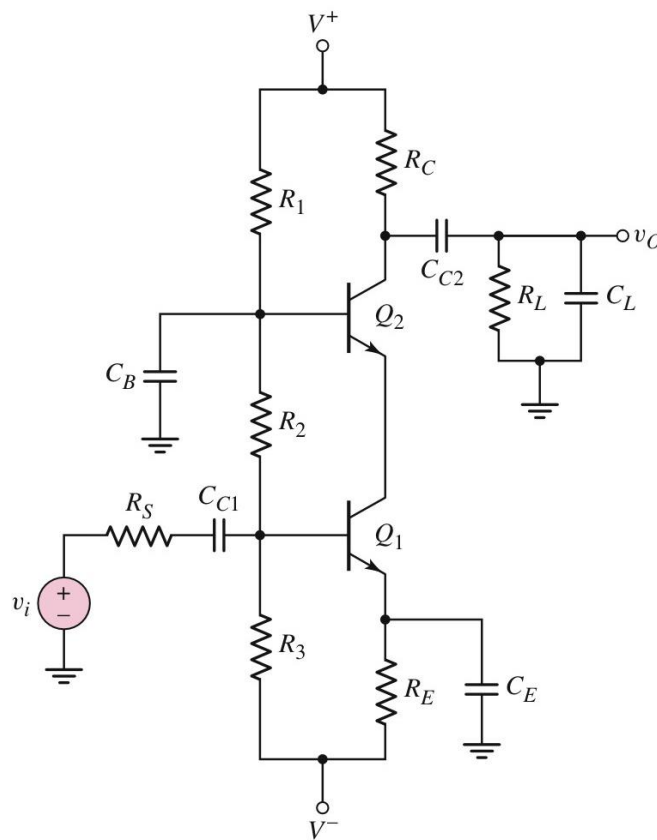**3. (total 40 points: 10 points, 10 points, 20 points)**

Assume that  $C_{C1}$ ,  $C_E$ , and  $C_{C2}$  acts as short circuits in this high frequency analysis.

- Derive the 3dB upper corner frequencies in terms of the transistor capacitors  $C_\mu$  and  $C_\pi$ .
- Derive the midband voltage gain.
- The circuit parameters are  $V^+ = 10V$ ,  $V^- = -10V$ ,  $R_S = 0.1k\Omega$ ,  $R_1 = 42.5k\Omega$ ,  $R_2 = 20.5k\Omega$ ,  $R_3 = 28.3k\Omega$ ,  $R_E = 5.4k\Omega$ ,  $R_C = 5k\Omega$ , and  $R_L = 10k\Omega$ . The transistor parameters are  $\beta_o = 150$ ,  $V_{BE(ON)} = 0.7V$ ,  $C_\pi = 12pF$ , and  $C_\mu = 2pF$ . Given that the quiescent collector current  $I_{CQ} = 1.02mA$ , determine the values of 3dB upper corner frequency for  $C_L$  acting as an open circuit and for  $C_L = 15pF$ .



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.