

#1

$$(a) R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(121)(4) = 48.4 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{EQ}}{1 + \beta} = \frac{1.5}{121} = 0.012397 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(\text{on}) + I_{EQ}R_E = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$\text{so } \frac{1}{R_1}(48.4)(12) = (0.012397)(48.4) + 0.7 + (1.5)(4)$$

which yields  $R_1 = 79.6 \text{ k}\Omega$  and  $R_2 = 124 \text{ k}\Omega$

$$(b) I_{CQ} = \left(\frac{120}{121}\right)(1.5) = 1.488 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{1.488} = 2.097 \text{ k}\Omega, \quad r_o = \frac{50}{1.488} = 33.6 \text{ k}\Omega$$

$$A_v = \frac{(1 + \beta)(r_o \parallel R_E \parallel R_L)}{r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)}$$

$$\text{Now } r_o \parallel R_E \parallel R_L = 33.6 \parallel 4 \parallel 4 = 1.888 \text{ k}\Omega$$

$$A_v = \frac{(121)(1.888)}{2.097 + (121)(1.888)} = 0.991$$

$$(c) R_o = R_E \parallel r_o \parallel \frac{r_\pi}{1 + \beta} = 4 \parallel 33.6 \parallel \frac{2.097}{121} \Rightarrow R_o = 17.25 \Omega$$

$$(d) f_L = \frac{1}{2\pi(R_o + R_L)C_{C2}} = \frac{1}{2\pi(17.25 + 4000)(2 \times 10^{-6})}$$

$$f_L = 19.8 \text{ Hz}$$


---

#2

$$V_{GS} + I_D R_S = 5$$

$$I_D = \frac{5 - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$5 - V_{GS} = (3)(10)(V_{GS}^2 - 2V_{GS} + 1)$$

$$30V_{GS}^2 - 59V_{GS} + 25 = 0$$

$$V_{GS} = \frac{59 \pm \sqrt{(59)^2 - 4(30)(25)}}{2(30)} \Rightarrow V_{GS} = 1.349 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(3)(1.35 - 1)$$


$$g_m = 2.093 \text{ mA/V}$$

On the output:

$$\tau_{P\mu} = (R_D \parallel R_L) C_{gdT} = (5 \parallel 4) \times 10^3 \times (4 \times 10^{-12})$$

$$\tau_{P\mu} = 8.89 \times 10^{-9} \text{ s}$$
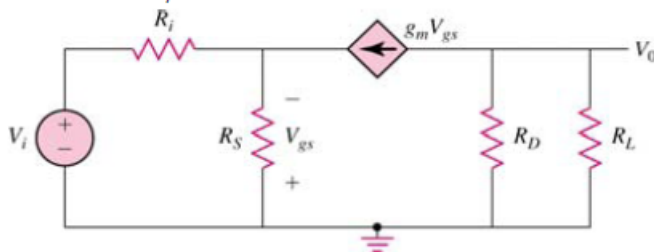
$$f_{P\mu} = \frac{1}{2\pi\tau_{P\mu}} \Rightarrow f_{P\mu} = 17.9 \text{ MHz}$$



$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$g_m V_{gs} + \frac{V_{gs}}{R_S} + \frac{V_i - (-V_{gs})}{R_S} = 0$$

$$V_{gs} \left( g_m + \frac{1}{R_S} + \frac{1}{R_S} \right) = -\frac{V_i}{R_S}$$

$$V_{gs} \left( 2.093 + \frac{1}{10} + \frac{1}{2} \right) = -\frac{V_i}{2}$$

$$V_{gs} = (0.1857)V_i$$

$$A_v = \frac{V_o}{V_i} = (2.093)(0.1857)(5 \parallel 4)$$

$$\underline{A_v = 0.864}$$

5.




$$C_{M1} = C_{M1} \left( 1 + \frac{g_{m2} r_{\pi 2}}{\beta} \right) = 2 C_{M1}$$

$$\tau_{\pi 1} = (R_S \parallel R_2 \parallel R_3 \parallel r_{\pi 1}) \cdot (C_{\pi 1} + C_{M1})$$

$$f_{HT} = \frac{1}{2\pi (R_S \parallel R_2 \parallel R_3 \parallel r_{\pi 1}) (C_{\pi 1} + 2C_{M1})} \quad *$$
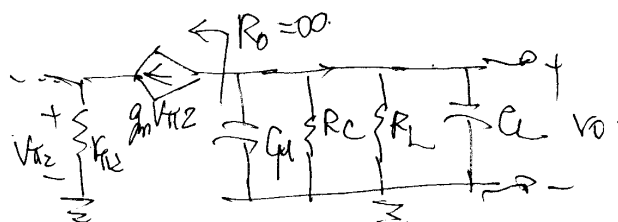
$$r_{\pi 1} = \frac{I_{C1}}{V_T}, \quad C_{\pi 1} = C_{\pi}, \quad C_{M1} = C_M$$



$$\tau_M = (R_C \parallel R_L) (C_M + C_L)$$

$$f_{HM} = \frac{1}{2\pi \tau_M} = \frac{1}{2\pi (R_C \parallel R_L) (C_M + C_L)} \quad *$$

$$\begin{aligned} (b) \quad V_o &= -g_m (R_C \parallel R_L) \cdot v_{\pi 2} \\ &= -g_m (R_C \parallel R_L) \cdot \frac{g_{m1} r_{\pi 2}}{\beta} v_{\pi 1} \\ &= -g_m (R_C \parallel R_L) \cdot \frac{r_{\pi 2}}{\beta (R_2 \parallel R_3 \parallel r_{\pi 1} + R_S)} V_i \end{aligned}$$

AV

$$\begin{aligned} K_T &= 120 \times \frac{0.026}{1.02} \\ &= 3 \text{ K} \end{aligned}$$

(c) ①  $C_L \rightarrow 0$

$$\begin{aligned} f_{HX} &= \frac{10^9}{2\pi \cdot (0.1 \parallel 20.5 \parallel 28.3 \parallel 3) \cdot (12 + 4)} \\ &= \frac{10^9}{2 \times 3.14 \times 0.096 \times 16} = 103.67 \text{ MHz} \end{aligned}$$

$$f_{HM} = \frac{10^9}{2\pi \times (51100) \times 2} = \frac{10^9}{2 \times 3.14 \times 3.33 \times 2} = 23.9 \text{ MHz (dominant)}$$

②  $C_L = 15 \text{ pF}$

$$f_{HM} = \frac{10^9}{2\pi \times 3.33 \times 17} = 2.8 \text{ MHz (dominant)}$$