
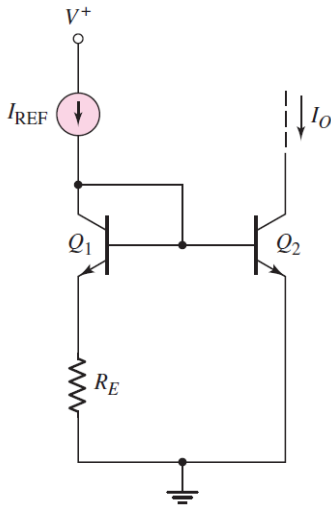


**Electronics II, EXAM-3, Spring 2018**  
 Department of Communication Engineering, National Central University  
 May 25, 2018, Prof. Dah-Chung Chang (E1-311)



**Exam Time: 10:00AM-12:30PM, 2018/5/25**

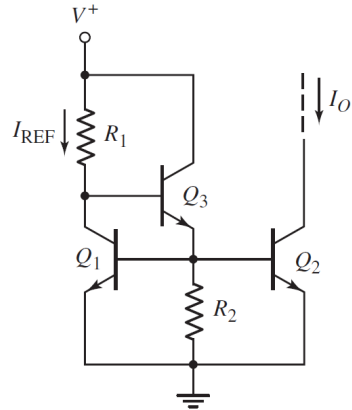1. (30%) The transistor parameters are  $\beta = 80, V_{BE}(\text{on}) = 0.7\text{ V}$  and  $V_A = \infty$ .
- Derive the expression for  $I_O$  in terms of  $I_{REF}, \beta, V_{BE}(\text{on}),$  and  $R_2$ .
  - For  $R_2 = 10\text{ k}\Omega$  and  $V^+ = 10\text{ V}$ , find  $R_1$  such that  $I_O = 0.7\text{ mA}$ .





2. (20%) Neglect base currents and assume  $V_A = \infty$ ,  $I_{REF} = 100\mu\text{ A}$ , and  $R_E = 700\Omega$ . For transistor parameters (reverse saturation currents from collector to emitter) of  $I_{S1} = I_{S2} = 5 \times 10^{-15}\text{ A}$ , find  $I_O$ .

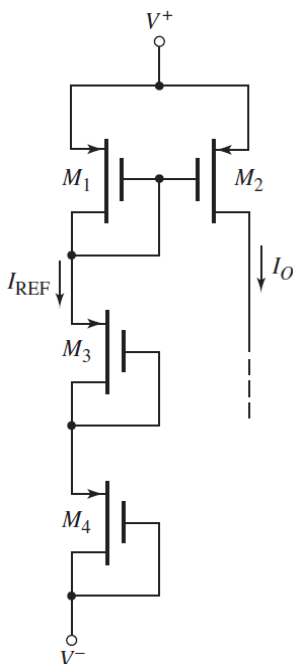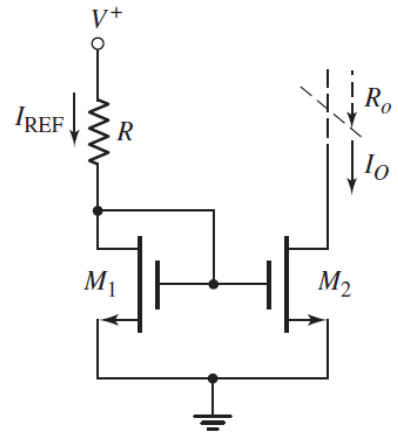3. (20%) Consider the circuit with  $V^+ = +2.5\text{ V}$  and  $R = 15\text{ k}\Omega$ . The transistor parameters are identical, with parameters  $V_{TN} = 0.5\text{ V}, k'_n = 80\mu\text{ A/V}^2, W/L = 6,$  and  $\lambda = 0$ . Determine  $I_O$ .



4. (25%) Consider the circuit with  $V^+ = +5\text{ V}$  and  $V^- = -5\text{ V}$ . The transistor parameters are  $V_{TP} = -1.2\text{ V}, k'_p = 80\mu\text{ A/V}^2,$   $(W/L)_1 = (W/L)_2 = 25,$   $(W/L)_3 = (W/L)_4 = 4,$  and  $\lambda = 0$ . Determine  $I_O$ .

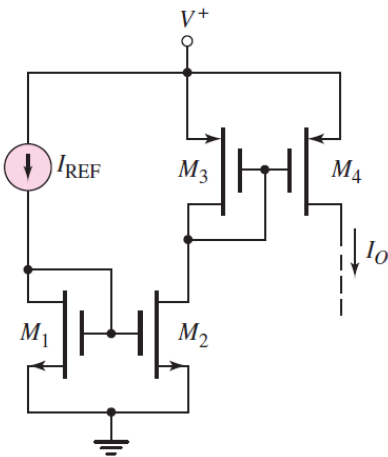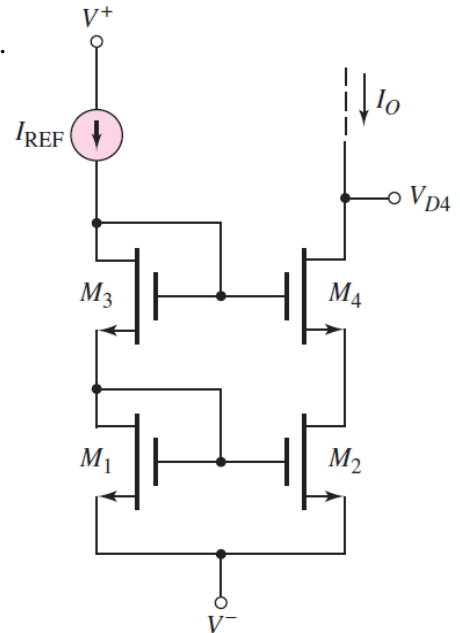5. (20%) Consider the circuit with  $V^+ = +5V$  and  $V^- = -5V$ . All transistors are identical, with parameters  $V_{TN} = 1V$ ,  $K_n = 80\mu A/V^2$ , and  $\lambda = 0.02V^{-1}$ . Let  $I_{REF} = 20\mu A$ , determine the output resistance  $R_o$  looking into the drain of  $M_4$ .



6. (20%) Transistor parameters are  $V_{TN} = 0.4V$ ,  $k'_n = 100\mu A/V^2$ ,  $V_{TP} = -0.6V$ ,  $k'_p = 40\mu A/V^2$ , and  $\lambda_n = \lambda_p = 0$ . The width-to-length ratios are  $(W/L)_1 = 15$ ,  $(W/L)_2 = (W/L)_3 = 9$ , and  $(W/L)_4 = 20$ . Let  $I_{REF} = 200\mu A$ , determine
- $I_o$ , and
  - the minimum  $V_{SD4}$  such that  $M_4$  is biased in the forward active mode.

7. (15%) Transistor parameters are  $V_{TN} = 1V$ ,  $K_n = 1mA/V^2$ , and  $\lambda_n = \lambda_p = 0.01V^{-1}$ . Assume  $M_1$  and  $M_2$  are matched and  $I_{REF} = 0.5mA$ . Find the small-signal voltage gain for the load resistance of  $R_L = 100k\Omega$ .

