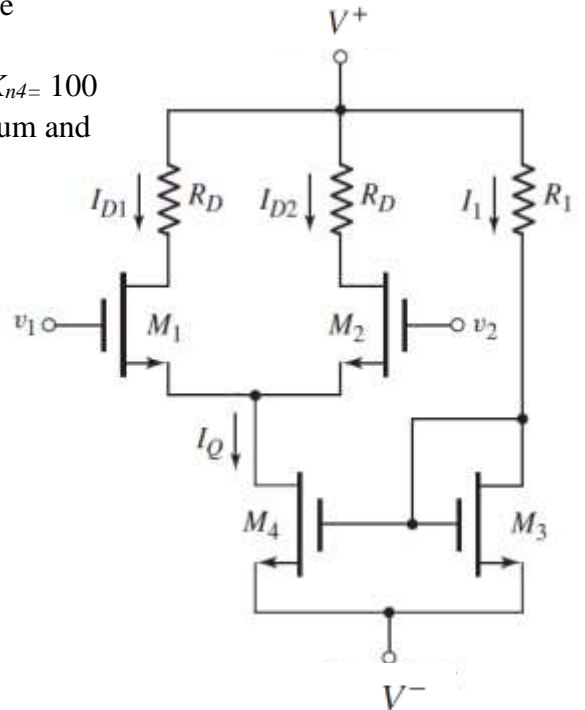



Electronics II, Exam-4, Spring 2018
 Department of Communication Engineering, National Central University
 June 15, 2018, Prof. Dah-Chung Chang (E1-311)

Note: Exam time is 10:00AM-12:00PM, 2018/6/15. The total is 120 points.


1. (20 pts) For the differential amplifier, the parameters are $V^+ = 5V$, $V^- = -5V$, $R_1 = 80\text{ k}\Omega$ and $R_D = 40\text{ k}\Omega$. The transistor parameters are: $K_{n1} = K_{n2} = 50\ \mu\text{ A/V}^2$, $K_{n3} = K_{n4} = 100\ \mu\text{ A/V}^2$, $\lambda = 0$, and $V_{TN} = 0.8\text{ V}$. Determine the maximum and minimum values of the common-mode input voltage?



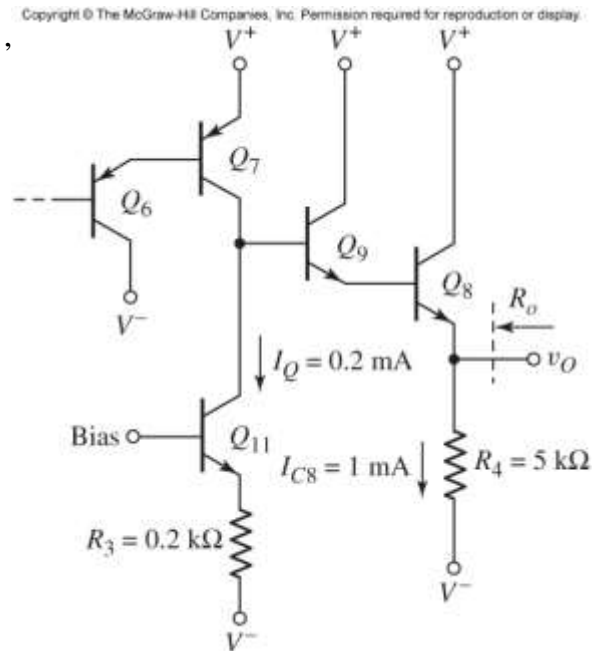2. (30 pts) Assume $\beta = 120$ for all npn transistors and $\beta = 90$ for all pnp transistors. Let $V_{A7} = 60V$ for Q_7 , $V_{A11} = 120V$ for Q_{11} , and $V_A = \infty$ for all other transistors. Determine the output resistance R_o .



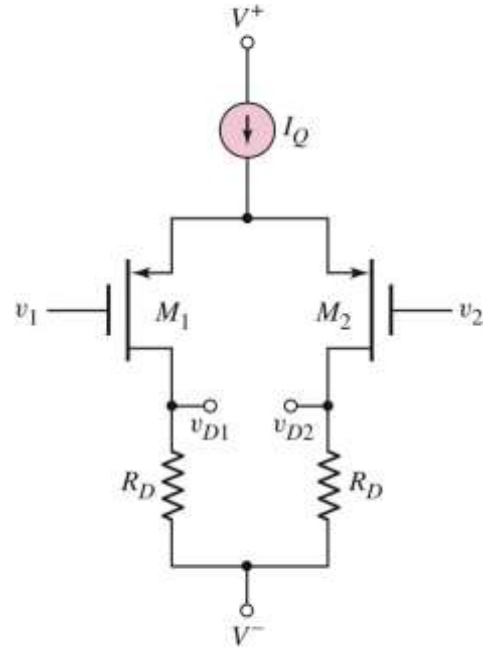3. (30 pts) The circuit and transistor parameters are $V^+ = 3V, V^- = -3V, R_D = 360k\Omega, I_Q = 12\mu A,$
 $V_{TP} = -0.4V, K_p = 30\mu A/V^2,$ and $\lambda = 0.$ The output resistance of the current source is $R_o = 4M\Omega.$ (a) Determine V_{SD} of the transistors for $v_1 = v_2 = 0$ (b) Determine the differential-mode and common-mode voltage gains for $v_o = v_{D2}.$



4. (40 pts) Given that $V_{BE(on)} = 0.7V, \beta = 150, V_A = \infty,$ and $R_2 = R_3.$ If $I_Q = 0.4mA,$ determine
 (a) R_2 (10 pts)
 (b) $I_{R4}, I_{R6},$ and I_{R7} (10 pts)
 (c) R_{i2} and R_{i3} (10 pts)
 (d) $A_{d1} = v_{O2}/(v_1 - v_2)$ and $A_2 = v_{O3}/v_{O2}.$ (10 pts)

