

#1

dc analysis

$$I_D = \frac{V^+ - V_{SG}}{R_S} = K_P (V_{SG} + V_{TP})^2$$

$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2$$

$$= 4(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(4)(2.44)}}{2(4)} = 1.707$$

$$g_m = 2K_P (V_{SG} + V_{TP}) = 2(1)(1.707 - 0.8)$$

$$g_m = 1.81 \text{ mA/V}$$

$$f_A = \frac{1}{2\pi R_{eq} \cdot C_{gsT}}$$

$$R_{eq} = \frac{1}{1.81} \parallel 4 \parallel 0.5 = 0.246 \text{ k}\Omega$$


$$f_A = \frac{1}{2\pi(246)(4 \times 10^{-12})} = 162 \text{ MHz}$$

3-dB frequency due to  $C_{gdT}$

$$f_B = \frac{1}{2\pi(R_D \parallel R_L)C_{gdT}}$$


$$= \frac{1}{2\pi(2 \parallel 4) \times 10^3 \times 10^{-12}}$$

$$f = 119 \text{ MHz}$$

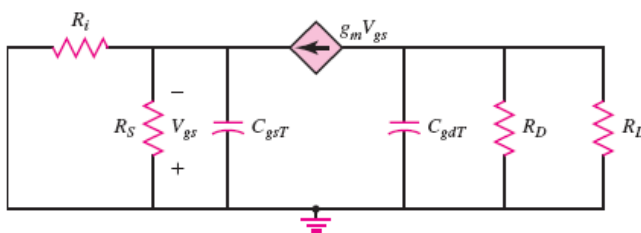

3-dB frequency due to  $C_{gsT}$ :  $R_{eq} = \frac{1}{g_m} \parallel R_S \parallel R_i$

Midband gain

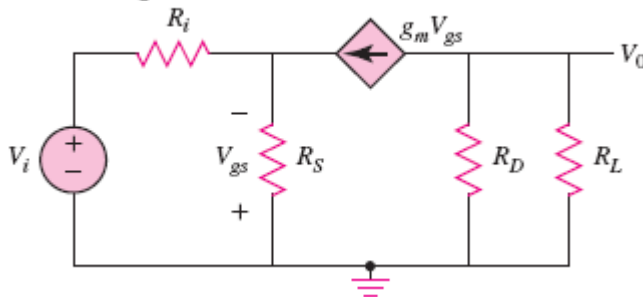

$$V_{gs} = \frac{-\frac{1}{g_m} \parallel R_S}{\frac{1}{g_m} \parallel R_S + R_i} \cdot V_i = \frac{-\frac{1}{1.81} \parallel 4}{\frac{1}{1.81} \parallel 4 + 0.5} \cdot V_i$$

$$= -0.492V_i$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$A_v = (0.492)(1.81)(4 \parallel 2) \Rightarrow \underline{A_v = 1.19}$$

#2

**Solution (DC Analysis):** We find, for each stage,

$$R_{TH} = R_1 \parallel R_2 = 55 \parallel 31 = 19.83 \text{ k}\Omega$$

and

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{31}{31 + 55} \right) (5) = 1.802 \text{ V}$$

Now

$$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_E} = \frac{1.802 - 0.7}{19.83 + (201)(1)} \Rightarrow 4.99 \mu\text{A}$$

so that

$$I_{CQ} = 0.998 \text{ mA}$$

**Solution (AC Analysis):** The small-signal diffusion resistance is

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(200)(0.026)}{0.988} = 5.21 \text{ k}\Omega$$


The input resistance looking into each base terminal is

$$R_i = r_\pi + (1 + \beta)R_E = 5.21 + (201)(1) = 206.2 \text{ k}\Omega$$

**Solution (AC Design):** The small-signal equivalent circuit is shown in Figure 7.74.

The time constant of the first stage is

$$\tau_A = (R_1 \parallel R_2 \parallel R_i)C_{C1}$$

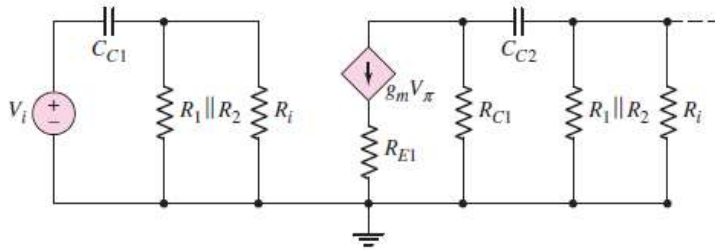

**Figure 7.74** Small-signal equivalent circuit of two-stage BJT amplifier with coupling capacitors for design application

and the time constant of the second stage is

$$\tau_B = (R_{C1} + R_1 \parallel R_2 \parallel R_i)C_{C2}$$

If the 3 dB frequency of each stage is to be 20 Hz, then

$$\tau_A = \tau_B = \frac{1}{2\pi f_{3\text{-dB}}} = \frac{1}{2\pi(20)} = 7.958 \times 10^{-3} \text{ s}$$

The coupling capacitor of the first stage must be

$$C_{C1} = \frac{\tau_A}{R_1 \parallel R_2 \parallel R_i} = \frac{7.958 \times 10^{-3}}{(55 \parallel 31 \parallel 206.2) \times 10^3} \Rightarrow 0.44 \mu\text{F}$$

and the coupling capacitor of the second stage must be

$$C_{C2} = \frac{\tau_B}{R_{C1} + R_1 \parallel R_2 \parallel R_i} = \frac{7.958 \times 10^{-3}}{(2.5 + 55 \parallel 31 \parallel 206.2) \times 10^3} \Rightarrow 0.386 \mu\text{F}$$

#3

$$V_{B1} = \left( \frac{R_3}{R_1 + R_2 + R_3} \right) (12) = \left( \frac{7.92}{58.8 + 33.3 + 7.92} \right) (12) = 0.9502 \text{ V}$$

Neglecting base currents

$$I_C = \frac{0.9502 - 0.7}{0.5} = 0.50 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ K}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

From Eq (7.119(a)),

$$\tau_{p\pi} = (R_S \parallel R_{B1} \parallel r_\pi) (C_{\pi1} + C_{M1})$$

$$R_{B1} = R_2 \parallel R_3 = 33.3 \parallel 7.92 = 6.398 \text{ k}\Omega$$

$$C_{M1} = 2C_{\mu1} = 6 \text{ pF}$$

Then

$$\tau_{p\pi} = (1 \parallel 6.398 \parallel 5.2) \times 10^3 \times (24 + 6) \times 10^{-12} \Rightarrow \tau_{p\pi} = 22.24 \text{ ns}$$

$$f_{H\pi} = \frac{1}{2\pi\tau_{p\pi}} = \frac{1}{2\pi(22.24 \times 10^{-9})} \Rightarrow f_{H\pi} = 7.15 \text{ MHz}$$

From Eq (7.120(a)),

$$\tau_{p\mu} = (R_C \parallel R_L) C_{\mu2} = (7.5 \parallel 2) \times 10^3 \times 3 \times 10^{-12} \Rightarrow \tau_{p\mu} = 4.737 \text{ ns}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{p\mu}} = \frac{1}{2\pi(4.737 \times 10^{-9})} \Rightarrow f_{H\mu} = 33.6 \text{ MHz}$$

From Eq. (7.125),

$$|A_v|_M = g_{m2} (R_C \parallel R_L) \left[ \frac{R_{B1} \parallel r_{\pi1}}{R_{B1} \parallel r_{\pi1} + R_S} \right] = (19.23)(7.5 \parallel 2) \left[ \frac{6.40 \parallel 5.2}{6.40 \parallel 5.2 + 1} \right]$$

$$|A_v|_M = 22.5$$