

#1

$$I_1 = \frac{10 - V_{GS4}}{R_1} = K_{n3} (V_{GS4} - V_{TN})^2$$

$$10 - V_{GS4} = (0.1)(80)(V_{GS4} - 0.8)^2$$

$$10 - V_{GS4} = 8(V_{GS4}^2 - 1.6V_{GS4} + 0.64)$$

$$8V_{GS4}^2 - 11.8V_{GS4} - 4.88 = 0$$

$$V_{GS4} = \frac{11.8 \pm \sqrt{(11.8)^2 + 4(8)(4.88)}}{2(8)} = 1.81 \text{ V}$$

$$I_1 = I_Q = \frac{10 - 1.81}{80} = 0.102 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{0.102}{2} = 0.0512 \text{ mA}$$

$$= K_{n1} (V_{GS1} - V_{TN})^2$$

$$0.0512 = 0.050(V_{GS1} - 0.8)^2 \Rightarrow V_{GS1} = 1.81 \text{ V}$$

$$v_{01} = v_{02} = 5 - (0.0512)(40) = 2.95 \text{ V}$$

$$\begin{aligned} \text{Max } v_{cm} : V_{DS1}(\text{sat}) &= V_{GS1} - V_{TN} \\ &= 1.81 - 0.8 = 1.01 \text{ V} \end{aligned}$$

$$\begin{aligned} v_{cm}(\text{max}) &= v_{01} - V_{DS1}(\text{sat}) + V_{GS1} \\ &= 2.95 - 1.01 + 1.81 \end{aligned}$$

$$v_{cm}(\text{max}) = 3.75 \text{ V}$$

$$\begin{aligned} \text{Min } v_{cm} : V_{DS4}(\text{sat}) &= V_{GS4} - V_{TN} \\ &= 1.81 - 0.8 = 1.01 \text{ V} \end{aligned}$$

$$\begin{aligned} v_{cm}(\text{min}) &= V_{GS1} + V_{DS4}(\text{sat}) - 5 \\ &= 1.81 + 1.01 - 5 \end{aligned}$$

$$v_{cm}(\text{min}) = -2.18 \text{ V}$$

$$-2.18 \leq v_{cm} \leq 3.75 \text{ V}$$

#2

$$r_{\pi 11} = \frac{(120)(0.026)}{0.2} = 15.6 \text{ k}\Omega$$

$$R'_E = R_3 \parallel r_{\pi 11} = 0.2 \parallel 15.6 = 0.1975 \text{ k}\Omega$$

$$g_{m11} = \frac{0.2}{0.026} = 7.692 \text{ mA/V}$$

$$r_{o11} = \frac{V_{A11}}{I_{C11}} = \frac{120}{0.2} = 600 \text{ k}\Omega$$

$$R_{C11} = r_{o11} (1 + g_{m11} R'_E) = 600 [1 + (7.692)(0.1975)] = 1512 \text{ k}\Omega$$

$$R_{C7} = r_{o7} = \frac{V_{A7}}{I_{C7}} = \frac{60}{0.2} = 300 \text{ k}\Omega$$

$$Z = R_{C7} \parallel R_{C11} = 300 \parallel 1512 = 250 \text{ k}\Omega$$

$$r_{\pi 8} = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$I_{C9} = \frac{1}{120} \left( \frac{120}{121} \right) = 0.008264 \text{ mA}$$

$$r_{\pi 9} = \frac{(120)(0.026)}{0.008264} = 377.5 \text{ k}\Omega$$

$$\text{Now } R_o = R_4 \parallel \left( \frac{r_{\pi 8} + \left( \frac{r_{\pi 9} + Z}{121} \right)}{121} \right) = 5 \parallel \left( \frac{3.12 + \left( \frac{377.5 + 250}{121} \right)}{121} \right) = 5 \parallel 0.06864$$

$$\text{Or } R_o = 67.7 \Omega$$

#3

(a)

$$v_1 = v_2 = 0$$

$$I_D = K_n (V_{SG} + V_{TP})^2$$

$$I_D = 6 \mu\text{A}$$

$$\sqrt{\frac{6}{30}} + 0.4 = V_{SG}$$

$$V_{SG} = 0.847 \text{ V}$$

$$V_S = +0.847 \text{ V}$$

$$v_D = I_D R_D - 3$$

$$= (6)(0.36) - 3 = -0.84 \text{ V}$$

$$V_{SD} = V_S - v_D = 0.847 - (-0.84)$$

$$v_{SD} = 1.69 \text{ V}$$

(b)

$$A_d = \frac{g_m R_D}{2} = \frac{(26.83)(0.36)}{2} \Rightarrow A_d = 4.83$$

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_O} = \frac{-(26.83)(0.36)}{1 + 2(26.83)(4)} = -0.0448$$

#4

See Texbook Example 11.15 and Example 11.16, but  $\beta = 150$  not 100 in here.

(a)

$$I_1 = \frac{10 - 0.7 - (-10)}{19.3} = 1 \text{ mA}$$

The bias current  $I_Q$  is determined from

$$I_Q R_2 = V_T \ln\left(\frac{I_1}{I_Q}\right)$$

$$R_2 = R_3 = 59.6 \Omega$$

(b) Neglecting base currents,

The collector currents are then

$$I_{C1} = I_{C2} = 0.2 \text{ mA}$$

The dc voltage at the collector of  $Q_2$  is

$$V_{O2} = 10 - I_{C2} R_C = 10 - (0.2)(20) = 6 \text{ V}$$

$$I_{R4} = \frac{V_{O2} - 2V_{BE(\text{on})}}{R_4} = \frac{6 - 1.4}{11.5} = 0.4 \text{ mA}$$

$$I_{R6} = I_Q = 0.4 \text{ mA}$$

$$V_{O3} = 10 - I_{R5} R_5 = 10 - (0.4)(5) = 8 \text{ V}$$

$$V_{B6} = V_{O3} - V_{BE(\text{on})} - I_{R6} R_6 = 8 - 0.7 - (0.4)(16.5) = 0.7 \text{ V}$$

$$I_{R7} = \frac{v_o - (-10)}{R_7} = \frac{10}{5} = 2 \text{ mA}$$

(c)

$$R_{i2} = r_{\pi 3} + (1 + \beta) r_{\pi 4}$$

$$r_{\pi 4} = \beta \frac{V_T}{I_{R4}} = 150 \times \frac{0.026}{0.4} = 9.75 \text{ (k}\Omega\text{)}$$

$$r_{\pi 3} = \beta \frac{V_T}{I_{R4}} = (150)^2 \times \frac{0.026}{0.4} = 1462.5 \text{ (k}\Omega\text{)}$$

$$R_{i2} = 1462.5 + 151 \times 9.75 = 2934.75 \text{ (k}\Omega\text{)}$$

$$R_{i3} = r_{\pi 5} + (1 + \beta) [R_6 + r_{\pi 6} + (1 + \beta) R_7]$$

$$r_{\pi 5} = \beta \frac{V_T}{I_{R6}} = 150 \times \frac{0.026}{0.4} = 9.75 \text{ (k}\Omega\text{)}$$

$$r_{\pi 6} = \beta \frac{V_T}{I_{R7}} = 150 \times \frac{0.026}{2} = 1.95 \text{ (k}\Omega\text{)}$$


$$R_{i3} = 9.75 + 151 \times (16.5 + 1.95 + 151 \times 5) = 116.8 \text{ M}\Omega$$

(d)

$$A_{d1} = \frac{g_m}{2} (R_c \parallel R_{i2})$$

$$g_m = \frac{I_Q}{2V_T} = \frac{0.4}{2 \times 0.026} = 7.7 \text{ (mA/V)}$$
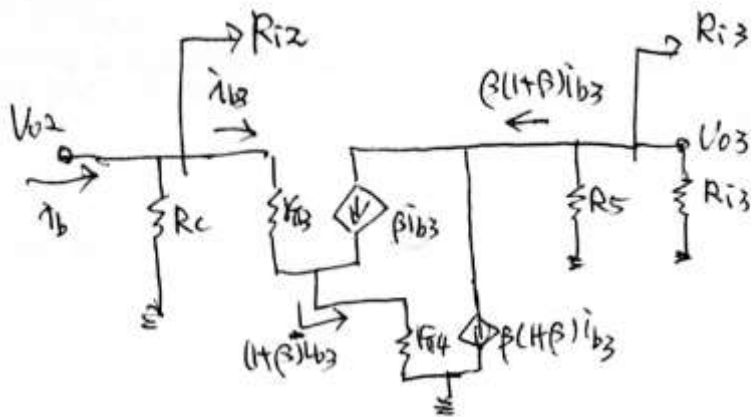
$$A_{d1} = \frac{7.7}{2} \times (20 \parallel 2934.75) = 16.5$$



$$V_{02} = i_{b3} \cdot (R_{i3} + (1+\beta)R_{e4}) = i_{b3} \cdot R_{i2}$$

$$V_{03} = \beta(1+\beta)i_{b3} \cdot (R_5 \parallel R_{i3}) \approx \beta(1+\beta)i_{b3} \cdot R_5$$

$$A_2 = \frac{V_{03}}{V_{02}} = \frac{\beta(1+\beta)R_5}{R_{i2}} = \frac{150 \times 151 \times 5}{2934.75} = 38.6$$