

1.


$$A_v = \frac{-g_m^2}{\frac{1}{r_{o3}r_{o4}} + \frac{1}{r_{o1}r_{o2}}}$$

$$g_m = 2\sqrt{\left(\frac{0.1}{2}\right)(25)(0.08)} = 0.6325 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.04)(0.08)} = 312.5 \text{ k}\Omega$$

$$A_v = \frac{-(0.6325)^2}{\frac{1}{(312.5)^2} + \frac{1}{(312.5)^2}} = \frac{-0.40}{2(0.00001024)} = -19,531$$

2.

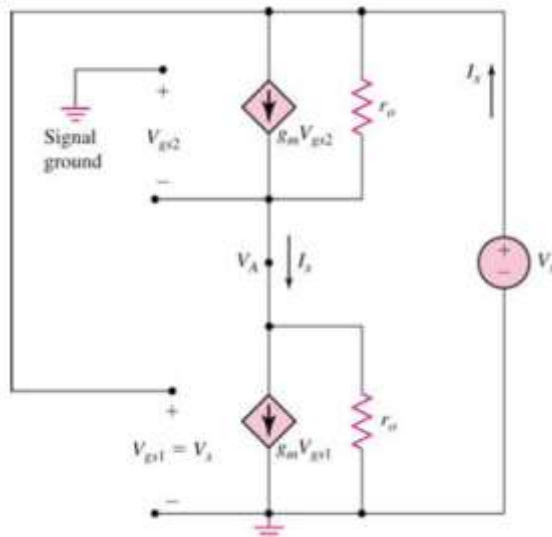

$$(1) \quad I_x = \frac{V_x - V_A}{r_o} + g_m V_{gs2}$$

$$I_x = \frac{V_A}{r_o} + g_m V_{gs1}$$

$$(2) \quad V_{gs1} = V_x, \quad V_{gs2} = -V_A$$

So

$$(1) \quad I_x = \frac{V_x}{r_o} - V_A \left(\frac{1}{r_o} + g_m \right)$$

$$(2) \quad I_x = \frac{V_A}{r_o} + g_m V_x \Rightarrow V_A = r_o [I_x - g_m V_x]$$

Then

$$I_x = \frac{V_x}{r_o} - r_o (I_x - g_m V_x) \left(\frac{1}{r_o} + g_m \right)$$

$$I_x = \frac{V_x}{r_o} - r_o \left[\frac{I_x}{r_o} + g_m I_x - \frac{g_m}{r_o} V_x - g_m^2 V_x \right]$$

$$I_x = \frac{V_x}{r_o} - I_x - g_m r_o I_x + g_m V_x + g_m^2 r_o V_x$$

$$I_x [2 + g_m r_o] = V_x \left[\frac{1}{r_o} + g_m + g_m^2 r_o \right]$$


Since $g_m \gg \frac{1}{r_o}$

$$I_x [2 + g_m r_o] \cong V_x (g_m) (1 + g_m r_o)$$

Then $\frac{V_x}{I_x} = R_o = \frac{2 + g_m r_o}{g_m (1 + g_m r_o)}$

Usually, $g_m r_o \gg 2$, so that $R_o \cong \frac{1}{g_m}$

3.

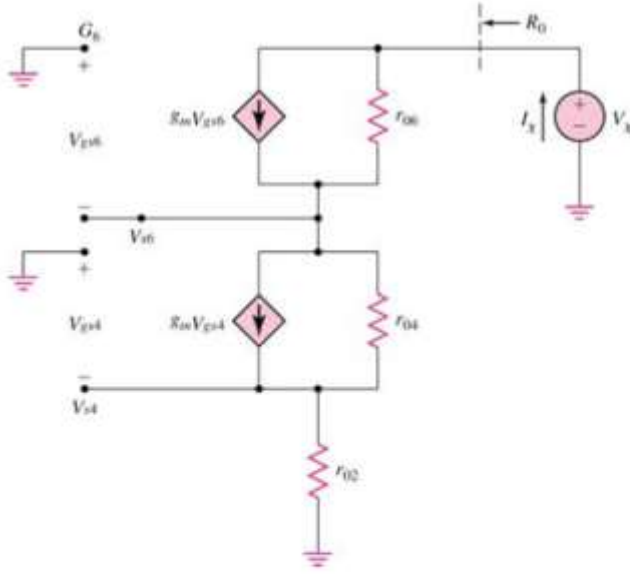

$$V_{gs4} = -I_X r_{02}$$

$$V_{S6} = (I_X - g_m V_{gs4}) r_{04} + I_X r_{02}$$

$$= (I_X + g_m I_X r_{02}) r_{04} + I_X r_{02}$$

$$V_{S6} = I_X [r_{02} + (1 + g_m r_{02}) r_{04}] = -V_{gs6}$$

$$I_X = g_m V_{gs6} + \frac{V_X - V_{S6}}{r_{06}} = \frac{V_X}{r_{06}} - V_{S6} \left(g_m + \frac{1}{r_{06}} \right)$$

$$I_X = \frac{V_X}{r_{06}} - I_X \left(g_m + \frac{1}{r_{06}} \right) [r_{02} + (1 + g_m r_{02}) r_{04}]$$

$$I_X \left\{ 1 + \left(g_m + \frac{1}{r_{06}} \right) [r_{02} + (1 + g_m r_{02}) r_{04}] \right\} = \frac{V_X}{r_{06}}$$

$$\frac{V_X}{I_X} = R_0 = r_{06} + (1 + g_m r_{06}) [r_{02} + (1 + g_m r_{02}) r_{04}]$$

$$I_0 \approx I_{REF} = 0.2 \text{ mA} = 0.2 (V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.2)(2 - 1) = 0.4 \text{ mA/V}$$

$$r_{02} = r_{04} = r_{06} = \frac{1}{\lambda I_0} = \frac{1}{(0.02)(0.2)} = 250 \text{ k}\Omega$$

$$R_0 = 250 + [1 + (0.4)(250)] \times \{ 250 + [1 + (0.4)(250)](250) \}$$

$$R_0 = 2575750 \text{ k}\Omega \Rightarrow \underline{R_0 = 2.58 \times 10^9 \Omega}$$

4.

$$I_{D2} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \cdot I_{REF} = \frac{9}{15}(200) \Rightarrow \underline{I_{D2} = 120 \mu\text{A}}$$

$$I_O = \frac{\left(\frac{W}{L}\right)_4}{\left(\frac{W}{L}\right)_3} \cdot I_{D2} = \left(\frac{20}{9}\right)(120) \Rightarrow \underline{I_O = 267 \mu\text{A}}$$

$$I_O = 266.7 = \left(\frac{40}{2}\right)(20)(V_{SG4} - 0.6)^2$$

$$V_{SG4} = 1.416 \text{ V}$$

$$V_{SD4}(\text{sat}) = 1.416 - 0.6 \Rightarrow \underline{V_{SD4}(\text{sat}) = 0.816 \text{ V}}$$
