## Note: Exam time is 10:00AM-12:10PM, 2019/6/14.

- 1. (**25 pts**) You have to draw the small-signal models (with corresponding transistor numbers) to explain how you derive the following answers:
  - (a) Find the common-mode input resistance of  $v_1$  and  $v_2$ . (5 pts)
  - (b) Find the relationship of  $v_{02}$  and  $(v_1 v_2)$ . (10 pts)
  - (c) Find the output resistance  $R_o$ . (10 pts)



2. (25 pts) Assume  $\beta = 100$  for all transistors and  $V_A = 100V$  for Q7 and Q11, and  $V_A = \infty$  for all other transisitors. Determine the output resistance  $R_o$ .



1

3. (25 pts) Assume that the parameters of the transistors are  $K_n = 0.2mA/V^2$ ,  $V_{TN} = 2V$ , and  $\lambda = 0.02V^{-1}$ . Determine the differential-mode voltage gain  $A_d = v_{O3} / v_d$ , where  $v_d = v_1 - v_2$ .



- 4. (25 pts) Consider the multistage bipolar circuit in which dc base currents are negligible. Assume the transistor parameters are  $\beta = 120$ ,  $V_{BE}(\text{on}) = 0.7$  V, and  $V_A = \infty$ .
  - (a) For  $v_1 = v_2 = -1.5$  V, find R,  $R_{E1}$ ,  $R_C$ , and  $R_{E2}$  such that  $v_{O2} = v_O = 0$ ,  $Ic_{O3} = 0.25$  mA, and  $Ic_{O4} = 2$  mA. (10 pts)
  - (b) Assuming *CE* acts as a short circuit, determine the differential-mode voltage gain  $A_d = v_0 / v_d$ , where  $v_d = v_1 - v_2$ . (15 pts)

