
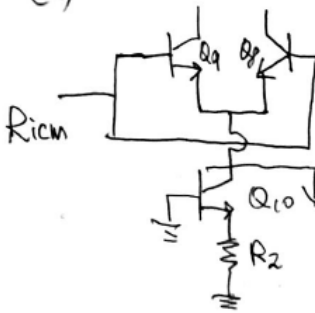


#1

(a)

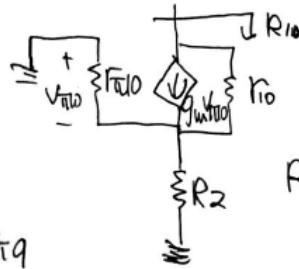

$$r_{\pi 8} = r_{\pi 9}$$



$$R_0 = (r_{\pi 10} \parallel R_2) + r_{o10} (1 + g_{m10} (r_{\pi 10} \parallel R_2))$$


$$\approx g_{m10} r_{o10} (r_{\pi 10} \parallel R_2)$$

$$2R_{icm} = r_{\pi 9} + (1 + \beta_9) \cdot 2R_0$$

$$R_{icm} \approx (1 + \beta_9) R_0$$


$$= (1 + \beta_9) \cdot g_{m10} \cdot r_{o10} (r_{\pi 10} \parallel R_2)$$

(b)

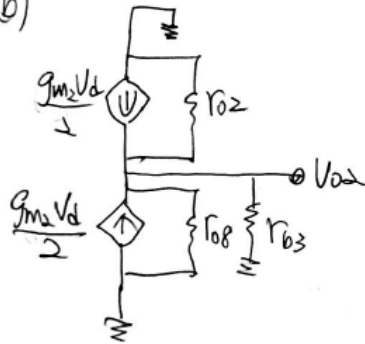

$$V_d = V_1 - V_2, \quad g_{m2} = g_{m8}$$

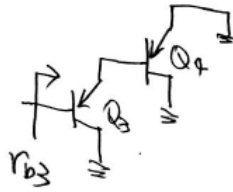
$$V_{o2} = g_{m2} \cdot V_d (r_{o2} \parallel r_{o8} \parallel r_{b3})$$



$$r_{b3} = r_{\pi 3} + (1 + \beta_3) r_{\pi 4}$$


$$= r_{\pi 3} + (1 + g_{m3} r_{\pi 3}) r_{\pi 4}$$
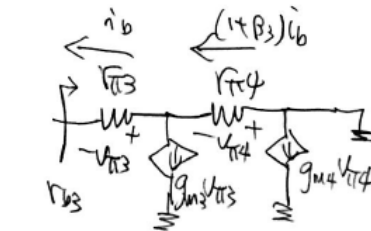
$$\frac{V_{o2}}{V_d} = g_{m2} [r_{o2} \parallel r_{o8} \parallel (r_{\pi 3} + (1 + g_{m3} r_{\pi 3}) r_{\pi 4})]$$



$$g_{m3} r_{b3} = \beta_3$$

(c)

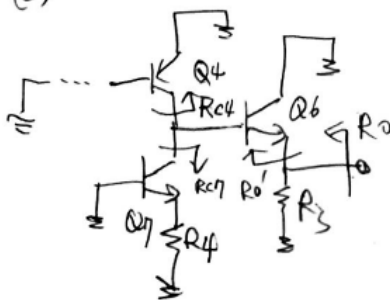

$$R_{o4} = r_{o4}$$

$$R_{c7} = (r_{\pi 7} \parallel R_4) + r_{o7} (1 + g_{m7} (r_{\pi 7} \parallel R_4))$$

$$\approx g_{m7} \cdot r_{o7} (r_{\pi 7} \parallel R_4)$$

$$R_0' = \frac{r_{\pi 6} + R_{c7} \parallel R_{c4}}{1 + \beta_6}$$

$$R_0 = R_3 \parallel R_0' = R_3 \parallel \frac{r_{\pi 6} + R_{c4} \parallel g_{m7} r_{o7} (r_{\pi 7} \parallel R_4)}{1 + g_{m6} r_{\pi 6}}$$

$$g_{m6} r_{\pi 6} = \beta_6$$

#2

$$R_o = R_A \parallel \left[\frac{r_{\pi 8} + \frac{r_{\pi 9} + r_{07} \parallel R_{011}}{1 + \beta}}{1 + \beta} \right]$$

$$r_{\pi 8} = \frac{\beta V_T}{I_{C8}} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$I_{C8} \approx \frac{I_{C9}}{\beta} = \frac{1}{100} = 0.01 \text{ mA}$$

$$r_{\pi 9} = \frac{(100)(0.026)}{0.01} = 260 \text{ k}\Omega$$

$$r_{07} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$r_{011} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$R_{011} = r_{011} [1 + g_m R'_E], \quad g_m = \frac{0.2}{0.026} = 7.69$$

$$r_{\pi 11} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$R'_E = 0.2 \parallel 13 = 0.197 \text{ k}\Omega$$

$$R_{011} = 500 [1 + (7.69)(0.197)] = 1257 \text{ k}\Omega$$

Then

$$R_o = 5 \parallel \left[\frac{2.6 + \frac{260 + 500 \parallel 1257}{101}}{101} \right]$$

$$= 5 \parallel 0.086$$

$$\Rightarrow \underline{R_o = 0.085 \text{ k}\Omega}$$

#3

$$I_1 = \frac{24 - V_{GS4}}{R_1} = k_n (V_{GS4} - V_{Th})^2$$

$$24 - V_{GS4} = (55)(0.2)(V_{GS4} - 2)^2$$

$$24 - V_{GS4} = 11(V_{GS4}^2 - 4V_{GS4} + 4)$$

$$11V_{GS4}^2 - 43V_{GS4} + 20 = 0$$

$$V_{GS4} = \frac{43 \pm \sqrt{(43)^2 - 4(11)(20)}}{2(11)} = 3.37 \text{ V}$$

$$I_1 = \frac{24 - 3.37}{55} = 0.375 \text{ mA} = I_Q$$

$$v_{o2} = 12 - \left(\frac{0.375}{2} \right) (40) = 4.5 \text{ V}$$

$$\frac{v_{o2} - V_{GS3}}{R_5} = I_{D3} = k_n (V_{GS3} - V_{Th})^2$$

$$4.5 - V_{GS3} = (0.2)(6)(V_{GS3}^2 - 4V_{GS3} + 4)$$

$$1.2V_{GS3}^2 - 3.8V_{GS3} + 0.3 = 0$$

$$V_{GS3} = \frac{3.8 \pm \sqrt{(3.8)^2 - 4(1.2)(0.3)}}{2(1.2)} = 3.09 \text{ V}$$

$$I_{D3} = \frac{4.5 - 3.09}{6} = 0.235 \text{ mA}$$

$$g_{m2} = 2\sqrt{K_n I_{D2}} = 2\sqrt{(0.2)\left(\frac{0.375}{2}\right)}$$
$$= 0.387 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2} g_{m2} R_D = \frac{1}{2} (0.387)(40) \Rightarrow A_{d1} = 7.74$$

$$A_2 = \frac{-g_{m3} R_{D2}}{1 + g_{m3} R_5}$$

$$g_{m3} = 2\sqrt{K_n I_{D3}} = 2\sqrt{(0.2)(0.235)}$$
$$= 0.434 \text{ mA/V}$$

$$A_2 = \frac{-(0.434)(4)}{1 + (0.434)(6)} = -0.482$$

$$\text{So } A_d = A_{d1} \cdot A_2 = (7.74)(-0.482) \Rightarrow \underline{A_d = -3.73}$$

#4

$$(a) R = \frac{5-0}{0.25} = 20 \text{ k}\Omega$$

$$R_{E1} = \frac{-0.7 - (-5)}{0.25} = 17.2 \text{ k}\Omega$$

$$R_C = \frac{5-0.7}{0.25} = 17.2 \text{ k}\Omega$$

$$R_{E2} = \frac{0 - (-5)}{2} = 2.5 \text{ k}\Omega$$

$$(b) A_{d1} = \frac{v_{o2}}{v_d} = \frac{g_{m1}}{2} (R \parallel r_{\pi3})$$

$$g_{m1} = \frac{0.25}{0.026} = 9.615 \text{ mA/V}$$

$$r_{\pi3} = \frac{(120)(0.026)}{0.25} = 12.48 \text{ k}\Omega$$

$$A_{d1} = \frac{(9.615)}{2} (20 \parallel 12.48) = 36.94$$

$$A_3 = -g_{m3} (R_C \parallel R_{i4})$$

$$R_{i4} = r_{\pi4} + (1 + \beta)R_{E2}$$

$$g_{m3} = \frac{0.25}{0.026} = 9.615 \text{ mA/V}$$

$$r_{\pi4} = \frac{(120)(0.026)}{2} = 1.56 \text{ k}\Omega$$

$$R_{i4} = 1.56 + (121)(2.5) = 304 \text{ k}\Omega$$

$$A_3 = -(9.615)(17.2 \parallel 304) = -156.5$$

$$A_4 = \frac{(1 + \beta)R_{E2}}{r_{\pi4} + (1 + \beta)R_{E2}} = \frac{(121)(2.5)}{1.56 + (121)(2.5)} = 0.995$$

$$\text{Now } A_d = \frac{v_o}{v_d} = A_{d1} \cdot A_3 \cdot A_4 = (36.94)(-156.5)(0.995) = -5752$$