

Electronics II Exam-2 Solution 2020

2020/5/8

(1)

$$(a) T_{j,\max} - T_{amb} = P(\theta_{dev-case} + \theta_{case-amb})$$

$$150 - 25 = 30(2.8 + \theta_{case-amb}) \Rightarrow \theta_{case-amb} = 1.37^\circ C/W$$

$$(b) T_{j,\max} = 25 + 20(2.8 + 1.37) = 108^\circ C$$

(2)

(a)

$$V_{DS} \geq V_{DS}(sat) = V_{GS} - V_{TN} = V_{GS}$$

$$V_{DS} = 10 - V_o(\max) \text{ and } I_D = I_L = K_n (V_{GS})^2$$

$$\frac{V_o(\max)}{R_L} = K_n (V_{GS})^2$$

$$V_{GS} = \sqrt{\frac{V_o(\max)}{R_L \cdot K_n}}$$

$$\text{So } 10 - V_o(\max) = \sqrt{\frac{V_o(\max)}{R_L \cdot K_n}} = \sqrt{(5)(0.4)}$$

$$[10 - V_o(\max)]^2 = \frac{V_o(\max)}{2}$$

$$100 - 20V_o(\max) + V_o^2(\max) = \frac{V_o(\max)}{2}$$

$$V_o^2(\max) - 20.5V_o(\max) + 100 = 0$$

$$V_o(\max) = \frac{20.5 \pm \sqrt{(20.5)^2 - 4(100)}}{2} \Rightarrow \underline{V_o(\max) = 8 \text{ V}}$$

$$i_L = \frac{8}{5} \Rightarrow i_L = 1.6 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{i_L}{K_n}} = \sqrt{\frac{1.6}{0.4}} = 2 \text{ V} \Rightarrow \underline{V_I = 10 \text{ V}}$$

b.

$$\overline{P_L} = \frac{1}{2} \cdot \frac{(8)^2}{5} = 6.4 \text{ mW}$$

$$\overline{P_S} = \frac{20(1.6)}{\pi} = 10.2 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{6.4}{10.2} \Rightarrow \underline{\eta = 62.7\%}$$

(3)

Circuit is not in breakdown.

$$\frac{10 - 0}{R_s + R_1} = i_2 = \frac{10}{5.6 + 1} \Rightarrow \underline{i_2 = 1.52 \text{ mA}}$$

$$v_o = -i_2 R_2 = -(1.52)(1) \Rightarrow \underline{v_o = -1.52 \text{ V}}$$

$$\underline{i_z = 0}$$

(4)

$$v_{OB} = \left(1 + \frac{40}{12}\right) v_I$$

$$v_{OC} = -\frac{30}{12} v_I$$

$$v_O = v_{OB} - v_{OC}$$

$$\frac{v_O}{v_I} = \frac{3.417}{0.5} = 6.83$$

(5)

$$i_1 = i_2 \text{ and } i_2 = \frac{v_x}{R_2} + i_D, \quad v_x = -i_2 R_F$$

$$\text{Then } i_1 = -i_1 \left(\frac{R_F}{R_2}\right) + i_D$$

$$\text{Or } i_D = i_1 \left(1 + \frac{R_F}{R_2}\right)$$

(6)

$$v_{O1} = \left(\frac{\delta}{4}\right) V^+$$

$$V^+ = 7.5 \text{ V}$$

$$\frac{v_O}{v_{O1}} = \frac{R'_4}{R'_3} \left(1 + \frac{2R'_2}{R'_1}\right) = 266.7$$

$$v_O = 500\delta$$