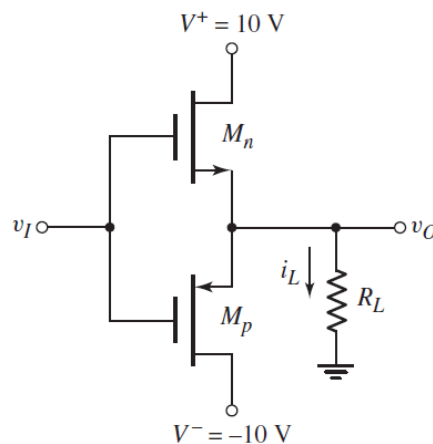



Electronics II, Exam-2, Spring 2020
 Department of Communication Engineering, National Central University
 May 8, 2020, Dr. Dah-Chung Chang (E1-311)

1. (10%) A power BJT must dissipate 30 W of power. The maximum allowed junction temperature is $T_{j,max} = 150^\circ\text{C}$, the ambient temperature is 25°C , and the device-to-case thermal resistance is $\theta_{\text{dev-case}} = 2.8^\circ\text{C/W}$.
 - (a) Find the maximum permissible thermal resistance between the case and ambient.
 - (b) Using the results of part (a), determine the junction temperature if the power dissipated in the transistor is 20 W.


2. (30%) Consider the class-B output stage with complementary MOSFETs. The transistor parameters are $V_{\text{TN}} = V_{\text{TP}} = 0$ and $K_n = K_p = 0.4 \text{ mA/V}^2$. Let $R_L = 5\text{k}\Omega$.
 - (a) Find the maximum output voltage such that M_n remains biased in the saturation region. What are the corresponding values of i_L and v_I for this condition?
 - (b) Determine the conversion efficiency for a symmetrical sine-wave output signal with the peak value found in part (a).



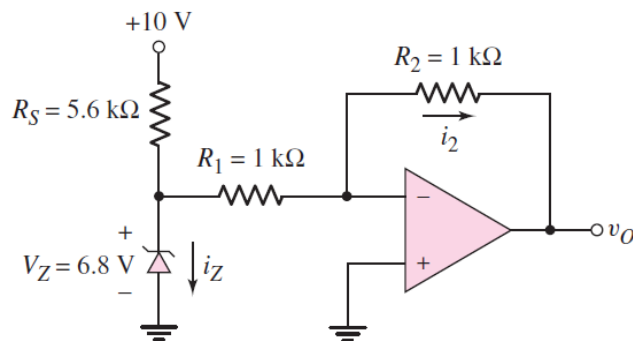
3. (15%) Assume that the breakdown voltage of the Zener diode is $V_Z = 6.8 \text{ V}$. Determine v_o , i_2 , and i_Z .



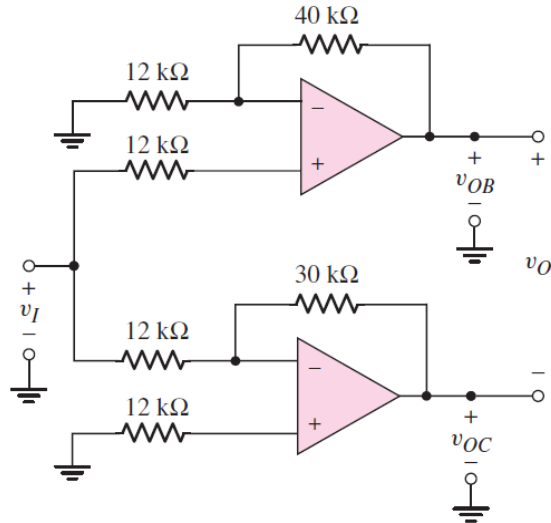4. (15%) What is the voltage gain v_O/v_I ?



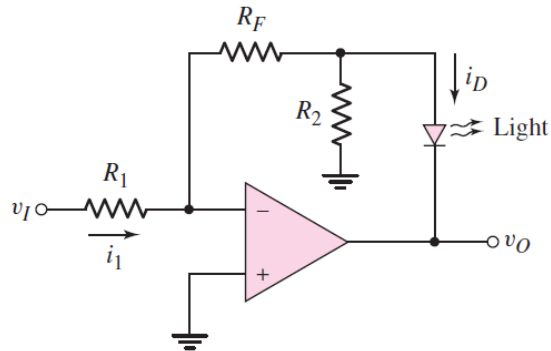5. (10%) Derive the expression for i_D in terms of i_1 and resistors.



6. (20%) Assume that the breakdown voltage of the Zener diode is $v_Z = 5.6$ V. Find v_O in terms of δ .

