

#1

(a)

$$R_1 = 38.6 \text{ K} \Rightarrow$$

$$I_1 = \frac{10 - 0.7 - (-10)}{R_1} = 0.5$$

$$R_2 = \frac{0.026}{0.14} \ln\left(\frac{0.5}{0.14}\right) \Rightarrow \underline{R_2 = 236 \Omega}$$

(b)

$$R_{icm} \approx (1 + \beta) R_o$$

$$R_o = r_{o4} (1 + g_{m4} R'_E) \quad g_{m4} = \frac{0.14}{0.026} = 5.385 \text{ mA/V}$$

$$r_{\pi4} = \frac{(180)(0.026)}{0.14} = 33.4 \text{ K}$$

$$R'_E = 33.4 \parallel 0.236 = 0.234 \text{ K}$$

$$r_{o4} = \frac{100}{0.14} = 714 \text{ K}$$

$$R_o = 714 [1 + (5.385)(0.234)] \\ = 1614 \text{ K}$$

$$R_{icm} = (181)(1614) \approx 292 \text{ M}\Omega$$

(c)

$$A_{cm} = \frac{-g_{m1} R_C}{1 + \frac{2(1 + \beta) R_o}{r_{\pi1}}} \quad g_{m1} = \frac{0.07}{0.026} = 2.692 \text{ mA/V}$$

$$r_{\pi1} = \frac{(180)(0.026)}{0.07} = 66.86 \text{ K}$$

$$A_{cm} = \frac{-(2.692)(40)}{1 + \frac{2(181)(1614)}{66.86}}$$

$$\underline{A_{cm} = -0.0123}$$

#2

(a) (b)

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$


$$r_{\pi 1} = \frac{(100)(0.026)}{(0.5/100)} = \frac{(100)^2 (0.026)}{0.5} = 520 \text{ k}\Omega$$

$$R_i = 520 + (101)(5.2) \Rightarrow \underline{R_i \cong 1.05 \text{ M}\Omega}$$

$$R_o = 5 \parallel \frac{r_{\pi 3} + 50}{101}, \quad r_{\pi 3} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$R_o = 5 \parallel \frac{2.6 + 50}{101} = 5 \parallel 0.521 \Rightarrow \underline{R_o = 0.472 \text{ k}\Omega}$$

(c)

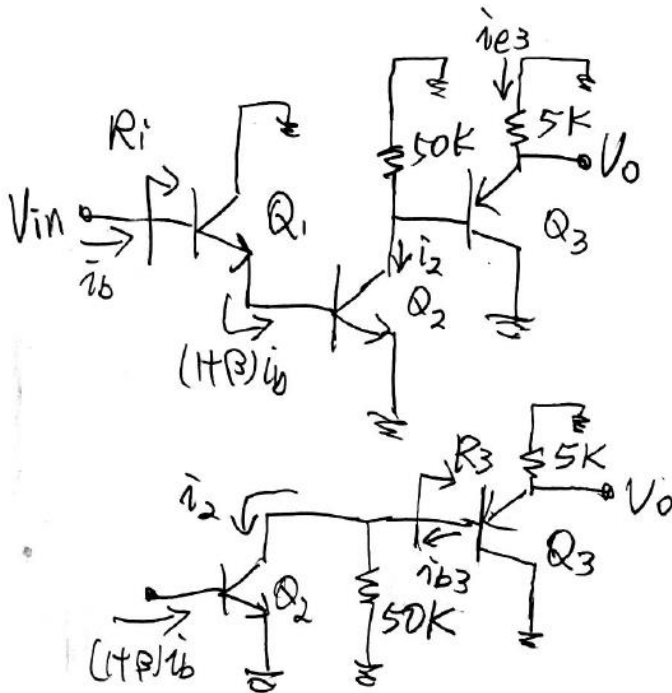

$$V_o = -i_{e3} \times 5$$

$$V_{in} = i_b \times R_i$$

$$R_3 = r_{\pi 3} + (1 + \beta) \times 5$$

$$= 2.6 + 5 \times 101 = 507.6 \text{ (k)}$$

$$i_2 = \beta (1 + \beta) i_b$$

$$i_{b3} = \frac{50}{50 + R_3} \times i_2, \quad i_{e3} = (1 + \beta) i_{b3}$$

$$V_o = -5 (1 + \beta) \cdot \frac{50}{50 + R_3} \times \beta (1 + \beta) i_b$$

$$\begin{aligned}
 A_v &= \frac{V_o}{V_{in}} = \frac{-5 \times 100 \times 10^2 \times 50}{R_i \times (50 + R_3)} \\
 &= - \frac{2550 \times 10^5}{1.05 \times 10^3 \times 557.6} \\
 &= - \frac{2550}{5.855} = -435.5
 \end{aligned}$$

#3

$$I_1 = I_3 = 400 \mu\text{A}$$

$$r_\pi = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$r_o(Q_3) = \frac{50}{0.4} = 125 \text{ k}\Omega$$

We have

$$A_d = \frac{\beta R_C}{2(r_\pi + R_B)} = \frac{(100)(28.5)}{2(13+10)} \Rightarrow A_d = 62$$

$$A_{cm} = - \frac{\beta R_C}{r_\pi + R_B} \left\{ \frac{1}{1 + \frac{2r_o(1+\beta)}{r_\pi + R_B}} \right\}$$

$$= - \frac{(100)(28.5)}{13+10} \left\{ \frac{1}{1 + \frac{2(125)(101)}{13+10}} \right\} \Rightarrow A_{cm} = -0.113$$

$$CMRR_{dB} = 20 \log_{10} \left(\frac{62}{0.113} \right) \Rightarrow CMRR_{dB} = 54.8 \text{ dB}$$

#4

$$I_1 = \frac{24 - V_{GS4}}{R_1} = k_n (V_{GS4} - V_{Th})^2$$

$$24 - V_{GS4} = (55)(0.2)(V_{GS4} - 2)^2$$

$$24 - V_{GS4} = 11(V_{GS4}^2 - 4V_{GS4} + 4)$$

$$11V_{GS4}^2 - 43V_{GS4} + 20 = 0$$

$$V_{GS4} = \frac{43 \pm \sqrt{(43)^2 - 4(11)(20)}}{2(11)} = 3.37 \text{ V}$$

$$I_1 = \frac{24 - 3.37}{55} = 0.375 \text{ mA} = I_Q$$

$$v_{02} = 12 - \left(\frac{0.375}{2}\right)(40) = 4.5 \text{ V}$$

$$\frac{v_{02} - V_{GS3}}{R_5} = I_{D3} = k_n (V_{GS3} - V_{Th})^2$$

$$4.5 - V_{GS3} = (0.2)(6)(V_{GS3}^2 - 4V_{GS3} + 4)$$

$$1.2V_{GS3}^2 - 3.8V_{GS3} + 0.3 = 0$$

$$V_{GS3} = \frac{3.8 \pm \sqrt{(3.8)^2 - 4(1.2)(0.3)}}{2(1.2)} = 3.09 \text{ V}$$

$$I_{D3} = \frac{4.5 - 3.09}{6} = 0.235 \text{ mA}$$

$$g_{m2} = 2\sqrt{K_n I_{D2}} = 2\sqrt{(0.2)\left(\frac{0.375}{2}\right)}$$
$$= 0.387 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2} g_{m2} R_D = \frac{1}{2} (0.387)(40) \Rightarrow A_{d1} = 7.74$$

$$A_2 = \frac{-g_{m3} R_{D2}}{1 + g_{m3} R_5}$$

$$g_{m3} = 2\sqrt{K_n I_{D3}} = 2\sqrt{(0.2)(0.235)}$$
$$= 0.434 \text{ mA/V}$$

$$A_2 = \frac{-(0.434)(4)}{1 + (0.434)(6)} = -0.482$$

$$\text{So } A_d = A_{d1} \cdot A_2 = (7.74)(-0.482) \Rightarrow \underline{A_d = -3.73}$$