

1.

$$(a) \frac{R_4}{R_3} = \frac{R_6}{R_5}$$

$$V_{01} = \frac{R_2}{R_3} (V_{o2} - V_{01})$$

$$V_{01} = \left(1 + \frac{R_2}{R_1}\right) V_{z1} - \frac{R_2}{R_1} V_{z2}$$

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_{z2} - \frac{R_2}{R_1} V_{z1}$$

$$\Rightarrow V_0 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{z2} - V_{z1})$$

$$(b) \frac{R_2}{R_1} = 2, \frac{R_4}{R_3} = 10, \frac{R_6}{R_5} = 11$$

$$V_0 = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_6/R_5}{1 + R_6/R_5}\right) \cdot V_{o2} - \frac{R_4}{R_3} V_{01}$$

$$= 11 \times \frac{11}{12} V_{o2} - 10 V_{01}$$

$$= 10.083 V_{o2} - 10 V_{01}$$

$$\begin{cases} V_{01} = 3V_{z1} - 2V_{z2} \\ V_{o2} = 3V_{z2} - 2V_{z1} \end{cases}$$

$$\Rightarrow V_0 = 10.083(3V_{z2} - 2V_{z1}) - 10(3V_{z1} - 2V_{z2})$$

$$= 50.25 V_{z2} - 50.167 V_{z1}$$

$$= A_{cm} \cdot \frac{V_{z1} + V_{z2}}{2} + A_d \cdot (V_{z2} - V_{z1})$$

$$= \left(A_d + \frac{A_{cm}}{2}\right) V_{z2} - \left(A_d - \frac{A_{cm}}{2}\right) V_{z1}$$

$$\Rightarrow \begin{cases} A_d + \frac{A_{cm}}{2} = 50.25 \\ A_d - \frac{A_{cm}}{2} = 50.167 \end{cases} \Rightarrow \begin{cases} A_d = 50.2085 \\ A_{cm} = 0.083 \end{cases}$$

$$CMRR(dB) = 20 \log_{10} \left( \frac{50.2085}{0.083} \right) = 20 \log_{10} (604.92) \\ = 55.634 \text{ (dB)}$$

2

$$R_1 = \frac{V_o - V_z}{I_z} = \frac{12 - 5.6}{2} = 3.2 \text{ k}\Omega$$

$$\frac{V_o}{V_z} = \left(1 + \frac{R_2}{R_3}\right) = \frac{12}{5.6} \Rightarrow \frac{R_2}{R_3} = 1.143$$

$$\text{Let } I_R = 2 \text{ mA, } \Rightarrow R_2 + R_3 = \frac{V_o}{I_R} = \frac{12}{2} = 6 \text{ k}\Omega$$

$$\text{Then } 1.143R_3 + R_3 = 6, \Rightarrow R_3 = 2.8 \text{ k}\Omega \text{ and } R_2 = 3.2 \text{ k}\Omega$$

$$R_L = 6 \text{ k}\Omega, I_{R_L} = 12 / 6 = 2 \text{ mA}$$

$$\text{Then } I_{R4} = 6 \text{ mA, } R_4 = \frac{15 - 12}{6} = 0.5 \text{ k}\Omega$$

3

$$(a) \quad A_v = \frac{-R_2}{Z_1}, \text{ where } Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$A_v = \frac{-j\omega R_2 C_1}{1 + j\omega R_1 C_1} = \frac{-R_2}{R_1} \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

$$(b) \quad \text{As } \omega \rightarrow \infty, \quad A_v = \frac{-R_2}{R_1}$$

$$(c) \quad |A_v| = \frac{R_2}{R_1} \cdot \frac{\omega R_1 C_1}{\sqrt{1 + (\omega R_1 C_1)^2}}$$

$$\text{Set } \frac{\omega R_1 C_1}{\sqrt{1 + (\omega R_1 C_1)^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega = \frac{1}{R_1 C_1} \Rightarrow f = \frac{1}{2\pi R_1 C_1}$$

2

4.

(a)

For  $v_O = 5 \text{ V}$ ,  $i_L = 5/20 = 0.25 \text{ A}$

Then, for  $I_Q = 0.05 \text{ A}$  when  $v_O = 0$ , we have

$$I_{DQ} = 0.05 = K \left( \frac{V_{BB}}{2} - |V_T| \right)^2 = (0.20) \left( \frac{V_{BB}}{2} - 1 \right)^2$$

which yields

$$V_{BB}/2 = 1.50 \text{ V}$$

$$V_{BB} = 3 \text{ V}$$

(b)

The input voltage for  $v_O$  positive is

$$v_I = v_O + v_{GSn} - \frac{V_{BB}}{2}$$

For  $v_O = 5 \text{ V}$  and  $i_{Dn} \cong i_L = 0.25 \text{ A}$ , we have

$$v_{GSn} = \sqrt{\frac{i_{Dn}}{K}} + |V_T| = \sqrt{\frac{0.25}{0.20}} + 1 = 2.12 \text{ V}$$

The source-to-gate voltage of  $M_p$  is

$$v_{SGp} = V_{BB} - v_{GSn} = 3 - 2.12 = 0.88 \text{ V}$$

(c)

$$v_I = 5 + 2.12 - 1.5 = 5.62 \text{ V}$$