

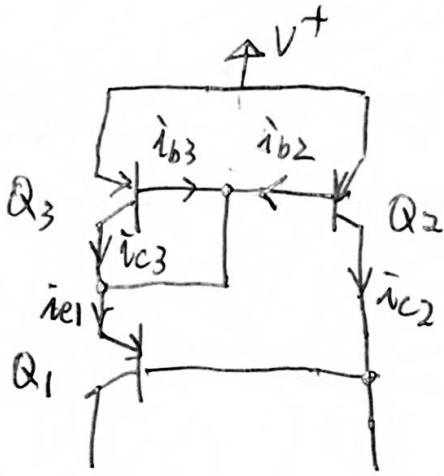


1.

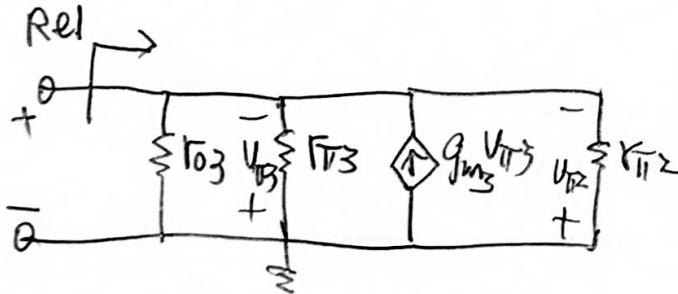

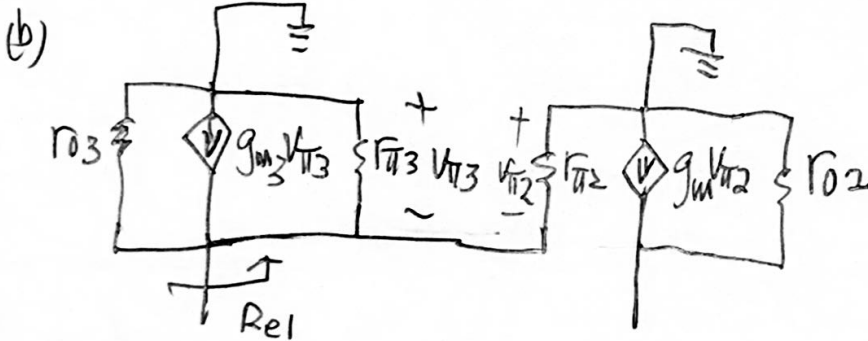(a) $\because V_{EB3} = V_{EB2}$
 $\therefore i_{c3} = i_{c2}, i_{b3} = i_{b2}$
 $i_{e1} = i_{c3} + 2i_{b2}$
 $= (\beta + 2)i_{b2} = \frac{\beta + 2}{\beta} i_{c2}$


when $\beta \rightarrow \infty, i_{e1} \approx i_{c2}$ *



$$R_{e1} = r_{o3} \parallel r_{\pi 3} \parallel r_{\pi 2} \parallel \frac{1}{g_{m3}} *$$


$\because \frac{1}{g_{m3}} \ll r_{\pi 2}, r_{\pi 3} \ll r_{o3}, \frac{1}{g_{m3}} \rightarrow 0$ (very small)

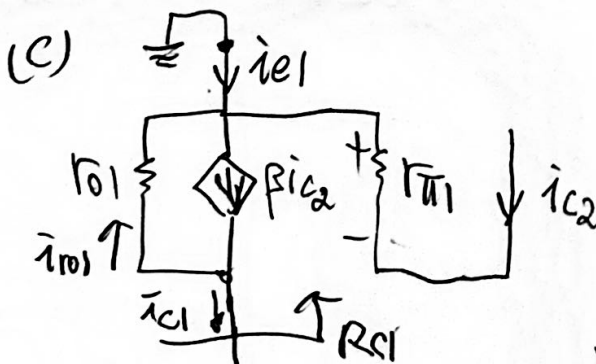$\therefore R_{e1} \rightarrow 0$ can be treated as virtual ground w.r.t. r_{o1} .



from (a), $i_{e1} = i_{c2}$
 $i_{c1} = i_{e1} + i_{c2} = 2i_{c2}$
 $\Rightarrow i_{r_{o1}} = (\beta - 2)i_{c2}$
 $\therefore R_{o1} = \frac{-i_{r_{o1}} \cdot r_{o1}}{-i_{c1}} = \frac{\beta - 2}{2} r_{o1} \approx \beta r_{o1} / 2$ *

(d)

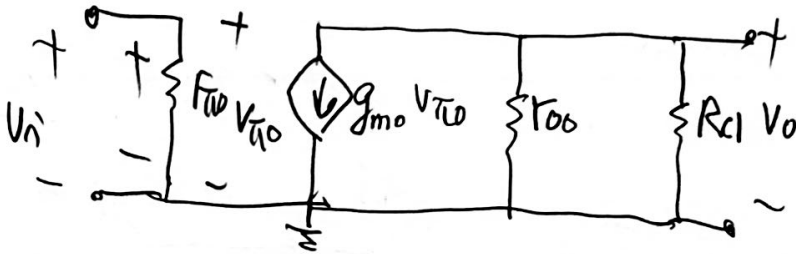

$$A_v = \frac{V_o}{V_i} = -g_{m0}(r_{o0} \parallel R_{L1})$$

$$g_{m0} = \frac{I_{REF}}{V_T} = \frac{1}{0.026} = 38.46 \text{ (mA/V)}$$

$$r_{o0} = \frac{V_{AN}}{I_{REF}} = \frac{150}{1} = 150 \text{ (k}\Omega\text{)}$$

$$R_{L1} = \frac{250}{2} \cdot \frac{V_{AP}}{1} = 125 \times 120 = 15000 \text{ (k}\Omega\text{)}$$

$$A_v = -38.46 \times \frac{15000 \times 150}{15000 + 150} = -5712 \#$$

2.

$$\begin{cases} I_{REF} = K_{p1}(V_{SG1} + V_{TP1})^2 = K_{p2}(V_{SG2} + V_{TP2})^2 \quad \text{--- (1)} \\ V^+ = V_{SG2} + V_{SG1} + V^- \quad \text{--- (2)} \end{cases}$$

From (1),

$$\begin{cases} \sqrt{K_{p1}}(V_{SG1} + V_{TP1}) = \sqrt{K_{p2}}(V_{SG2} + V_{TP2}) \\ V^+ = V_{SG2} + V_{SG1} + V^- \end{cases}$$

Solve for \$V_{SG2}\$, then $I_{REF} = K_{p2}(V_{SG2} + V_{TP2})^2 \#$

$$\begin{cases} V_{SG1} - 1 = 3(V_{SG2} - 1) \\ 6 = V_{SG2} + V_{SG1} \end{cases} \Rightarrow V_{SG2} = 2, \quad V_{SG3} = V_{SG2} = 2$$

$$V_{SD3}(\text{sat}) = V_{SG3} + V_{TP} = 1,$$

if \$M_3\$ remains biased in the saturation region,

$$V_{SD3} \geq V_{SD3}(\text{sat}) = 1$$

$$\therefore V_{SD3} = V^+ - V^- - I_0 R = 6 - 12 I_0 \geq 1, \quad I_0 \leq \frac{5}{12} \text{ (mA)} \#$$

$$(c) \quad 0.2 = \frac{0.1}{2} \left(\frac{W}{L}\right)_3 (2-1)^2 = \frac{0.1}{2} \left(\frac{W}{L}\right)_3 \Rightarrow \left(\frac{W}{L}\right)_3 = 4 \#$$

$$3. (a) I_{REF} = \frac{\mu_n}{2} \left(\frac{W}{L}\right)^3 (V_{GS3} - 1)^2$$

$$0.1 = \frac{0.08}{2} \times 4 \cdot (V_{GS3} - 1)^2$$

$$V_{GS3} = 1 + 0.79 = 1.79$$

$\therefore \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$, for a same I_{REF} current,

$$\Rightarrow V_{GS1} = V_{GS2} = V_{GS} \quad *$$

$$\therefore V^+ = V_{GS1} + V_{GS2} + V_{GS3} = 2V_{GS} + V_{GS3}$$

$$V_{GS} = \frac{5 - 1.79}{2} = 1.605$$

$$0.1 = \frac{0.08}{2} \cdot \left(\frac{W}{L}\right)_2 (1.605 - 1)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_1 = \frac{20}{8 \times (0.605)^2} = 6.83 \quad *$$

$$(b) I_{ol, min} = \frac{\mu_n}{2} \left(\frac{W}{L}\right)_4 (V_{GS4} - 1)^2 (1 + \lambda_4 V_{DS4(sat)})$$

$$0.5 = \frac{0.08}{2} \left(\frac{W}{L}\right)_4 (0.79)^2 (1 + 0.05 \times 0.79)$$

$$\left(\frac{W}{L}\right)_4 = \frac{1}{0.08 \times (0.79)^2 \times 1.0395} \approx 19.27 \quad *$$


$$(c) V_{GS3} = V_{GS5} + I_{O2} \cdot R_S \geq V_{TN} + I_{O2} \cdot R_S, \because V_{GS5} \geq V_{TN}$$

$$1.79 \geq 1 + 0.04 \cdot R_S, \quad R_S \leq 19.75 \text{ (k}\Omega) \quad *$$

$$(d) 40 = \frac{80}{2} \left(\frac{W}{L}\right)_5 (V_{GS5} - 1)^2 (1 + \lambda_5 V_{DS5(sat)})$$

$$V_{GS5} = V_{GS3} - I_{O2} \cdot R_S = 1.79 - 0.04 \times 10 = 1.39$$
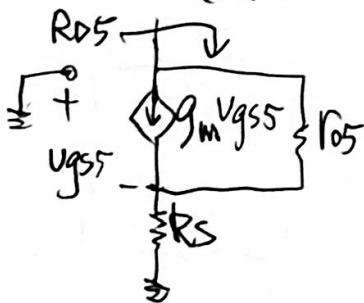
$$1 = \left(\frac{W}{L}\right)_5 \times (0.39)^2 (1 + 0.01 \times 0.39), \quad \left(\frac{W}{L}\right)_5 = 6.55 \quad *$$



$$R_{D5} = R_S + r_{o5} (1 + g_m R_S)$$

$$g_m = 2 \sqrt{I_{O2} \cdot K_{n5}} = 2 \sqrt{0.04 \times 0.262} = 0.205 \text{ (mA/V)}$$

$$r_{o5} = 1 / (\lambda_5 \cdot I_{O2}) = 1 / (0.01 \times 0.04) = 2500 \text{ (k}\Omega)$$

$$R_{D5} = 10 + 2500 (1 + 0.205 \times 10) = 7635 \text{ (k}\Omega) \quad *$$