
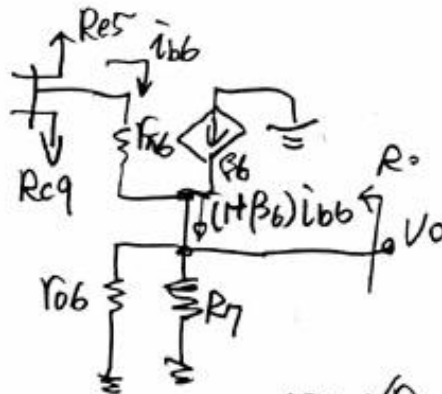



Electronics II 2021.  
25th June, D.C. Chang

#1

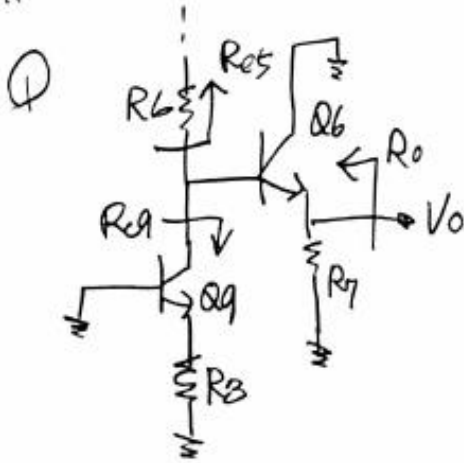


$$R_o = r_{o6} \parallel R_7 \parallel \frac{r_{\pi 6} + (R_{e5} \parallel R_{c9})}{1 + \beta_6}$$

②

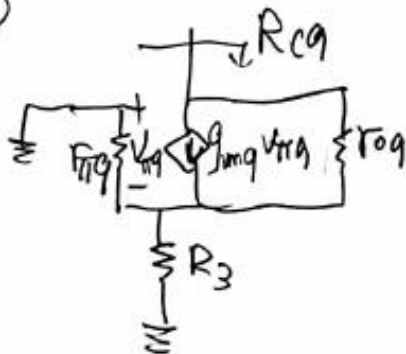


$$R_{c9} = (r_{\pi 9} \parallel R_3) + r_{o9} (1 + g_{m9} (r_{\pi 9} \parallel R_3))$$


③

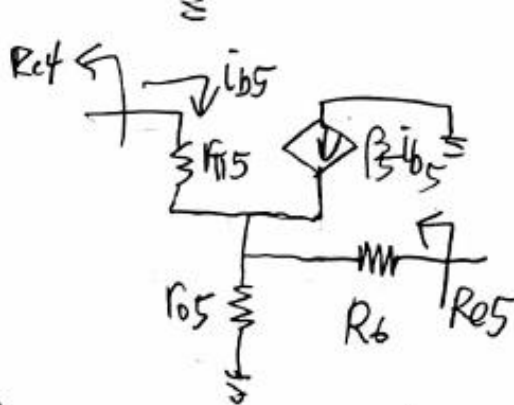

$$R_{e5} = R_6 + r_{o5} \parallel \frac{r_{\pi 5} + R_{c4}}{1 + \beta_5}$$

④

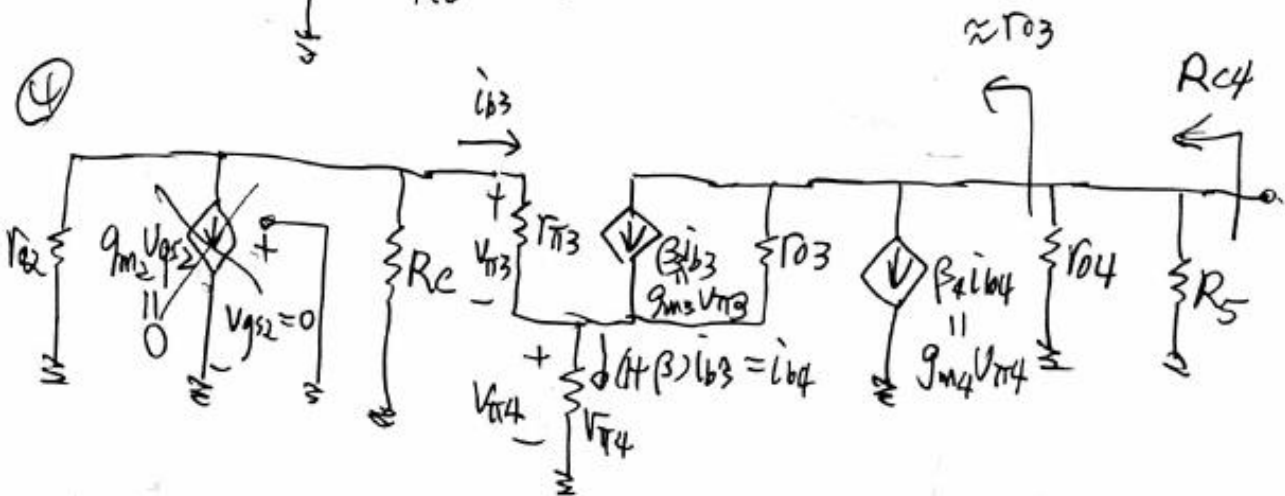

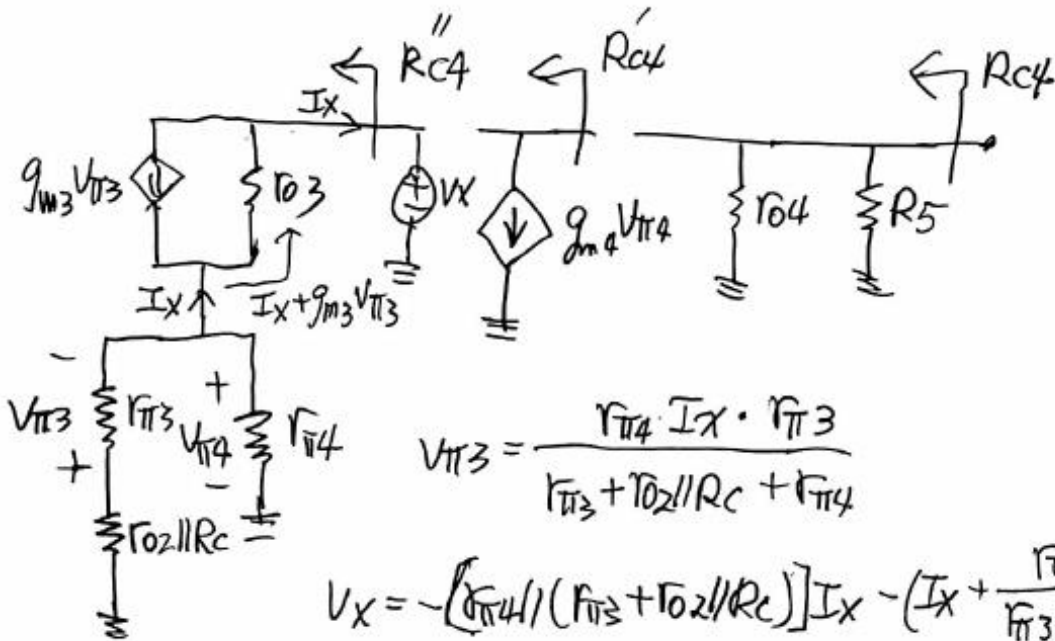

$$v_{\pi 3} = \frac{r_{\pi 4} I_X \cdot r_{\pi 3}}{r_{\pi 3} + r_{o2} \parallel R_C + r_{\pi 4}}$$

$$v_X = - \left[ \frac{r_{\pi 4}}{r_{\pi 3} + r_{o2} \parallel R_C} \right] I_X - \left( I_X + \frac{r_{\pi 4} I_X \cdot r_{\pi 3} g_{m3}}{r_{\pi 3} + r_{o2} \parallel R_C + r_{\pi 4}} \right) r_{o3}$$

$$R_{o4}'' = - \frac{v_X}{I_X} = r_{\pi 4} \parallel (r_{o3} + r_{o2} \parallel R_C) + \left( 1 + \frac{\beta_3 r_{\pi 4}}{r_{\pi 3} + r_{o2} \parallel R_C + r_{\pi 4}} \right) r_{o3}$$

$$\approx \frac{\beta_3 r_{\pi 4} \cdot r_{o3}}{r_{\pi 3} + r_{\pi 4} + r_{o2} \parallel R_C} \approx \beta_3 r_{o3} \text{ (order of magnitude)}$$

$$v_{\pi 4} = - \frac{r_{\pi 3} + r_{o2} \parallel R_C}{r_{\pi 3} + r_{\pi 4} + r_{o2} \parallel R_C} I_X \cdot r_{\pi 4}$$

$$R_{o4}' = \frac{v_X}{g_{m4} v_{\pi 4}} \approx \frac{\frac{\beta_3 r_{\pi 4} \cdot r_{o3}}{r_{\pi 3} + r_{\pi 4} + r_{o2} \parallel R_C} \cdot I_X}{\frac{\beta_4 (r_{\pi 3} + r_{o2} \parallel R_C)}{r_{\pi 3} + r_{\pi 4} + r_{o2} \parallel R_C} \cdot I_X}$$

$$\approx \frac{\beta_3 \cdot r_{\pi 4} \cdot r_{o3}}{\beta_4 (r_{\pi 3} + r_{o2} \parallel R_C)} \approx r_{o3} \text{ (order of magnitude)}$$

$$R_{o4} = R_5 \parallel r_{o4} \parallel R_{o4}' \parallel R_{o4}''$$

Approximation:

$$R_{o2} \approx \frac{r_{\pi 6} + R_{e5}}{1 + \beta_6} \parallel R_7$$

$$R_{o4} \approx R_5$$

$$R_{e5} \approx R_6 + \frac{r_{\pi 5} + R_5}{1 + \beta_5}$$

$$\approx \frac{1}{1 + \beta_6} \left( r_{\pi 6} + R_6 + \frac{r_{\pi 5} + R_5}{1 + \beta_5} \right) \parallel R_7$$


$$R_{o9} \approx g_{m9} \cdot (r_{\pi 9} \parallel R_3) \cdot r_{o9}$$

#2. (a)  $V_{O2} = 2 \text{ (V)}$ ,  $I_R = \frac{I_Q}{2} = 0.25 \text{ (mA)}$


$$R = \frac{5-2}{0.25} = 12 \text{ (k}\Omega\text{)}$$

$$V_2 = V_{O2} - V_{DS2} + V_{GS2} \leq V_{O2} - V_{DS2(\text{sat})} + V_{GS2}$$
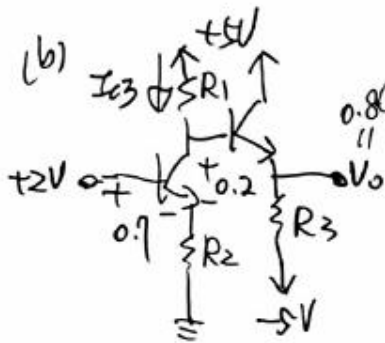
$$= V_{O2} - (V_{GS2} - V_{TN}) + V_{GS2} = V_{O2} + V_{TN} = 2.8 \text{ (V)}$$



$0.8 \text{ (V)}$   $V_O = 2 - 0.7 + V_{CE3} - 0.7 \geq 0.6 + V_{CE3(\text{sat})}$   
 $V_{CE3(\text{sat})} = 0.2 \text{ (V)}$   
 $\therefore V_O \geq 0.6 + 0.2 = 0.8 \text{ (V)}$ ,  $V_O(\text{min}) = 0.8 \text{ (V)}$   
 $I_{C3} \cdot R_2 = 2 - 0.7 = 1.3$ ,  $R_2 = \frac{1.3}{0.25} = 5.2 \text{ (k}\Omega\text{)}$   
 $I_{C3} \cdot R_1 = 5 - (0.8 + 0.7) = 3.5$ ,  $R_1 = \frac{3.5}{0.25} = 14 \text{ (k}\Omega\text{)}$

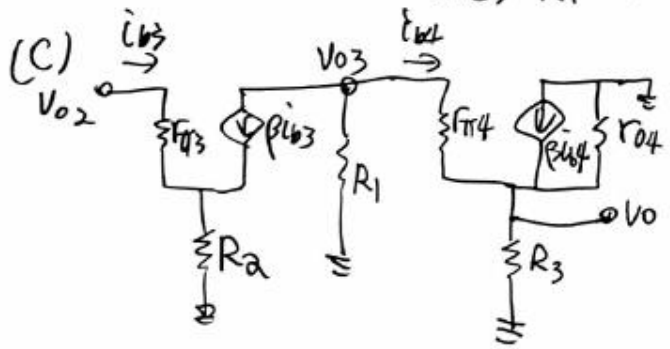

$$V_{O2} = i_{b3} \cdot [r_{\pi 3} + (1+\beta) R_2]$$

$$V_{O3} = -\beta i_{b3} [R_1 \parallel (r_{\pi 4} + (1+\beta)(R_3 \parallel R_5))]$$

$$V_{O3} = i_{b4} [r_{\pi 4} + (1+\beta)(R_3 \parallel R_5)]$$

$$V_O = (1+\beta) i_{b4} \cdot (R_3 \parallel R_5)$$

$$\frac{V_O}{V_{O2}} = \frac{V_{O3}}{V_{O2}} \cdot \frac{V_O}{V_{O3}}$$

$$= \frac{-\beta [R_1 \parallel (r_{\pi 4} + (1+\beta)(R_3 \parallel R_5))]}{r_{\pi 3} + (1+\beta) R_2} \times \frac{(1+\beta)(R_3 \parallel R_5)}{r_{\pi 4} + (1+\beta)(R_3 \parallel R_5)}$$

$$r_{\pi 3} = \frac{\beta V_T}{I_{C3}} = \frac{250 \times 0.026}{0.25} = 26 \text{ (k}\Omega\text{)}$$

$$r_{\pi 4} = \frac{\beta V_T}{I_{C4}} = \frac{250 \times 0.026}{2} = 3.25 \text{ (k}\Omega\text{)}$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{90}{2} = 45 \text{ (k}\Omega\text{)}$$


$$R_3 = \frac{0.8 - (-5)}{2} = 2.9 \text{ (k}\Omega\text{)}$$

$$R_3 \parallel r_{o4} = 2.9 \parallel 45 = 2.7244$$


$$r_{\pi 4} + (1+\beta)(R_3 \parallel r_{o4}) = 3.25 + 251 \times 2.7244 = 687.0744$$

$$\frac{V_O}{V_{O2}} = \frac{-250 \times (14 \parallel 687)}{26 + 251 \times 5.2} \times \frac{251 \times 2.7244}{687.0744} = -\frac{3430}{1331.2} \times 0.995$$

$$= -2.564$$

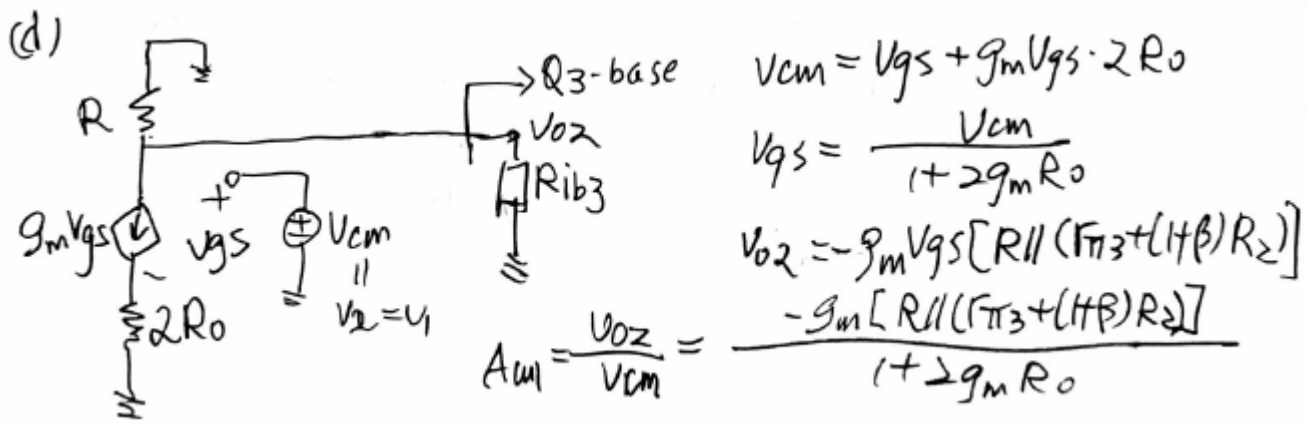

(e)  $A_d = \frac{V_{o2}}{V_d}$

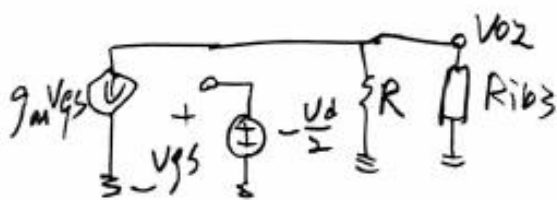


$V_{o2} = \frac{1}{2} g_m V_d \cdot (R \parallel R_{iB3})$

$A_d = \frac{1}{2} g_m (R \parallel R_{iB3})$

$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \left| \frac{\frac{1}{2} g_m}{\frac{g_m}{1 + 2g_m R_o}} \right|$   
 $= \frac{1 + 2g_m R_o}{2}$

$g_m = \sqrt{2k_n I_a} = \sqrt{2 \times 0.2 \times 0.5}$   
 $= 0.4472 \text{ (mA/V)}$

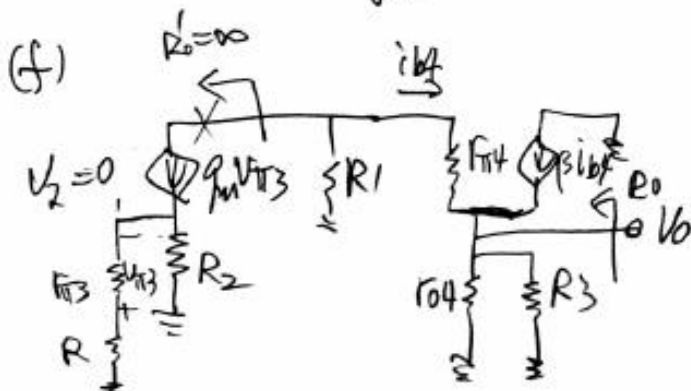
$CMRR_{dB} = 20 \log_{10} \left( \frac{1 + 2 \times 0.4472 \times 200}{2} \right)$   
 $= 20 \log_{10} (89.94) = 39.079 \text{ (dB)}$



$R_o = r_{o4} \parallel R_3 \parallel \frac{\Gamma_{\pi 4} + R_1}{1 + \beta}$   
 $R_o = 45 \parallel 2.9 \parallel \frac{7.25 + 14}{251}$   
 $= 45 \parallel 2.9 \parallel 0.0687$   
 $= 0.067 \text{ (k}\Omega\text{)}$



#3.

(a)

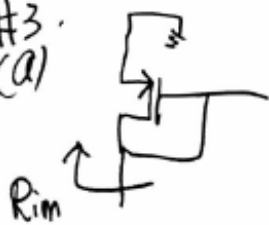

$$R_{im} = r_o \parallel \frac{1}{g_m}$$

(b) Differential-mode

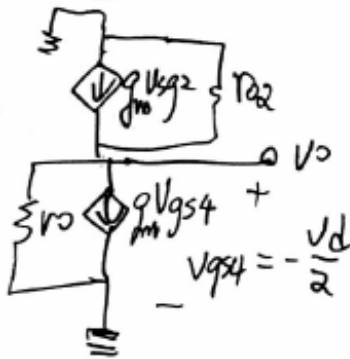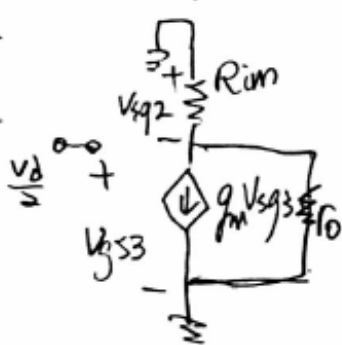

$$R_o = r_o$$

$$G_{V2} = -\frac{1}{2} g_m V_d$$

$$R_{om} = r_{o2} = r_o$$

$$V_{gs2} = i_d \cdot R_{im} = \frac{1}{2} g_m V_d \left( \frac{1}{g_m} \parallel r_o \right)$$


$$\approx \frac{1}{2} V_d$$

$$V_o = \left( \frac{1}{2} g_m V_d \right) \times 2 \times (r_o \parallel r_o)$$


$$= g_m V_d \cdot \frac{r_o}{2} = \frac{1}{2} g_m r_o V_d$$

$$A_d = \frac{V_o}{V_d} = \frac{1}{2} g_m r_o$$

(c)

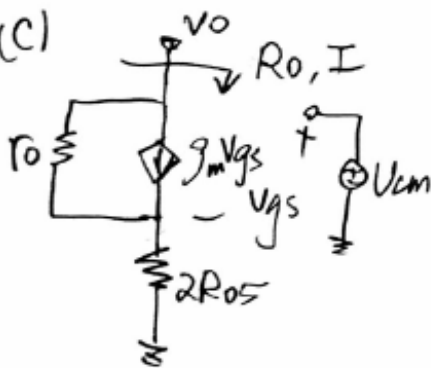


①  $R_o : (V_{cm} = 0)$

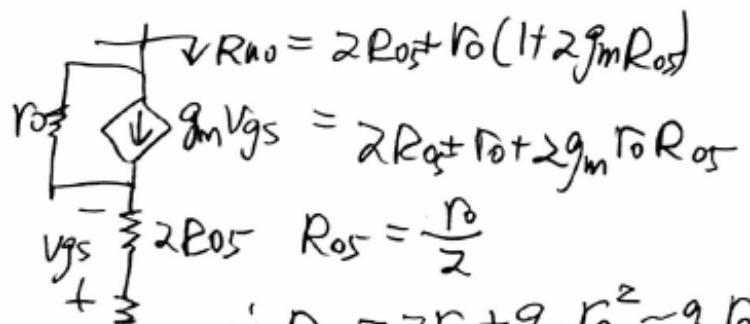

$$\therefore R_o = 2r_o + g_m r_o^2 \approx g_m r_o^2$$

②

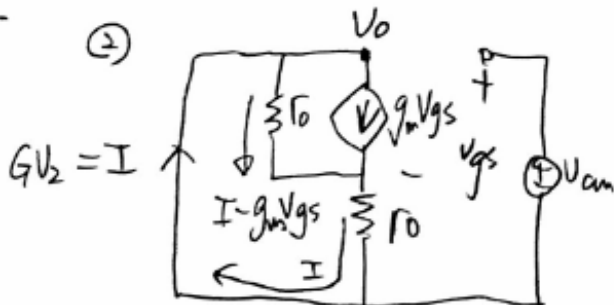

$$V_{cm} = v_{gs} + I \cdot r_o, \quad v_{gs} = V_{cm} - I r_o$$



$$(I - g_m v_{gs}) r_o + I r_o = 0$$

$$I r_o - g_m r_o (V_{cm} - I r_o) + I r_o = 0$$

$$2I r_o + I g_m r_o^2 = g_m r_o V_{cm}$$

$$G_{V2} = I = \frac{g_m V_{cm}}{2 + g_m r_o} \approx \frac{V_{cm}}{r_o}$$

(d)

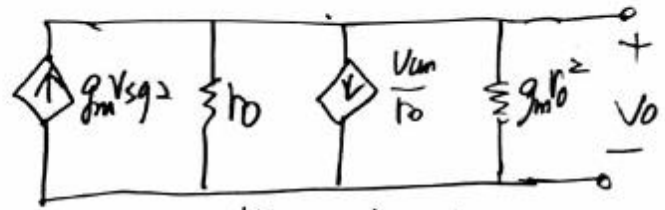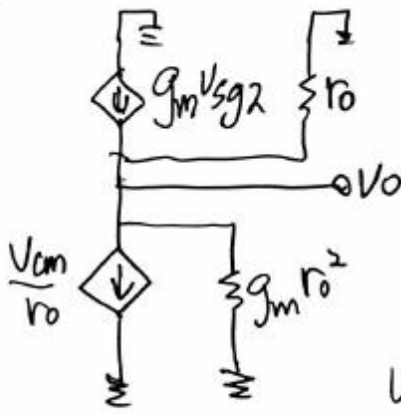

$$v_{sq2} = i_d \cdot \left( \frac{1}{g_m} \parallel r_o \right) = \frac{v_{cm}}{r_o} \cdot \left( \frac{1}{g_m} \parallel r_o \right)$$

$$v_o = -\frac{v_{cm}}{r_o} \left( 1 - g_m \left( \frac{1}{g_m} \parallel r_o \right) \right) \cdot (r_o \parallel g_m r_o^2)$$

$$\approx -\frac{v_{cm}}{g_m r_o^2} \cdot (r_o \parallel g_m r_o^2)$$

$$A_{cm} = \frac{v_o}{v_{cm}} \approx -\frac{r_o \parallel g_m r_o^2}{g_m r_o^2} \approx -\frac{1}{g_m r_o}$$

$$(e) \quad CMRR = \left| \frac{A_d}{A_{cm}} \right| = \frac{\frac{1}{2} g_m r_o}{\frac{1}{g_m r_o}} = \frac{1}{2} g_m^2 r_o^2$$

$$g_m = \sqrt{2k_n I_Q}, \quad r_o = \frac{2}{\lambda I_Q}$$

$$CMRR = \frac{1}{2} \cdot 2k_n I_Q \cdot \frac{4}{\lambda^2 I_Q^2} = \frac{4k_n}{\lambda^2 I_Q} \quad \#$$