

(1)

$$R_{TH} = R_1 \parallel R_2 = 1.2 \parallel 1.2 = 0.6 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) (V_{cc}) = \left(\frac{1.2}{1.2 + 1.2} \right) (5) = 2.5 \text{ V}$$

$$I_{BQ} = \frac{2.5 - 0.7}{0.6 + (101)(0.05)} = 0.319 \text{ mA}$$

$$I_{CQ} = 31.9 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{31.9} = 0.0815 \text{ k}\Omega$$

$$\tau_{C_{c1}} \gg \tau_{C_{c2}} \text{ and } f = \frac{1}{2\pi\tau} \text{ so that } f_{3-dB}(C_{c1}) \ll f_{3-dB}(C_{c2})$$

Then, for $f_{3-dB}(C_{c1}) \Rightarrow C_{c2}$ acts as an open and for $f_{3-dB}(C_{c2}) \Rightarrow C_{c1}$ acts as a short circuit.

$$f_{3-dB}(C_{c2}) = 25 \text{ Hz} = \frac{1}{2\pi\tau_2}, \text{ so that } \tau_2 = \frac{1}{2\pi(25)} = 0.006366 \text{ s} = R_{eq} C_{c2}$$

where

$$\begin{aligned} R_{eq} &= R_L + R_E \left| \left(\frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} \right) \right| \\ &= 10 + 50 \left| \left(\frac{81.5 + 600 \parallel 300}{101} \right) \right| = 10 + 50 \parallel 2.787 \Rightarrow \end{aligned}$$

$$R_{eq} = 12.64 \text{ }\Omega \Rightarrow C_{c2} = \frac{0.00637}{12.6} \Rightarrow \underline{C_{c2} = 504 \text{ }\mu F}$$

$$R_{ib} = r_\pi + (1 + \beta) R_E \text{ Assume } C_{c2} \text{ an open}$$

$$R_{ib} = 81.5 + (101)(50) = 5132 \text{ }\Omega$$

$$\tau_1 = (100)\tau_2 = (100)(0.006366) = 0.6366 \text{ s} = R_{eq1} C_{c1}$$

$$R_{eq1} = R_s + R_{TH} \parallel R_{ib} = 300 + 600 \parallel 5132 = 837.2 \text{ }\Omega$$

$$\text{So } C_{c1} = \frac{0.6366}{837.2} \Rightarrow \underline{C_{c1} = 760 \text{ }\mu F}$$

(2)

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left(\frac{22}{22 + 8} \right) (20) - 10$$

$$V_G = 4.67 \text{ V}$$

$$I_D = \frac{10 - V_{SG} - 4.67}{R_S} = K_P (V_{SG} + V_{TP})^2$$

$$5.33 - V_{SG} = (1)(0.5)(V_{SG}^2 - 4V_{SG} + 4)$$

$$0.5V_{SG}^2 - V_{SG} - 3.33 = 0$$

$$V_{SG} = \frac{1 \pm \sqrt{1+4(0.5)(3.33)}}{2(0.5)} \Rightarrow V_{SG} = 3.77 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(3.77 - 2)$$

$$g_m = 3.54 \text{ mA/V}$$

b.

$$C_M = C_{gdT}(1 + g_m(R_D \| R_L))$$

$$C_M = (3)[1 + (3.54)(2\|5)] \Rightarrow C_M = 18.2 \text{ pF}$$

a.

$$r = R_{eq}(C_{gsT} + C_M)$$

$$R_{eq} = R_i \| R_1 \| R_2 = 0.5 \| 8 \| 22 = 0.461 \text{ k}\Omega$$

$$r = (0.461 \times 10^3)(15 + 18.2) \times 10^{-12}$$

$$= 1.53 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi r} \Rightarrow f_H = 10.4 \text{ MHz}$$

c.

$$V_0 = -g_m V_{gs}(R_D \| R_L)$$

$$V_{gs} = \left(\frac{R_1 \| R_2}{R_1 \| R_2 \| R_i} \right) V_i = \left(\frac{5.87}{5.87 + 0.5} \right) V_i \Rightarrow V_{gs} = (0.9215) V_i$$

$$A_v = -(3.54)(0.9215)(2\|5) \Rightarrow A_v = -4.66$$

(3)

dc analysis

$$I_D = \frac{V^+ - V_{SG}}{R_S} = K_P(V_{SG} + V_{TP})^2$$


$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2 \\ = 4(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(4)(2.44)}}{2(4)} = 1.707$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(1.707 - 0.8)$$

$$g_m = 1.81 \text{ mA/V}$$

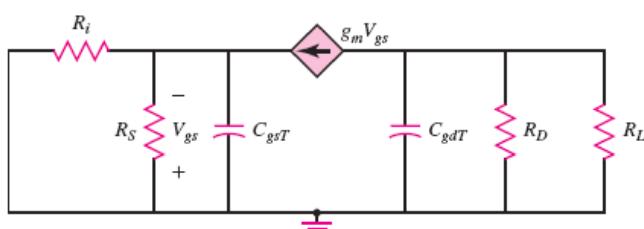

$$3 \cdot dB \text{ frequency due to } C_{gsT} : R_{eq} = \frac{1}{g_m} \| R_S \| R_i$$

$$f_A = \frac{1}{2\pi R_{eq} \cdot C_{gdT}}$$

$$R_{eq} = \frac{1}{1.81} \| 4 \| 0.5 = 0.246 \text{ k}\Omega$$


$$f_A = \frac{1}{2\pi(246)(4 \times 10^{-12})} = 162 \text{ MHz}$$

3-dB frequency due to C_{gdT}

$$\begin{aligned} f_B &= \frac{1}{2\pi(R_D \| R_L)C_{gdT}} \\ &= \frac{1}{2\pi(2 \| 4) \times 10^3 \times 10^{-12}} \end{aligned}$$

$$\underline{f = 119 \text{ MHz}}$$

Midband gain

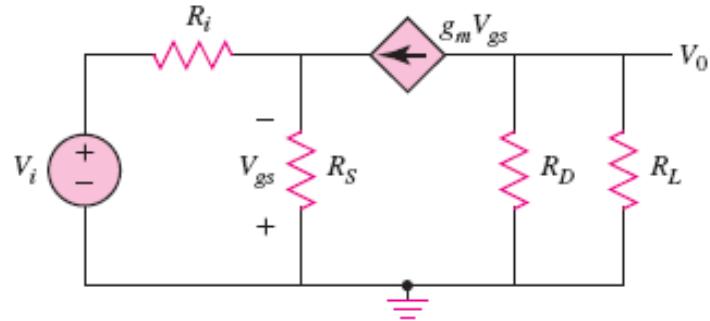

$$\begin{aligned} V_{gs} &= -\frac{1}{g_m} \| R_s \cdot V_i = -\frac{1}{1.81} \| 4 \cdot V_i \\ &= -0.492 V_i \end{aligned}$$

$$V_0 = -g_m V_{gs} (R_D \| R_L)$$

$$A_v = (0.492)(1.81)(4 \| 2) \Rightarrow \underline{A_v = 1.19}$$