

Exam-2, Electronics 2022 DCchang.

#1. $V_{CE} = V_{CC} - I_C \cdot R_L = 30 - 1.4 \times 20 = 2 \text{ (V)}$

$P_T = I_C \cdot V_{CE} = 1.4 \times 2 = 2.8 \text{ (W)}$

$\therefore T_{junc} - T_{amb} = P_T \cdot (\Sigma \theta)$

$\therefore 150 - 24 = 2.8 (\theta_{junc-case} + 43)$ without sink.
 $= 126$

$\Rightarrow \theta_{junc-case} = 45 - 43 = 2 \text{ (}^\circ\text{C/W)}$

with heat sink,

$P_{sink}(2+1+3) = 126 \Rightarrow P_{sink} = 21 \text{ (W)}$

$V_{CE} = \frac{21}{1.4} = 15 \text{ (V)}$

$= 30 - 1.4 \cdot R_L, R_L = \frac{15}{1.4} = \underline{10.714 \text{ (}\Omega)}$

#2. (a) $I_{DQ} = 20\% \times \frac{8}{25} = 64 \text{ mA}$

At the Q-point,

$I_{DQ} = K \cdot (V_{GS} - |V_T|)^2$

$64 = 250 (V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 1.706 \text{ (V)}$

$\therefore V_{BB} = 2 \cdot V_{GS} = \underline{3.412 \text{ (V)}}$

(b) $V_o = -12, I_L = I_{Dp} = \frac{12}{25} = 480 \text{ (mA)}$

$480 = K (V_{Ssp} - 1.2)^2$

$\Rightarrow V_{Ssp} = 1.2 + \sqrt{\frac{480}{250}} = 2.586 \text{ (V)}$

$V_I = -12 - 2.586 + 1.706 = \underline{-12.88 \text{ (V)}}$

$\therefore V_{Ssp} > |V_T| \therefore M_p$ turns on

$V_{GS} = 3.412 - V_{Ssp} = 0.826 < |V_T|$

$\therefore M_n$ turns off.

#3 (a) $\frac{V_o}{V_i} = -\frac{Z_2}{R_1}$, $Z_2 = R_2 \parallel \frac{1}{sC_2}$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$\therefore \frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

(b) as $\omega \rightarrow 0$, $\frac{V_o}{V_i} = -\frac{R_2}{R_1}$

as $\omega \rightarrow \infty$, $\frac{V_o}{V_i} = 0$

\therefore lowpass filter.

(c) $\frac{V_o}{V_i} \Big|_{\omega \rightarrow 0} = -\frac{R_2}{R_1}$

\therefore 3 dB freq at $\left| \frac{1}{1 + j\omega R_2 C_2} \right| = \frac{1}{\sqrt{2}}$

or $1 + (\omega R_2 C_2)^2 = 2$

$\Rightarrow \omega = \frac{1}{R_2 C_2}$ or $f = \frac{1}{2\pi R_2 C_2}$ *

#4.

$$V_{o1} = \left(1 + \frac{40}{12}\right) V_i$$

$$V_{o2} = -\frac{30}{12} V_i$$

$$\frac{V_o}{V_i} = \frac{V_{o1} - V_{o2}}{V_i} = 1 + \frac{40}{12} + \frac{30}{12} = 1 + \frac{70}{12} = 6.833$$
 *

#5.

(a) $V_{o1} = -\frac{R_2}{R_1} V_{cm}$

$$V_{o2} = \frac{R_4}{R_3 + R_4} \cdot V_{cm} \left(1 + \frac{R_4}{R_3}\right)$$

$$\frac{V_o}{V_{cm}} = \frac{V_{o1} + V_{o2}}{V_{cm}} = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_4}{R_3}\right) - \frac{R_2}{R_1} = \frac{\frac{R_4}{R_3} - \frac{R_2}{R_1}}{1 + \frac{R_4}{R_3}}$$

(b) when $\frac{R_4}{R_3} = \frac{R_2}{R_1}$ or $R_1 R_4 = R_2 R_3$, $\frac{V_o}{V_{cm}} = 0$.