
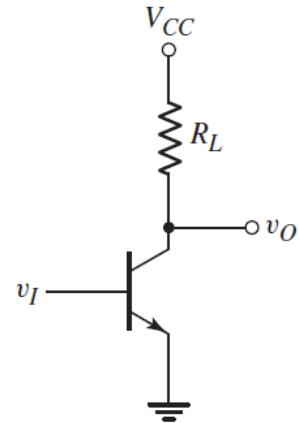


Electronics II, Exam-2, Spring 2022
 Department of Communication Engineering, National Central University
 April 22, 2022, Prof. Dah-Chung Chang (E1-311)

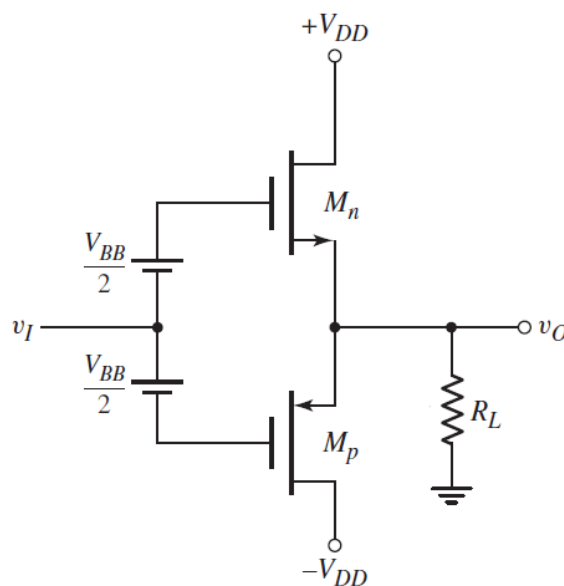1. (20%) Assume that $V_{CC} = 30V$ and a power BJT is operating with an average collector current of $I_C = 1.4A$. Consider that the power BJT is able to be fixed onto a heat sink. The thermal resistance parameters related to the heat sink are $\theta_{\text{case-snk}} = 1^\circ\text{C/W}$, $\theta_{\text{snk-amb}} = 3^\circ\text{C/W}$, and $\theta_{\text{case-amb}} = 43^\circ\text{C/W}$. Suppose that the BJT junction temperature is 150°C and the ambient temperature is 24°C when the power BJT works for $R_L = 20\Omega$ without the heat sink. Determine the minimum R_L with which the power BJT can work at the same temperature when the heat sink is used.




2. (30%) Consider the MOSFET class-AB output stage. The circuit parameters are $V_{DD} = 15V$ and $R_L = 25\Omega$. The transistors are matched with parameters $K = 0.25\text{ A/V}^2$ and $|V_T| = 1.2V$. The quiescent drain currents are to be 20 percent of the load current when $v_O = 8V$.
- Determine V_{BB} . (15%)
 - Find the input voltage v_I and explain the operating status of transistors M_n and M_p when $v_O = -12V$. (15%)




3. (25%)

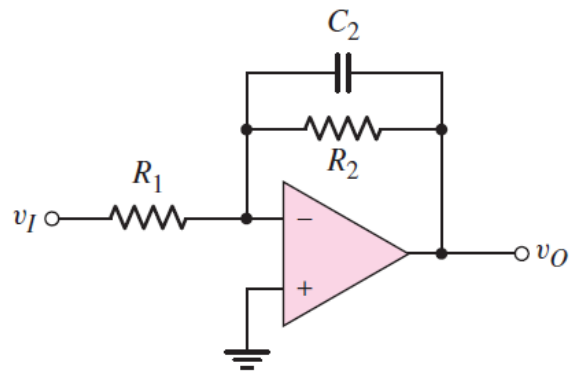- (a) Find the voltage transfer function of the right circuit in terms of the input signal frequency f . (10%)
- (b) Is the circuit a lowpass or a highpass filter and why? (5%)
- (c) Find the 3dB corner frequency. (10%)



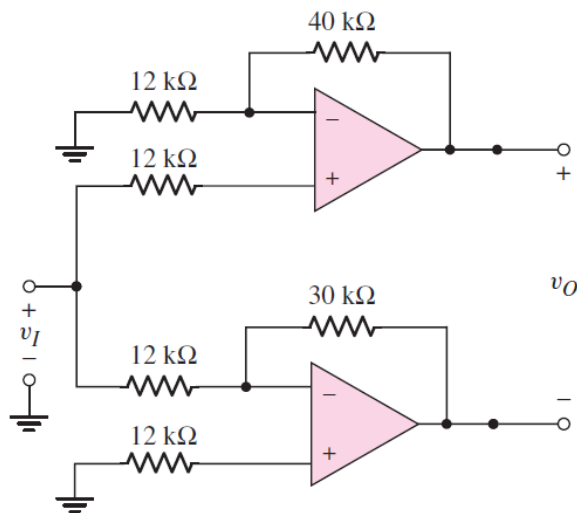4. (10%) Find the voltage gain v_O / v_I .



5. (15%)

- (a) Find the gain v_O / v_{cm} . (10%)
- (b) On what condition is the gain to be zero? (5%)

