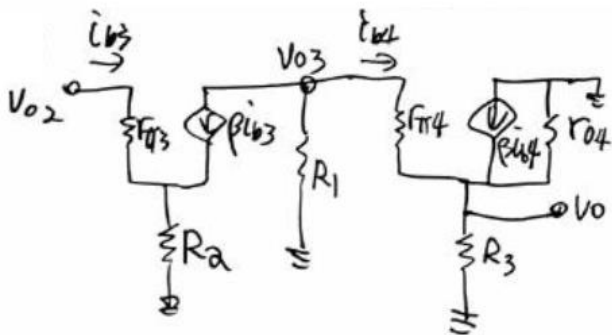


- (1)
(a)



$$v_{o2} = i_{b3} \cdot [\tau_{\pi 3} + (1 + \beta) R_2]$$

$$v_{o3} = -\beta i_{b3} [R_1 \parallel (\tau_{\pi 4} + (1 + \beta)(R_3 \parallel r_{o4}))]$$


$$v_{o3} = i_{b4} [\tau_{\pi 4} + (1 + \beta)(R_3 \parallel r_{o4})]$$

$$v_o = (1 + \beta) i_{b4} \cdot (R_3 \parallel r_{o4})$$

$$\frac{v_o}{v_{o2}} = \frac{v_{o3}}{v_{o2}} \cdot \frac{v_o}{v_{o3}}$$

$$= \frac{-\beta [R_1 \parallel (\tau_{\pi 4} + (1 + \beta)(R_3 \parallel r_{o4}))]}{\tau_{\pi 3} + (1 + \beta) R_2} \times \frac{(1 + \beta)(R_3 \parallel r_{o4})}{\tau_{\pi 4} + (1 + \beta)(R_3 \parallel r_{o4})}$$

- (b)

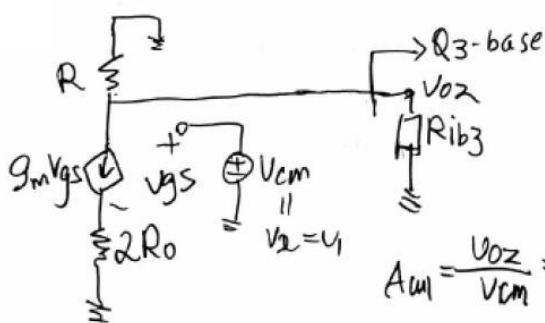

$$v_{cm} = v_{gs} + g_m v_{gs} \cdot 2 R_o$$


$$v_{gs} = \frac{v_{cm}}{1 + 2g_m R_o}$$

$$v_{o2} = -g_m v_{gs} [R \parallel (\tau_{\pi 3} + (1 + \beta) R_2)]$$

$$A_{cm} = \frac{v_{o2}}{v_{cm}} = \frac{-g_m [R \parallel (\tau_{\pi 3} + (1 + \beta) R_2)]}{1 + 2g_m R_o}$$

- (c)

$$A_d = \frac{v_{o2}}{v_d}$$

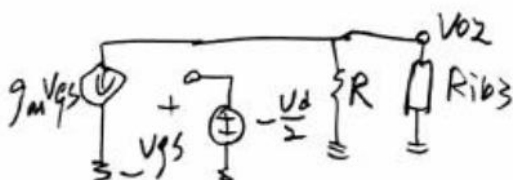

$$v_{o2} = \frac{1}{2} g_m v_d \cdot (R \parallel Rib_3)$$


$$A_d = \frac{1}{2} g_m (R \parallel Rib_3)$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \left| \frac{\frac{1}{2} g_m}{\frac{g_m}{1 + 2g_m R_o}} \right|$$

$$= \frac{1 + 2g_m R_o}{2}$$

$$CMR_{dB} = 20 \log_{10} \left(\frac{1 + 2g_m R_0}{2} \right)$$

(d)

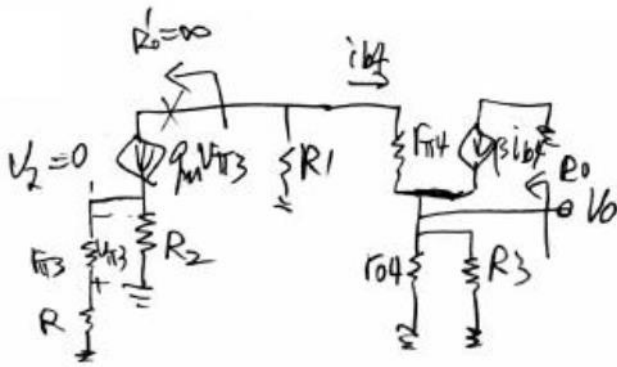

$$R_o = r_{o4} \parallel R_3 \parallel \frac{r_{\pi 4} + R_1}{1 + \beta}$$

(2)

$$I_{B5} = \frac{I_{E5}}{1 + \beta} = \frac{I_{B3} + I_{B4}}{1 + \beta} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)}$$

$$\text{Now } I_{C3} + I_{C4} \approx I_Q$$

$$\text{So } I_{B5} \approx \frac{I_Q}{\beta(1 + \beta)}$$

$$I_{B6} = \frac{I_{E6}}{1 + \beta} = \frac{I_{Q1}}{\beta(1 + \beta)}$$

For balance, we want $I_{B6} = I_{B5}$

So that $I_{Q1} = I_Q$

(3)

$$r_{\pi 11} = \frac{(120)(0.026)}{0.2} = 15.6 \text{ k}\Omega$$

$$R'_E = R_3 \parallel r_{\pi 11} = 0.2 \parallel 15.6 = 0.1975 \text{ k}\Omega$$

$$g_{m11} = \frac{0.2}{0.026} = 7.692 \text{ mA/V}$$

$$r_{o11} = \frac{V_{A11}}{I_{C11}} = \frac{120}{0.2} = 600 \text{ k}\Omega$$

$$R_{C11} = r_{o11} (1 + g_{m11} R'_E) = 600 [1 + (7.692)(0.1975)] = 1512 \text{ k}\Omega$$

$$R_{C7} = r_{o7} = \frac{V_{A7}}{I_{C7}} = \frac{60}{0.2} = 300 \text{ k}\Omega$$

$$Z = R_{C7} \parallel R_{C11} = 300 \parallel 1512 = 250 \text{ k}\Omega$$

$$r_{\pi 8} = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$I_{C9} = \frac{1}{120} \left(\frac{120}{121} \right) = 0.008264 \text{ mA}$$

$$r_{\pi 9} = \frac{(120)(0.026)}{0.008264} = 377.5 \text{ k}\Omega$$

$$\text{Now } R_o = R_4 \parallel \left[\frac{r_{\pi 8} + \left(\frac{r_{\pi 9} + Z}{121} \right)}{121} \right] = 5 \parallel \left[\frac{3.12 + \left(\frac{377.5 + 250}{121} \right)}{121} \right] = 5 \parallel 0.06864$$

$$\text{Or } R_o = 67.7 \Omega$$

(4)

4. (a) 参考课本 Example 11.18

$$I_{Q1} = 0.4 \text{ mA}$$

$$I_{C2} = 0.2 \text{ mA} \Rightarrow V_{O2} = 10 - I_{C2} \cdot R_{E2} = 6 \text{ V}$$

$$I_{R4} = \frac{V_{O2} - 2 \times 0.7}{R_4} = 0.4 \text{ mA} \approx I_{R5}$$

$$V_{O3} = 10 - 5 \cdot I_{R5} = 8 \text{ V}$$

$$V_{B6} = 8 - 0.7 - I_{Q1} \cdot R_6 = 8 - 0.7 - 0.4 \times 16.5 = 0.7 \text{ V}$$

$$\Rightarrow V_{O1} = 0.7 - 0.7 = 0 \text{ V}$$


(b) $R_{i2} = r_{\pi 3} + (1 + \beta) r_{\pi 4}$

$$r_{\pi 4} = \beta \cdot \frac{V_T}{I_{R4}} = 120 \cdot \frac{0.026}{0.4} = 7.8 \text{ k}\Omega$$

$$r_{\pi 3} = \beta \cdot \frac{V_T}{I_{R4} / \beta} = (120) \cdot r_{\pi 4} = 936 \text{ k}\Omega$$

$$R_{i2} = 936 + 121 \times 7.8 = 1880 \text{ k}\Omega$$

(c)

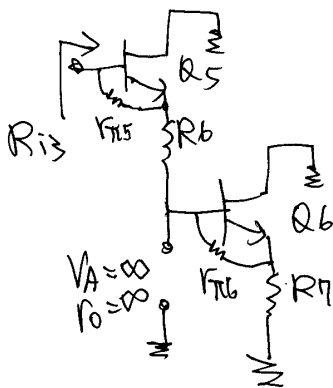

$$R_{i3} = r_{\pi 5} + (1 + \beta) (R_6 + r_{\pi 6} + (1 + \beta) R_7)$$

$$r_{\pi 5} = \beta \cdot \frac{V_T}{I_{R6}} = 120 \cdot \frac{0.026}{0.4} = 7.8 \text{ k}\Omega$$

$$I_{R7} = 10/5 = 2 \text{ mA}$$

$$r_{\pi 6} = \beta \cdot \frac{V_T}{I_{R7}} = 120 \cdot \frac{0.026}{2} = 1.56 \text{ k}\Omega$$

$$R_{i3} = 7.8 + 121 \cdot (16.5 + 1.56 + 121 \times 5) = 75.4 \text{ M}\Omega$$

(d) $A_d = A_{d1} \cdot A_{d2} \cdot A_{d3}$

$$A_{d1} = \frac{g_m}{2} \cdot (R_{C1} \parallel R_{i2}) = \frac{1}{4} \cdot \frac{0.4}{0.026} \cdot (20 \parallel 1880) = 76.11$$

$$A_{d2} = \frac{I_{R4}}{2V_T} \cdot (R_{C2} \parallel R_{i3}) = \frac{0.4}{2 \times 0.026} \cdot (5 \parallel 75.4 \times 10^3) = 38.46$$

$$A_{d3} \approx 1$$

$$A_d = 76.11 \times 38.46 = 2927$$