

(1)

$$R_{TH} = R_1 \parallel R_2 = 40 \parallel 5 = 4.44 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{5}{5 + 40} \right) (10) = 1.111 \text{ V}$$

$$I_{BQ} = \frac{1.111 - 0.7}{4.44 + (121)(0.5)} = 0.00633 \text{ mA}$$

$$I_{CQ} = 0.760 \text{ mA}$$

$$r_{\pi} = \frac{(120)(0.026)}{0.760} = 4.11 \text{ k}\Omega$$

$$g_m = \frac{0.760}{0.026} = 29.23 \text{ mA/V}$$

$$r_o = \infty$$

$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})}$$

$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_T} = \frac{29.23 \times 10^{-3}}{2\pi(250 \times 10^6)}$$

$$C_{\pi} + C_{\mu} = 18.6 \text{ pF}; C_{\mu} = 3 \text{ pF} \Rightarrow C_{\pi} = 15.6 \text{ pF}$$

$$C_M = C_{\mu} [1 + g_m(R_C \parallel R_L)]$$

$$C_M = 3 [1 + (29.2)(5 \parallel 2.5)] \Rightarrow C_M = 149 \text{ pF}$$

For upper frequency:

$$\tau_H = R_{eq}(C_{\pi} + C_M)$$

$$R_{eq} = r_{\pi} \parallel R_1 \parallel R_2 \parallel R_S = 4.11 \parallel 40 \parallel 5 \parallel 0.5$$

$$R_{eq} = 0.405 \text{ k}\Omega$$

$$\tau_H = (0.405 \times 10^3)(15.6 + 149) \times 10^{-12}$$

$$= 6.67 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} \Rightarrow f_H = 2.39 \text{ MHz}$$

For lower frequency:


$$\tau_L = R_{eq}C_{C1}$$

$$R_{eq} = R_S + R_1 \parallel R_2 \parallel r_{\pi} = 0.5 + 40 \parallel 5 \parallel 4.11$$

$$R_{eq} = 2.64 \text{ k}\Omega$$

$$\tau_L = (2.64 \times 10^3)(4.7 \times 10^{-6}) = 1.24 \times 10^{-2} \text{ s}$$
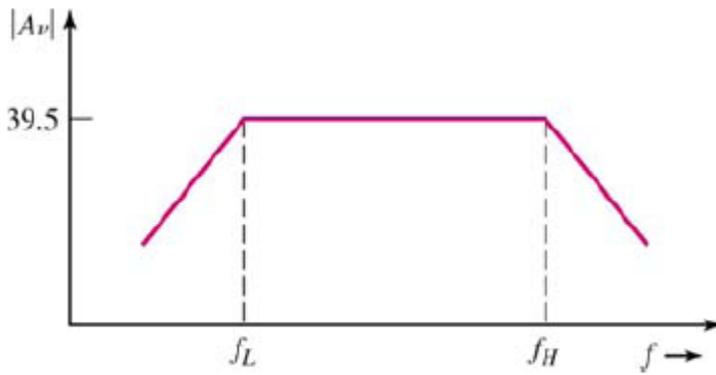
$$f_L = \frac{1}{2\pi\tau_L} \Rightarrow f_L = 12.8 \text{ Hz}$$



$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_\pi = \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) V_i$$

$$V_\pi = \left(\frac{2.135}{2.135 + 0.5} \right) V_i = 0.8102 V_i$$

$$|A_v| = (29.23)(0.8102)(5 \parallel 2.5)$$

$$\underline{|A_v| = 39.5}$$

(2)

$$I_D = K_P (V_{SG} + V_{TP})^2 = \frac{9 - V_{SG}}{R_S}$$

$$(2)(1.2)(V_{SG}^2 - 4V_{SG} + 4) = 9 - V_{SG}$$

$$2.4V_{SG}^2 - 8.6V_{SG} + 0.6 = 0$$

$$V_{SG} = \frac{8.6 \pm \sqrt{(8.6)^2 - 4(2.4)(0.6)}}{2(2.4)}$$

$$V_{SG} = 3.512 \text{ V}$$

$$g_m = 2K_P (V_{SG} + V_{TP}) = 2(2)(3.512 - 2)$$

$$g_m = 6.049 \text{ mA/V}$$

$$I_D = (2)(3.512 - 2)^2 = 4.572 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_o} = \frac{1}{(0.01)(4.56)} \Rightarrow r_o = 21.9 \text{ k}\Omega$$

$$C_M = C_{gdT} (1 + g_m (r_o \parallel R_D))$$

$$C_M = (1) [1 + (6.04)(21.9 \parallel 1)] \Rightarrow \underline{C_M = 6.785 \text{ pF}}$$

$$\tau_H = (R_i \parallel R_G)(C_{gsT} + C_M)$$

$$\tau_H = (2 \parallel 100) \times 10^3 \times (10 + 6.78) \times 10^{-12}$$

$$\tau_H = 3.29 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} \Rightarrow f_H = 4.84 \text{ MHz}$$

$$V_o = -g_m(r_o \parallel R_D) \cdot V_{gs}$$

$$V_{gs} = \left(\frac{R_G}{R_G + R_i} \right) \cdot V_i = \left(\frac{100}{102} \right) \cdot V_i$$

$$A_v = -(6.04) \left(\frac{100}{102} \right) (21.9 \parallel 1)$$

$$A_v = -5.67$$

(3)

The dc analysis

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)(10)} = 0.00838 \text{ mA}$$

$$I_{CQ} = 0.838 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.838} = 3.10 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 32.22 \text{ mA/V}$$

For the input

$$\tau_{p\pi} = \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right] C_\pi = \left[\left(\frac{3.10}{101} \right) \parallel 10 \parallel 1 \right] \times 10^3 \times 24 \times 10^{-12}$$

$$= 7.13 \times 10^{-10} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi\tau_{p\pi}} = \frac{1}{2\pi(7.13 \times 10^{-10})} \Rightarrow f_{H\pi} = 223 \text{ MHz}$$

For the output

$$\begin{aligned}\tau_{p\mu} &= (R_C \parallel R_L) C_\mu = (10 \parallel 1) \times 10^3 \times 3 \times 10^{-12} \\ &= 2.73 \times 10^{-9} \text{ s}\end{aligned}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{p\mu}} = \frac{1}{2\pi(2.73 \times 10^{-9})} \Rightarrow f_{H\mu} = 58.4 \text{ MHz}$$

$$\begin{aligned}(A_v)_M &= g_m (R_C \parallel R_L) \left[\frac{R_E \parallel \left(\frac{r_\pi}{1+\beta} \right)}{R_E \parallel \left(\frac{r_\pi}{1+\beta} \right) + R_S} \right] \\ &= (32.22)(10 \parallel 1) \left[\frac{10 \parallel \left(\frac{3.1}{101} \right)}{10 \parallel \left(\frac{3.1}{101} \right) + 1} \right] \Rightarrow (A_v)_M = 0.870\end{aligned}$$