
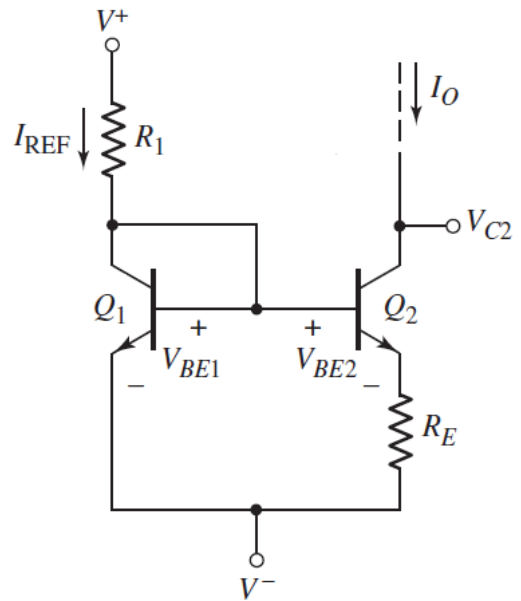


Electronics II, Exam-3, Spring 2023
 Department of Communication Engineering, National Central University
 May 12, 2023, Prof. Dah-Chung Chang (E1-311)

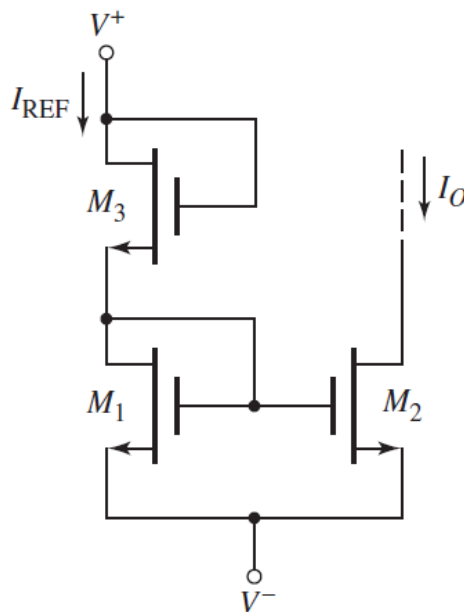
1. (25%) The parameters of the circuit are: $V^+ = 5V$, $V^- = 0$, $I_{REF} = 0.7mA$, and $I_O = 25\mu A$ at $V_{C2} = 1V$. The transistor parameters are: $\beta = 150$, $V_{BE1(on)} = 0.7V$, and $V_A = 100V$. Determine the change in I_O when V_{C2} changes from 1V to 4V.



2. (25%) The bias voltages of the circuit are $V^+ = 1.8V$ and $V^- = -1.8V$, and the transistor parameters are $V_{TN} = 0.4V$, $k'_n = 100\mu A/V^2$, and $\lambda = 0$. Find those W/L ratios for three transistors such that $I_{REF} = 0.5mA$ and $I_O = 0.1mA$, and that M_2 remains biased in the saturation region for $V_{DS2} \geq 0.4V$.



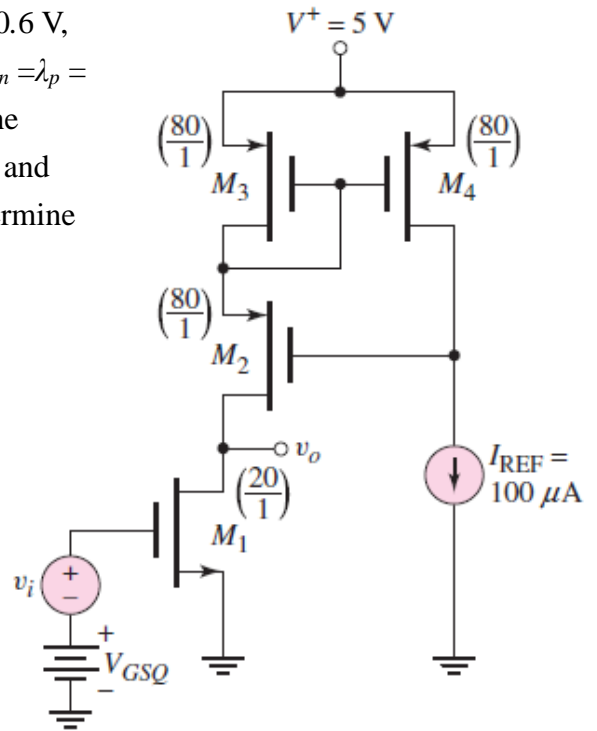3. (25%) The parameters of the transistors are $V_{TN} = 0.6 \text{ V}$, $V_{TP} = -0.6 \text{ V}$, $k'_n = 100 \mu\text{A}/\text{V}^2$, $k'_p = 60 \mu\text{A}/\text{V}^2$, and $\lambda_n = \lambda_p = 0.02 \text{ V}^{-1}$. The width-to-length ratios are shown in the figure. The value of V_{GSQ} is such that $I_{D1} = 100 \mu\text{A}$, and M_1 and M_2 are biased in the saturation region. Determine the small-signal voltage gain $A_v = v_o/v_i$.



4. (25%) The bias voltage of the MOSFET amplifier with active load is $V^+ = 3 \text{ V}$. The transistor parameters are $V_{TN} = 0.5 \text{ V}$, $V_{TP} = -0.5 \text{ V}$, $k'_n = 100 \mu\text{A}/\text{V}^2$, $k'_p = 60 \mu\text{A}/\text{V}^2$, and $\lambda_n = \lambda_p = 0.02 \text{ V}^{-1}$. The quiescent values are $V_O = 1.5 \text{ V}$ and $V_I = 1.2 \text{ V}$.
- Find the three transistor W/L ratios, such that $I_{REF} = I_O = 100 \mu\text{A}$. Assume M_1 and M_2 are matched. (15%)
 - Determine the small-signal voltage gain $A_v = v_o/v_i$. (10%)

