

1.

a. Neglecting base currents

$$I_1 = I_3 = 400 \mu\text{A} \Rightarrow R_1 = \frac{30 - 0.7}{0.4} \Rightarrow \underline{R_1 = 73.25 \text{ k}\Omega}$$

$$V_{CE1} = 10 \text{ V} \Rightarrow V_{C1} = 9.3 \text{ V}$$

$$R_C = \frac{15 - 9.3}{0.2} \Rightarrow \underline{R_C = 28.5 \text{ k}\Omega}$$

b.

$$r_\pi = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$r_0(Q_3) = \frac{50}{0.4} = 125 \text{ k}\Omega$$

We have

$$A_d = \frac{\beta R_C}{2(r_\pi + R_B)} = \frac{(100)(28.5)}{2(13+10)} \Rightarrow \underline{A_d = 62}$$


$$A_{cm} = -\frac{\beta R_C}{r_\pi + R_B} \left\{ \frac{1}{1 + \frac{2r_0(1+\beta)}{r_\pi + R_B}} \right\}$$

$$= -\frac{(100)(28.5)}{13+10} \left\{ \frac{1}{1 + \frac{2(125)(101)}{13+10}} \right\} \Rightarrow \underline{A_{cm} = -0.113}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{62}{0.113} \right) \Rightarrow \underline{CMRR_{dB} = 54.8 \text{ dB}}$$

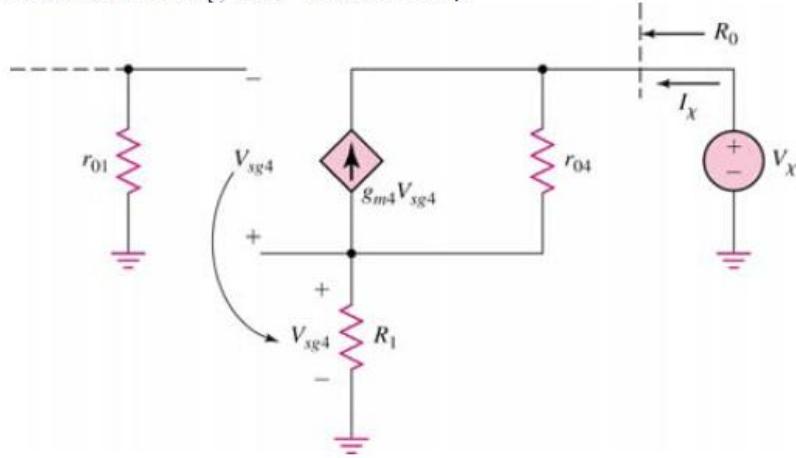2.

Resistance looking into drain of  $M_4$ .



$$V_{sg4} \cong I_X R_1$$

$$I_X + g_{m4} V_{sg4} = \frac{V_X - V_{sg4}}{r_{o4}}$$

$$I_X \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right] = \frac{V_X}{r_{o4}}$$

$$\text{Or } R_o = r_{o4} \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right]$$

$$A_d = g_{m2} (r_{o2} \| R_o)$$

$$g_{m2} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.080)(0.1)} \\ = 0.179 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$g_{m4} = 2\sqrt{K_P I_{DQ}} = 2\sqrt{(0.080)(0.1)} \\ = 0.179 \text{ mA/V}$$

$$r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$R_0 = 500 \left[ 1 + (0.179)(1) + \frac{1}{500} \right] = 590.5 \text{ k}\Omega$$

$$A_d = (0.179)[667 \| 590.5] \Rightarrow \underline{\underline{A_d = 56.06}}$$

3.

$$I_{CQ3} = 0.25 \text{ mA, and } I_{CQ4} = 2 \text{ mA.}$$

$$A_{d1} = \frac{v_o}{v_d} = \frac{g_m}{2} (R \parallel r_{\pi 3})$$

$$g_m = \frac{0.25}{0.026} = 9.615 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(120)(0.026)}{0.25} = 12.48 \text{ k}\Omega$$

$$A_{d1} = \frac{(9.615)}{2} (20 \parallel 12.48) = 36.94$$

$$A_3 = -g_m (R_C \parallel R_{i4})$$

$$R_{i4} = r_{\pi 4} + (1 + \beta) R_{E2}$$

$$g_m = \frac{0.25}{0.026} = 9.615 \text{ mA/V}$$

$$r_{\pi 4} = \frac{(120)(0.026)}{2} = 1.56 \text{ k}\Omega$$

$$R_{i4} = 1.56 + (121)(2.5) = 304 \text{ k}\Omega$$

$$A_3 = -(9.615)(17.2 \parallel 304) = -156.5$$

$$A_4 = \frac{(1 + \beta) R_{E2}}{r_{\pi 4} + (1 + \beta) R_{E2}} = \frac{(121)(2.5)}{1.56 + (121)(2.5)} = 0.995$$

---

Now  $A_d = \frac{v_o}{v_d} = A_{d1} \cdot A_3 \cdot A_4 = (36.94)(-156.5)(0.995) = -5752$

4.

$$v_{o1} = -g_{m1}(r_{o1} \parallel R_{o3} \left( \frac{v_d}{2} \right))$$

$$A_{d1} = \frac{v_{o1}}{v_d} = -\frac{1}{2} g_{m1}(r_{o1} \parallel R_{o3})$$

$$g_{m1} = \frac{I_{CQ}}{V_T} = \frac{0.2}{0.026} = 7.692 \text{ mA/V}$$

$$r_{o1} = \frac{V_{A1}}{I_{CQ}} = \frac{120}{0.2} = 600 \text{ k}\Omega$$

$$R_{o3} = r_{o3} \parallel r_{\pi3} \left( \frac{1}{g_{m3}} \right), \text{ where } g_{m3} = 7.692 \text{ mA/V},$$

$$r_{\pi3} = \frac{(120)(0.026)}{0.2} = 15.6 \text{ k}\Omega, \quad r_{o3} = 400 \text{ k}\Omega$$

$$\text{Then } R_{o3} = 400 \left( 15.6 \right) \left( \frac{1}{7.692} \right) = 15.014 \parallel 0.130 = 0.1289 \text{ k}\Omega$$

$$A_{d1} = -\frac{1}{2} (7.692)(600 \parallel 0.1289) = -0.4956$$

$$A_{d2} = +\frac{1}{2} g_{m2}(r_{o2} \parallel R_{o4}) = +0.4956$$