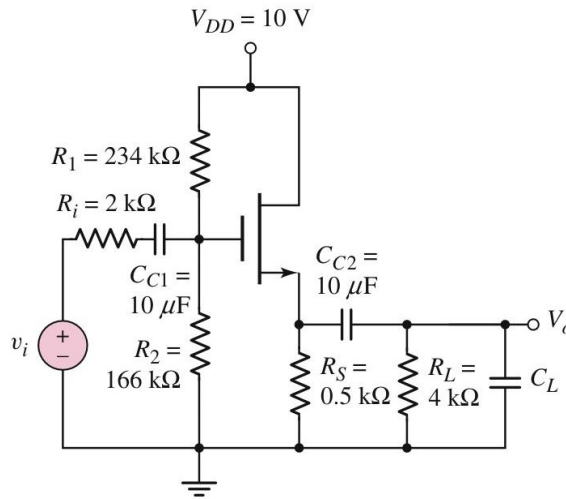


**Electronics II, Midterm, Spring 2024**  
 Department of Communication Engineering, National Central University  
 March 29, 2024, Prof. Dah-Chung Chang (E1-311)


---

1. (25%) Let  $K_n = 0.5\text{mA}/\text{V}^2$ ,  $V_{TN} = 2\text{V}$ , and  $\lambda = 0$ .
- Determine the maximum value of  $C_L$  such that the bandwidth is at least 5MHz. (15%)
  - What is the magnitude of the small-signal midband voltage gain? (10%)




Copyright © The McGraw-Hill Companies, Inc.  
 Permission required for reproduction or display.

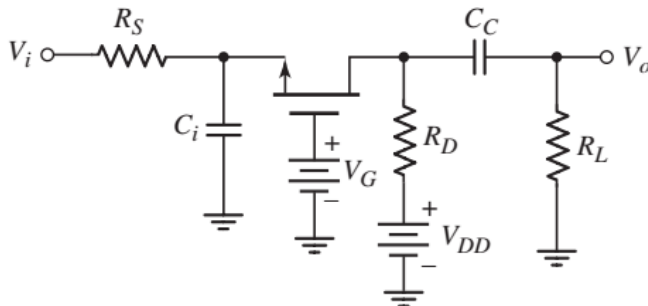2. (25%) Consider the circuit as shown below.
- Derive the transfer function  $T(s) = V_o(s) / V_i(s)$ , assuming  $\lambda = 0$  for the transistor. Determine the expression for the time constant associated with the input portion of the circuit. (15%)
  - Determine the expression for the time constant associated with the output portion of the circuit. **You need to explain the equivalent resistance in the time constant, or you will not get the score.** (10%)



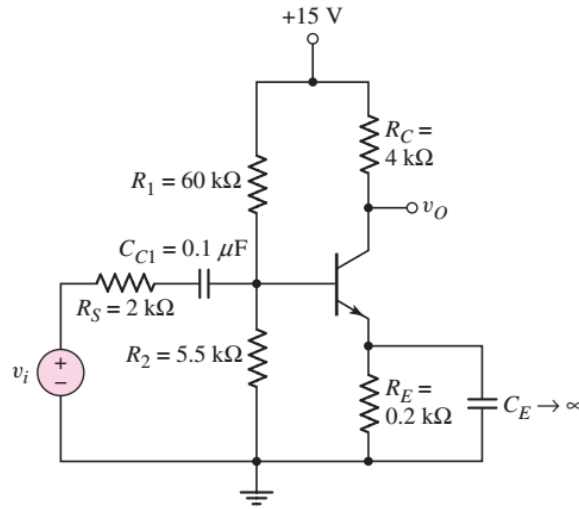3. (25%) Assume the emitter bypass capacitor is very large, and the transistor parameters are:  $\beta = 100$ ,  $V_{BE(on)} = 0.7V$ ,  $V_A = \infty$ ,  $C_\mu = 2pF$ , and  $f_T = 400MHz$ . Determine the lower and upper 3 dB frequencies for the small-signal voltage gain.



4. (25%) Assume that  $C_{C1}$ ,  $C_E$ , and  $C_{C2}$  acts as short circuits in this high frequency analysis.
- Derive the 3dB upper corner frequencies in terms of the transistor capacitors  $C_\mu$  and  $C_\pi$ . (10%)
  - Derive the midband voltage gain. (5%)
  - The circuit parameters are  $V^+ = 10V$ ,  $V^- = -10V$ ,  $R_S = 0.1k\Omega$ ,  $R_1 = 42.5k\Omega$ ,  $R_2 = 20.5k\Omega$ ,  $R_3 = 28.3k\Omega$ ,  $R_E = 5.4k\Omega$ ,  $R_C = 5k\Omega$ , and  $R_L = 10k\Omega$ . The transistor parameters are  $\beta_o = 150$ ,  $V_{BE(ON)} = 0.7V$ ,  $C_\pi = 12pF$ , and  $C_\mu = 2pF$ . Given that the quiescent collector current  $I_{CQ} = 1.02mA$ , determine the values of 3dB upper corner frequency for  $C_L$  acting as an open circuit and for  $C_L = 15pF$ . (10%)

