

(1)

(a)

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{166}{166 + 234} \right) (10) \\ = 4.15 \text{ V}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$4.15 - V_{GS} = (0.5)(0.5)(V_{GS}^2 - 4V_{GS} + 4)$$

$$0.25V_{GS}^2 - 3.15 = 0 \Rightarrow V_{GS} = 3.55 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.5)(3.55 - 2)$$

$$g_m = 1.55 \text{ mA/V}$$

$$R_0 = R_S \parallel \frac{1}{g_m} = 0.5 \parallel \frac{1}{1.55} = 0.5 \parallel 0.645$$


$$R_0 = 0.282 \text{ k}\Omega$$

$$r = (R_0 \parallel R_L) C_L \text{ and } f_H = \frac{1}{2\pi r}$$

$$\beta\omega \approx f_H = 5 \text{ MHz} \Rightarrow r = \frac{1}{2\pi(5 \times 10^6)} = 3.18 \times 10^{-8} \text{ s}$$

$$C_L = \frac{r}{R_0 \parallel R_L} = \frac{3.18 \times 10^{-8}}{(0.282 \parallel 4) \times 10^3} \Rightarrow \underline{C_L = 121 \text{ pF}}$$

(b)

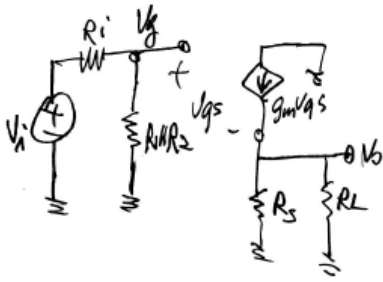

$$V_g = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \cdot V_i$$

$$V_g = V_{gs} + g_m (R_S \parallel R_L) V_{gs}$$

$$= [1 + g_m (R_S \parallel R_L)] \cdot V_{gs}$$

$$V_o = g_m (R_S \parallel R_L) V_{gs}$$

$$= g_m (R_S \parallel R_L) \cdot \frac{V_g}{1 + g_m (R_S \parallel R_L)}$$

$$\Rightarrow A_v = \frac{V_o}{V_i} = \frac{g_m (R_S \parallel R_L)}{1 + g_m (R_S \parallel R_L)} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i}$$

$$g_m = 1.55 \text{ mA/V}$$

$$R_S \parallel R_L = \frac{2}{4.5} = 0.445 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 99.11 \text{ k}\Omega$$

$$A_v = \frac{1.55 \times 0.445}{1 + 1.55 \times 0.445} \times \frac{99.11}{99.11 + 2} = 0.4$$

(2)

$$(a) \frac{V_{gs}}{V_i} = \frac{-\left(\frac{1}{g_m} \parallel \frac{1}{sC_i}\right)}{\left(\frac{1}{g_m} \parallel \frac{1}{sC_i}\right) + R_S}$$

$$\text{Now } \left( \frac{1}{g_m} \parallel \frac{1}{sC_i} \right) = \frac{\left( \frac{1}{g_m} \right) \left( \frac{1}{sC_i} \right)}{\frac{1}{g_m} + \frac{1}{sC_i}} = \frac{\frac{1}{g_m}}{1 + s \left( \frac{1}{g_m} \right) C_i}$$

$$\text{So } \frac{V_{gs}}{V_i} = \frac{-\frac{1}{g_m}}{\frac{1}{g_m} + R_S \left( 1 + s \left( \frac{1}{g_m} \right) C_i \right)} = \left( \frac{-\frac{1}{g_m}}{\frac{1}{g_m} + R_S} \right) \cdot \frac{1}{\left[ 1 + s \left( \frac{1}{g_m} \parallel R_S \right) C_i \right]}$$

We have

$$V_o = -g_m V_{gs} \left[ \frac{R_D}{R_D + R_L + \frac{1}{sC_C}} \right] \cdot R_L = -g_m V_{gs} \left[ \frac{R_D R_L (sC_C)}{1 + s(R_D + R_L)C_C} \right]$$

$$V_o = -g_m V_{gs} \left( \frac{R_D R_L}{R_D + R_L} \right) \left[ \frac{s(R_D + R_L)C_C}{1 + s(R_D + R_L)C_C} \right]$$

$$\text{Then } T(s) = \frac{V_o(s)}{V_i(s)} = \frac{+g_m (R_D \parallel R_L)}{1 + g_m R_S} \cdot \frac{1}{\left[ 1 + s \left( \frac{1}{g_m} \parallel R_S \right) C_i \right]} \cdot \left[ \frac{s(R_D + R_L)C_C}{1 + s(R_D + R_L)C_C} \right]$$

$$\tau = \left( \frac{1}{g_m} \parallel R_S \right) C_i$$

(b)

$$\tau = (R_D + R_L) C_C$$

Notice: You need to explain why the output resistance looking into the drain is **infinity**.

We have explained this several times in class. Please refer to our class video.

**The score is 0 if the answer is given without definitely explaining the reason!!**

(3)

$$R_{TH} = R_1 \parallel R_2 = 60 \parallel 5.5 = 5.04 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5.5}{5.5 + 60} \right) (15) = 1.26 \text{ V}$$

$$I_{BQ} = \frac{1.26 - 0.7}{5.04 + (101)(0.2)} = 0.0222 \text{ mA}$$

$$I_{CQ} = 2.22 \text{ mA}$$

$$r_{\pi} = \frac{(100)(0.026)}{2.22} = 1.17 \text{ k}\Omega$$

$$g_m = \frac{2.22}{0.026} = 85.4 \text{ mA/V}$$

Lower 3 - dB frequency:

$$\tau_L = R_{eq} \cdot C_{C1}$$

$$R_{eq} = R_S + R_1 \parallel R_2 \parallel r_{\pi} \\ = 2 + 60 \parallel 5.5 \parallel 1.17 = 2.95 \text{ k}\Omega$$

$$\tau_L = (2.95 \times 10^3) (0.1 \times 10^{-6}) = 2.95 \times 10^{-4} \text{ s}$$

$$f_L = \frac{1}{2\pi\tau_L} = \frac{1}{2\pi(2.95 \times 10^{-4})} \Rightarrow f_L = 540 \text{ Hz}$$

Upper 3 - dB frequency:

$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})} \Rightarrow 400 \times 10^6 = \frac{85.4 \times 10^{-3}}{2\pi(C_{\pi} + C_{\mu})}$$

$$C_{\pi} + C_{\mu} = 34 \text{ pF}; \quad C_{\mu} = 2 \text{ pF}; \quad C_{\pi} = 32 \text{ pF}$$

$$C_M = C_{\mu} (1 + g_m R_C) = 2 [1 + (85.4)(4)] \Rightarrow C_M = 685 \text{ pF}$$


$$C_i = C_{\pi} + C_M = 32 + 685 = 717 \text{ pF}$$

$$R_{eq} = R_S \parallel R_1 \parallel R_2 \parallel r_{\pi} = 2 \parallel 60 \parallel 5.5 \parallel 1.17 \Rightarrow R_{eq} = 0.644 \text{ k}\Omega$$

$$\tau = R_{eq} \cdot C_i = (0.644 \times 10^3) (717 \times 10^{-12}) \\ = 4.62 \times 10^{-7} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} \Rightarrow f_H = 344 \text{ kHz}$$

(4)

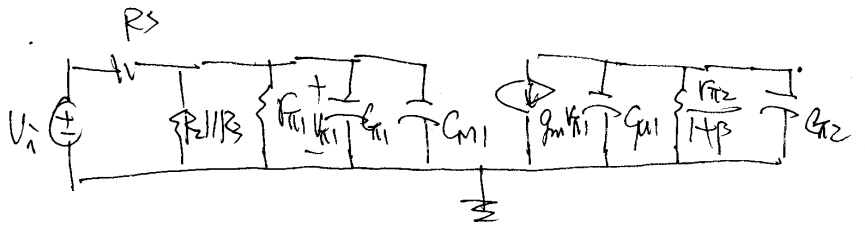


$$C_{M1} = C_{\pi 1} \left( 1 + \frac{g_{m2} r_{\pi 2}}{1 + \beta} \right) = 2 C_{\pi 1}$$

$$\tau_{\pi 1} = (R_S \parallel R_2 \parallel R_3 \parallel r_{\pi 1}) \cdot (C_{\pi 1} + C_{M1})$$

$$f_{H\pi} = \frac{1}{2\pi (R_S \parallel R_2 \parallel R_3 \parallel r_{\pi 1}) (C_{\pi 1} + 2C_{\pi 1})} \quad *$$
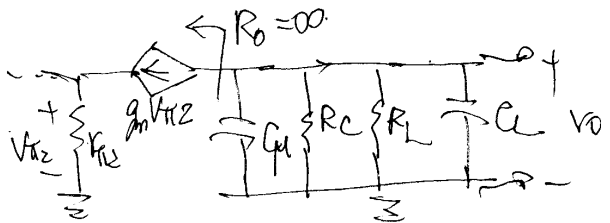
$$r_{\pi} = \frac{I_{CQ}}{V_T}, \quad C_{\pi 1} = C_{\pi}, \quad C_{M1} = C_M$$



$$\tau_M = (R_C \parallel R_L) (C_M + C_L)$$

$$f_{HM} = \frac{1}{2\pi \tau_M} = \frac{1}{2\pi (R_C \parallel R_L) (C_M + C_L)} \quad *$$

$$\begin{aligned} (b) \quad V_o &= -g_m (R_C \parallel R_L) \cdot v_{\pi 2} \\ &= -g_m (R_C \parallel R_L) \cdot \frac{g_{m1} r_{\pi 2}}{1 + \beta} v_{\pi 1} \\ &= -g_m (R_C \parallel R_L) \cdot \frac{g_{m1} r_{\pi 2}}{R_2 \parallel R_3 \parallel r_{\pi 1} + R_S} V_i \end{aligned}$$

$A_V$

$$\begin{aligned} r_{\pi} &= 120 \times \frac{0.026}{1.02} \\ &= 3 \text{ k} \end{aligned}$$

(c) ①  $C_L \rightarrow 0$ 

$$\begin{aligned} f_{HX} &= \frac{10^9}{2\pi \cdot (0.1 \parallel 20.5 \parallel 28.3 \parallel 3) \cdot (12 + 4)} \\ &= \frac{10^9}{2 \times 3.14 \times 0.096 \times 16} = 103.67 \text{ MHz} \end{aligned}$$

$$f_{HM} = \frac{10^9}{2\pi \times (5 \parallel 10) \times 2} = \frac{10^9}{2 \times 3.14 \times 3.33 \times 2} = 23.9 \text{ MHz (dominant)}$$

②  $C_L = 15 \text{ pF}$ 

$$f_{HM} = \frac{10^9}{2\pi \times 3.33 \times 17} = 2.8 \text{ MHz (dominant)}$$