
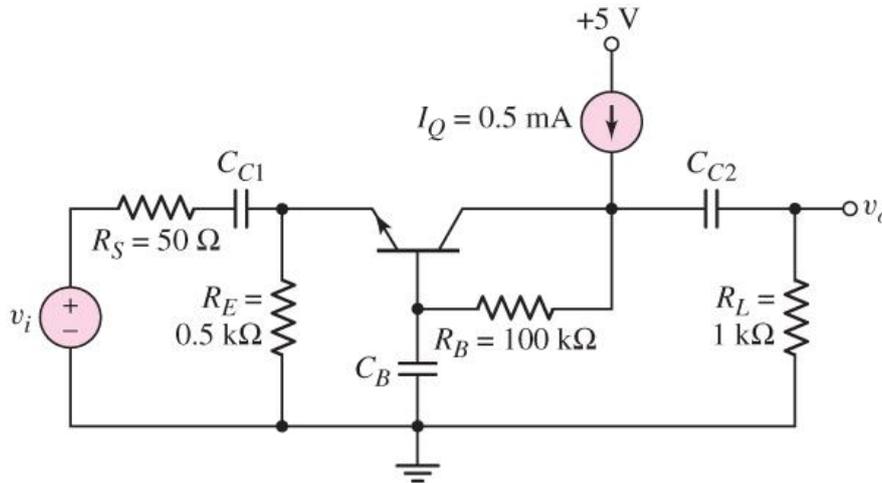


Electronics II, Exam-1, Spring 2020
 Department of Communication Engineering, National Central University
 April 10, 2020, Dr. Dah-Chung Chang (E1-311)

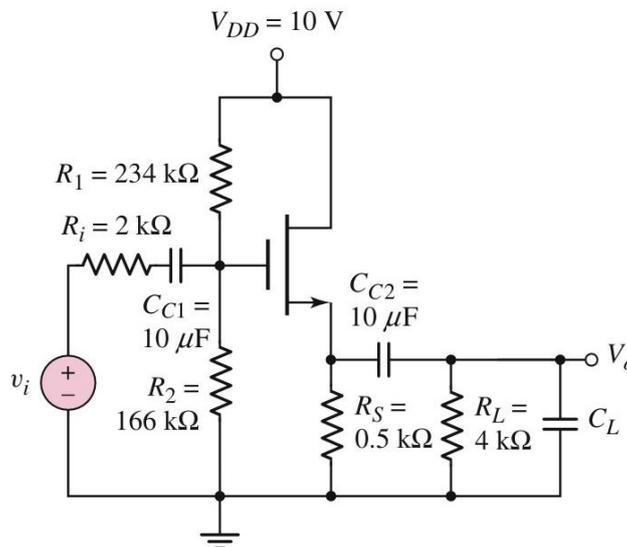1. (35%) The transistor parameters are $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_A = \infty$, $C_\pi = 10pF$, and $C_\mu = 1pF$.
- Determine the upper 3dB frequencies corresponding to the input and output portions of the equivalent circuit. (20%)
 - Calculate the midband small-signal voltage gain? (15%)
 (Assume that the signal frequency is sufficiently high such that the outside capacitors connected to the transistor can be treated as short circuits).



2. (35%) Let $K_n = 0.5mA/V^2$, $V_{TN} = 2V$, and $\lambda = 0$.
- Determine the maximum value of C_L such that the bandwidth is at least 5MHz. (20%)
 - What is the magnitude of the small-signal midband voltage gain? (15%)



Copyright © The McGraw-Hill Companies, Inc.
 Permission required for reproduction or display.

3. (30%) The transistor parameters are $\beta = 120$, $V_{BE(\text{on})} = 0.7\text{V}$, $V_A = \infty$, $C_\mu = 3\text{pF}$, and $f_T = 250\text{MHz}$. Determine the lower and upper corner 3dB frequencies.

