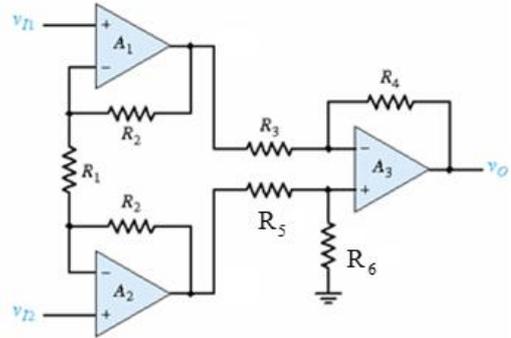



1. (25%) Consider the following instrumentation amplifier.

- (a) Assume that $R_4 / R_3 = R_6 / R_5$. Find v_o in relation of v_{I1} and v_{I2} . (10%)
- (b) Assume that $R_2 / R_1 = 1$, $R_4 / R_3 = 10$, and $R_6 / R_5 = 12$. Determine CMRR(dB). (15%)



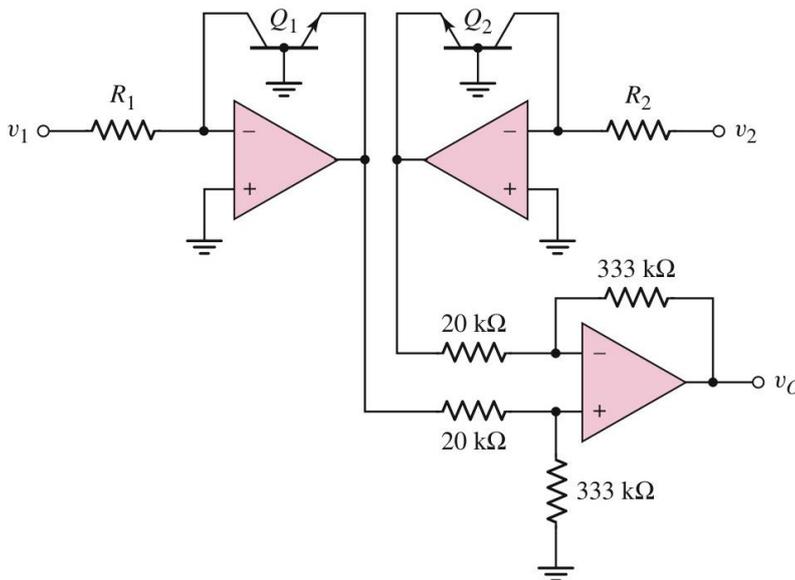
2. (25%) Let the semiconductor parameter for the transistor be $V_T = 0.026V$. Derive the following result

$$v_o = 0.4329 \ln \left(\frac{v_2 R_1}{v_1 R_2} \right).$$



3. (20%) The output of the voltage reference circuit is 10V. Use a Zener diode with a breakdown voltage of 6V. Assume that the Zener diode is biased at the current range of 1 mA to 1.5mA and the PN diode cut-in voltage is 0.6V. The resistor parameters are $R_3 = 10K\Omega$ and $R_4 = 30K\Omega$.

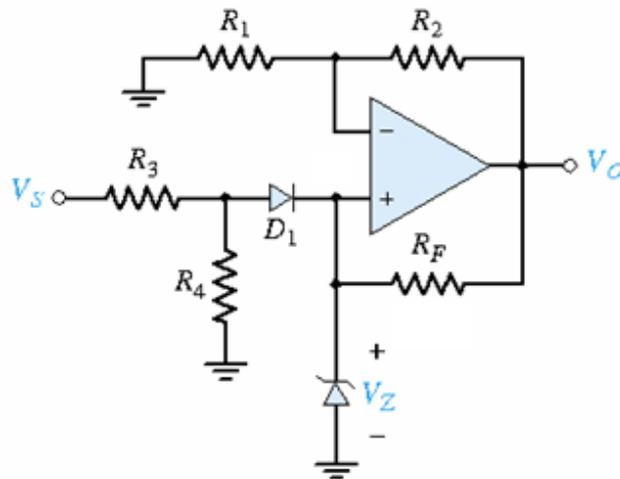- (a) Find the ratio of R_2 / R_1 and the value of R_F . (10%)
 (b) Find the possible current values supplied by V_S . (10%)



4. (20%)

Consider a power MOSFET for which the thermal resistance parameters are:

$$\theta_{\text{dev-case}} = 1.75 \text{ }^\circ\text{C/W} \quad \theta_{\text{case-snk}} = 1 \text{ }^\circ\text{C/W}$$

$$\theta_{\text{snk-amb}} = 5 \text{ }^\circ\text{C/W} \quad \theta_{\text{case-amb}} = 50 \text{ }^\circ\text{C/W}$$

The ambient temperature is $T_{\text{amb}} = 30 \text{ }^\circ\text{C}$, and the maximum junction or device temperature is $T_{j,\text{max}} = T_{\text{dev}} = 150 \text{ }^\circ\text{C}$.

Determine

- (a) the maximum power dissipation in a transistor, with and without the heat sink. (10%)
 (b) the temperature of the transistor case and heat sink. (10%)
5. (10%) For the common-emitter output stage shown on the right, let $V_{CC} = 12 \text{ V}$ and $R_L = 1 \text{ k}\Omega$. Assume the transistor Q-point is in the center of the load line. Assume the sinusoidal output voltage is limited to a 9 V peak-to-peak value. Determine the power conversion efficiency.

